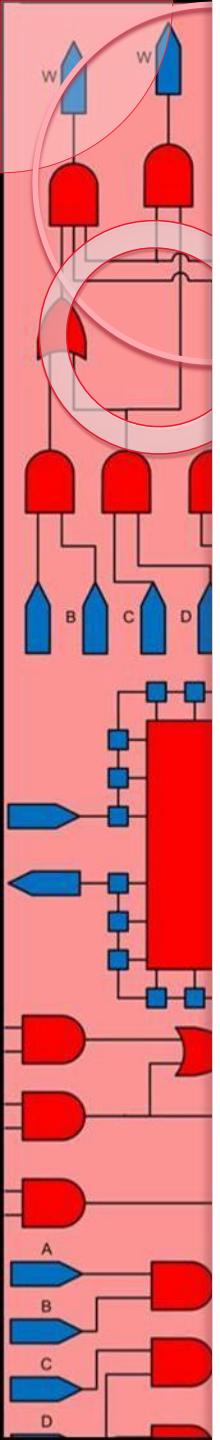


Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 1: Verilog as a Design Tool



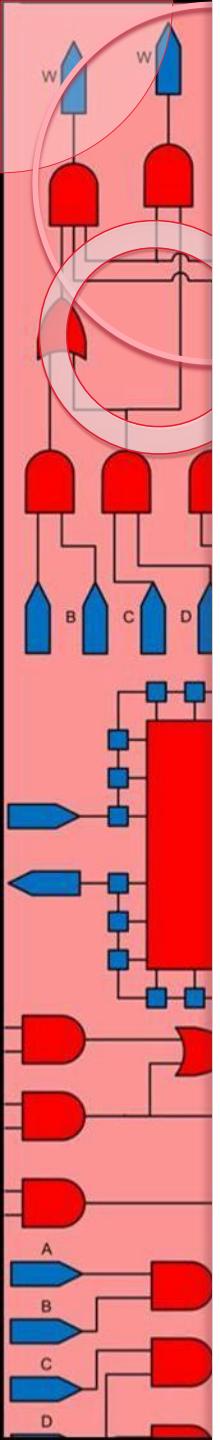
# Verilog as a Design Tool


- Simulation
- Synthesis
- Language
- A simulation Environment
- Summary



# Verilog as a Design Tool


## Verilog for simulation

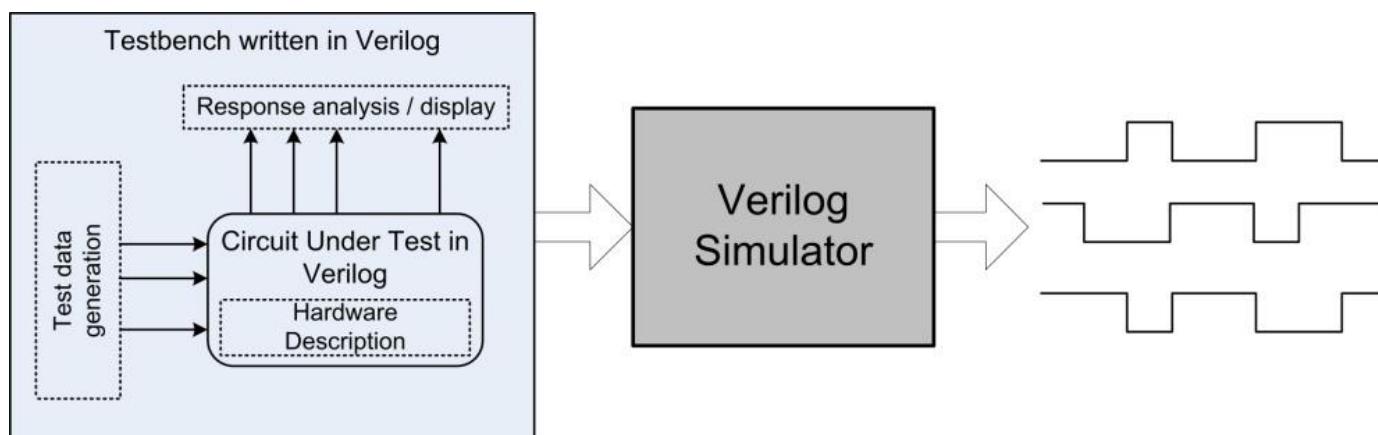


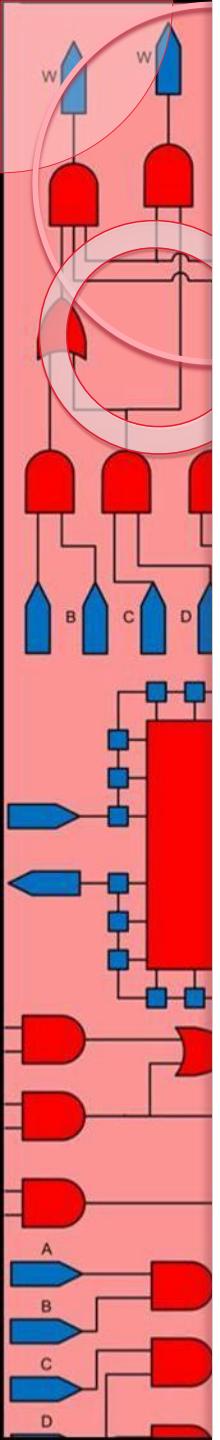

# Verilog as a Design Tool

## Verilog for Synthesis

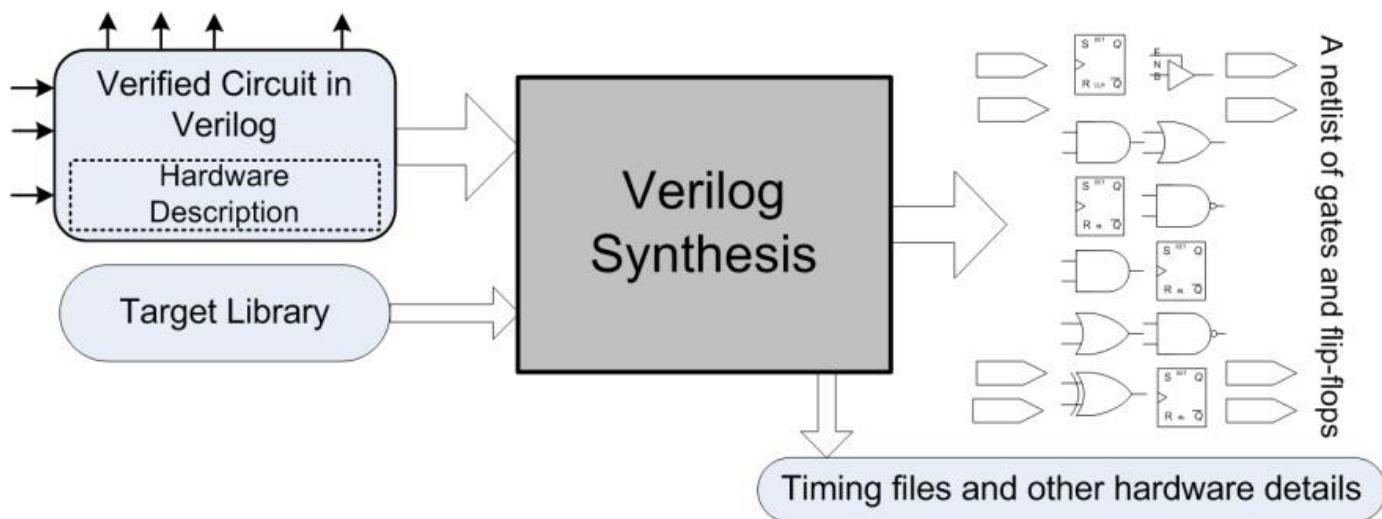

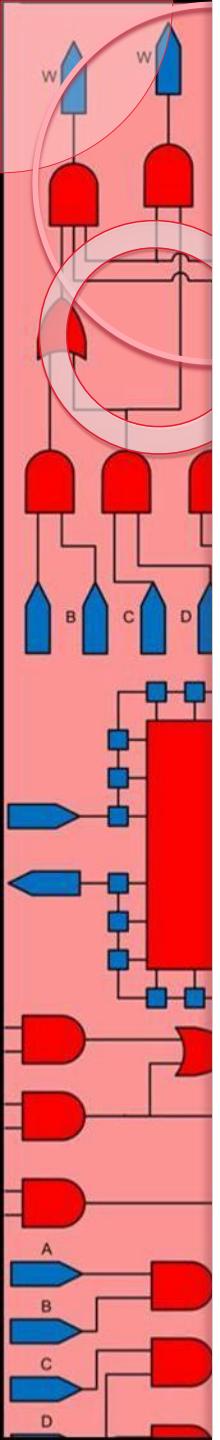


# Verilog as a Design Tool

- Modules


Design File: design1.v
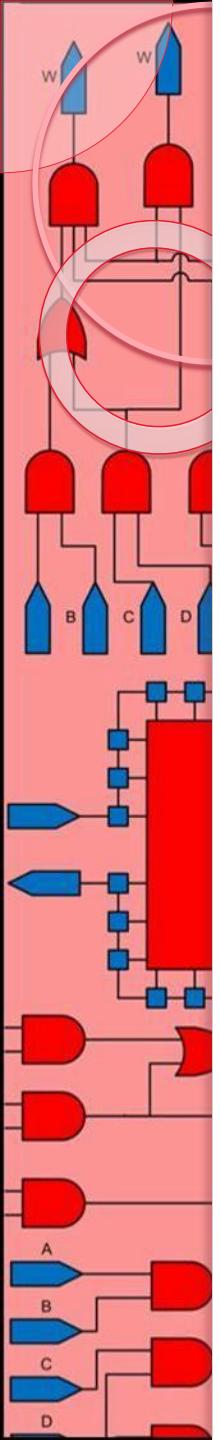
```
module design1
    .
    .
    .
endmodule
```



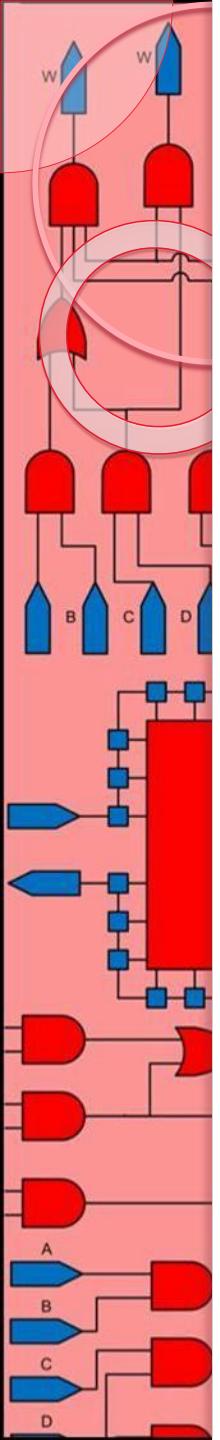
# Verilog as a Design Tool

- ModelSim simulation environment
  - Define a project
  - Enter your design
  - Generate a testbench providing inputs
  - Simulate your design
  - Observe waveforms and outputs
  - Verify the operation of the design
  - Finish simulation


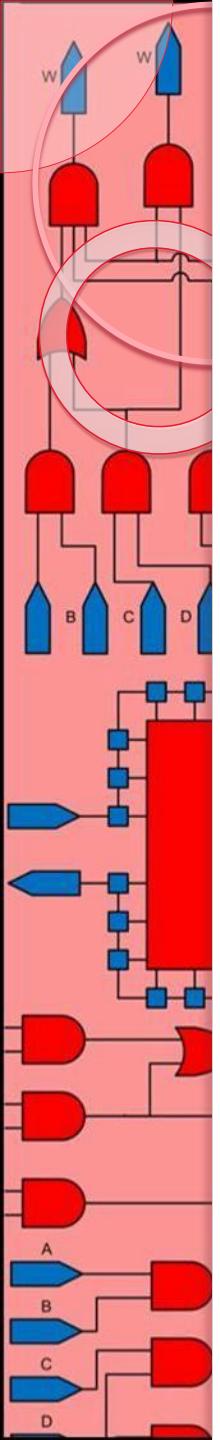
# Verilog as a Design Tool

- Summary
  - Covered terminologies
  - A simple simulation tool
  - Became familiar with running the software




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 2: Gate Level Description

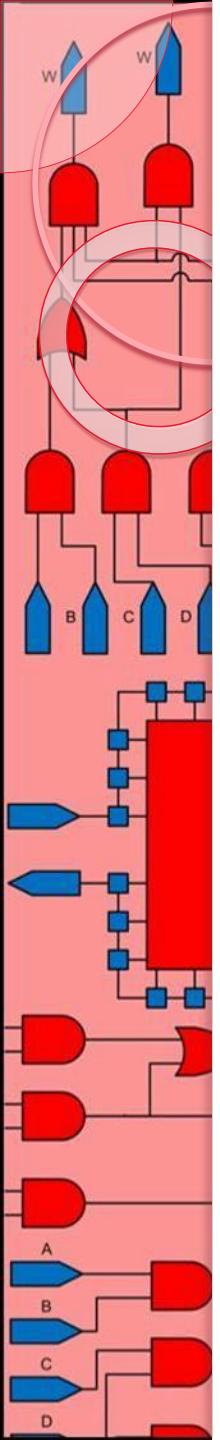

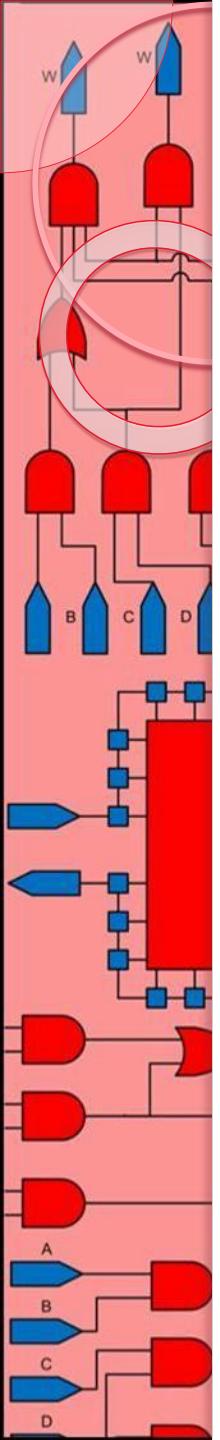
# Verilog for Gate Level Descriptions

- Basic Structures of Verilog
- Levels of Abstraction
- Combinational Gates
- Writing Testbenches
- Summary


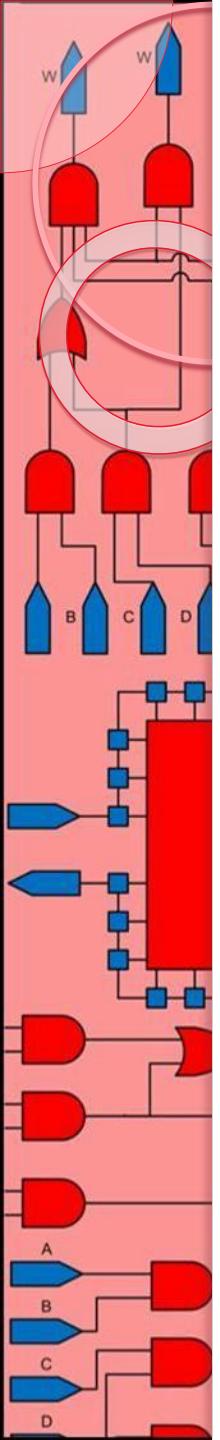
# Basic Structures of Verilog

- Modules
- Module Outline
- Module Ports
- Module Variables
- Wires



# Basic Structures of Verilog


- Modules


Design File: design1.v

```
module design1
    .
    .
    .
endmodule
```

# Basic Structures of Verilog

- **Modules**

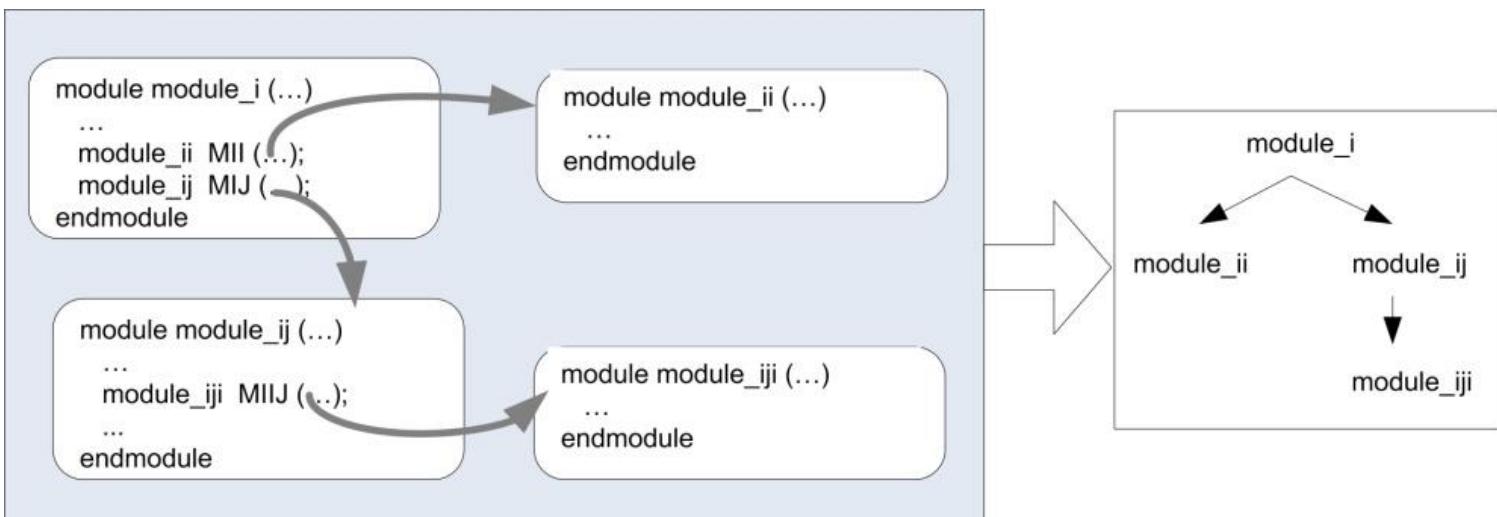


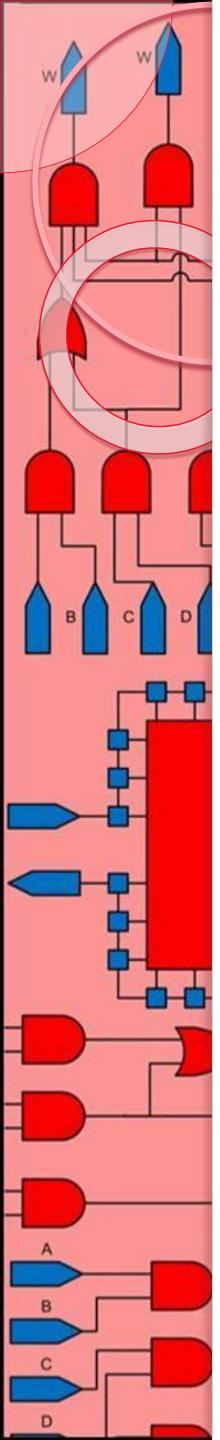
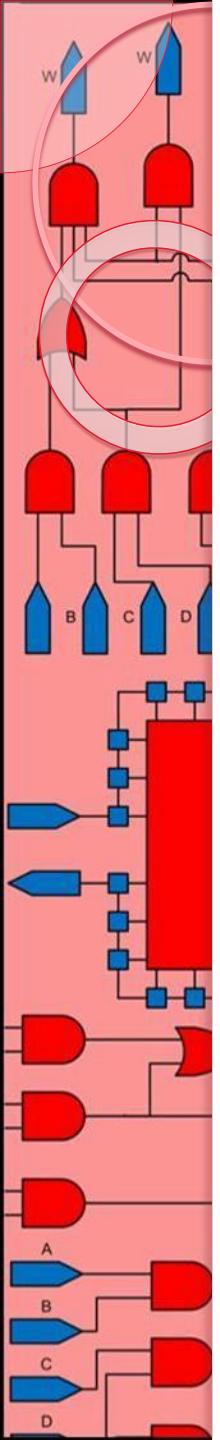
# Basic Structures of Verilog

- Module Outline


```
module name (ports or ports and their declarations);  
  port declarations if not in the header;  
  other declarations;  
  . . .  
  statements  
  . . .  
endmodule
```


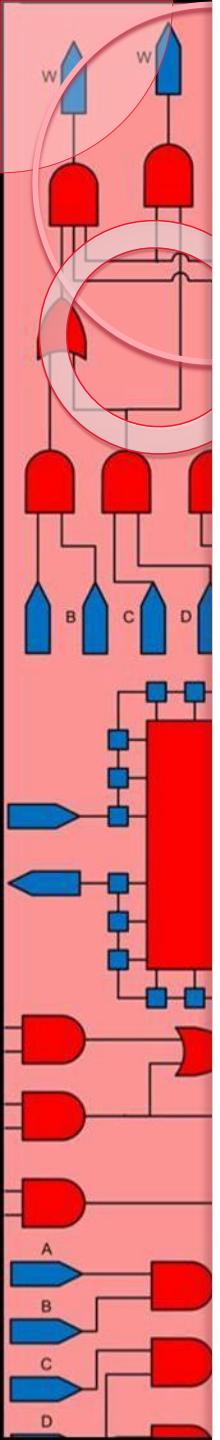
# Basic Structures of Verilog

- Module Ports

```
module acircuit (input a, b, output w);
    // a comment
    // wires and variable declarations
    // operation of the circuit
    .
    .
endmodule
```



# Basic Structures of Verilog

- Module Outline


```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```


```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @(i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

# Combinational Circuits

- Gate Level Combinational Circuits

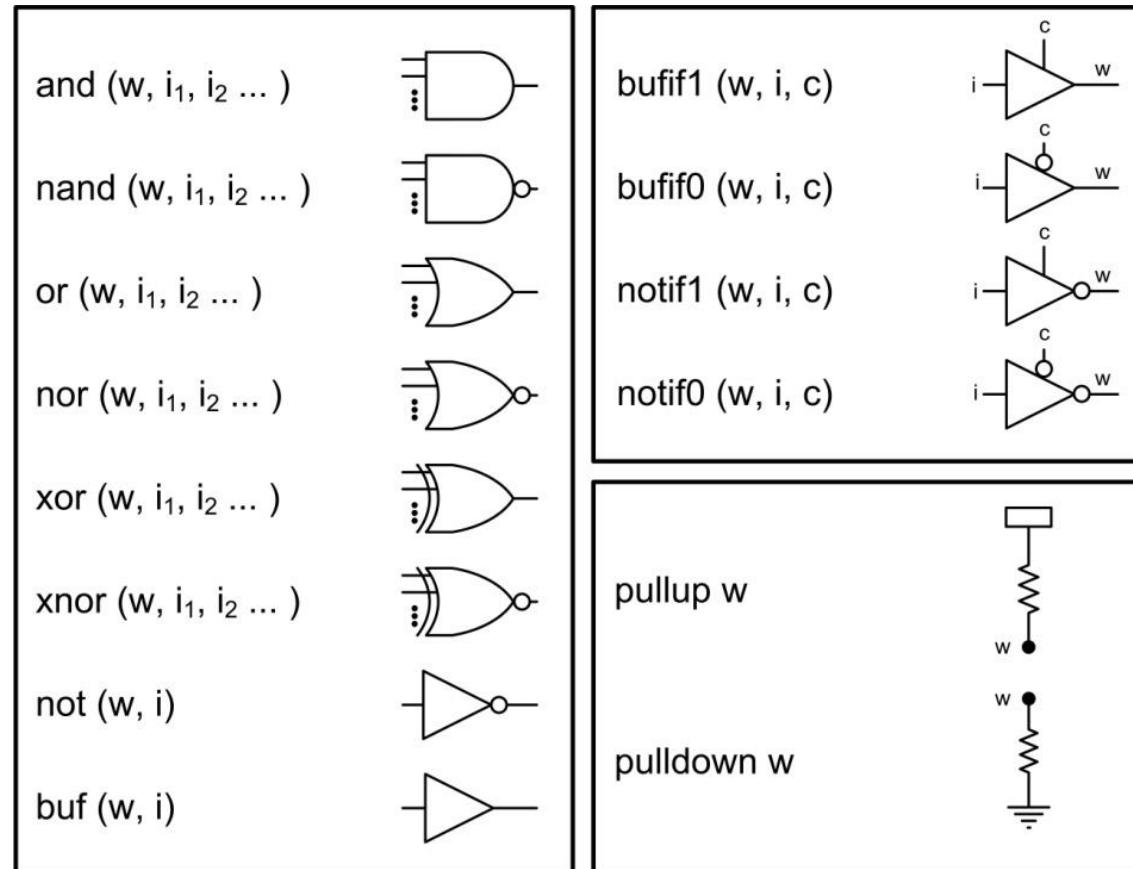

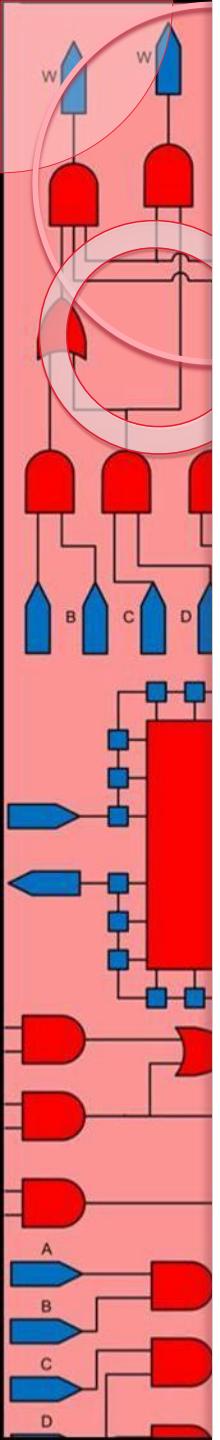


# Combinational Circuits

- Gate Level Combinational Circuits
  - Majority Example
  - Multiplexer Example

# Combinational Circuits

- Majority Example

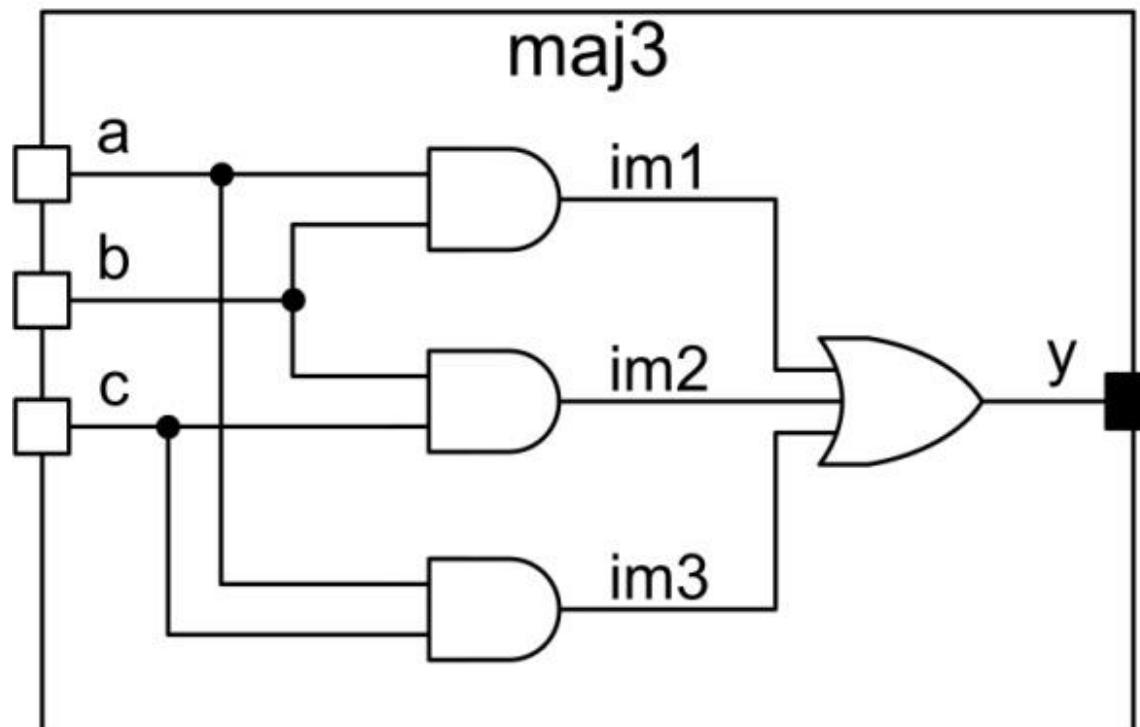

# Combinational Circuits

- Majority Example

```
`timescale 1ns/1ns


module maj3 ( input a, b, c, output y );


    wire im1, im2, im3;

    and U1 ( im1, a, b );
    and U2 ( im2, b, c );
    and U3 ( im3, c, a );
    or  U4 ( y, im1, im2, im3 );

endmodule
```

Verilog Code for the Majority Circuit

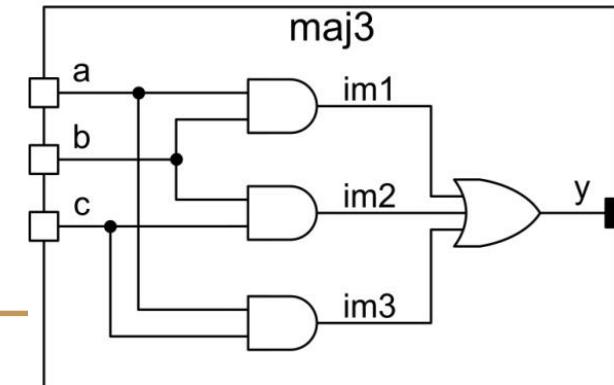

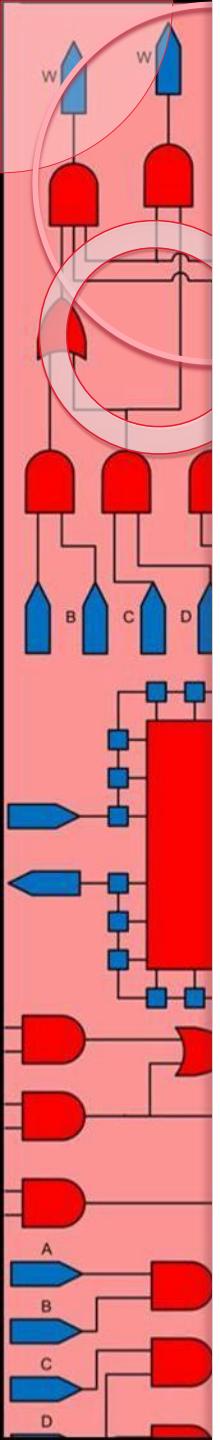

# Writing Testbenches

- Apply random data to test maj3

```
`timescale 1ns/1ns


module maj3Tester ();
    reg ai=0, bi=0, ci=0;
    wire yo;

    maj3 MUT ( ai, bi, ci, yo );

    initial begin
        #23; ai=0; bi=0; ci=1;
        #23; ai=1; bi=0; ci=1;
        #23; ai=0; bi=0; ci=0;
        #23; ai=1; bi=1; ci=1;
        #23; ai=0; bi=1; ci=0;
        #23; $stop;
    end
endmodule
```


# Simulation Results

- Simulating maj3

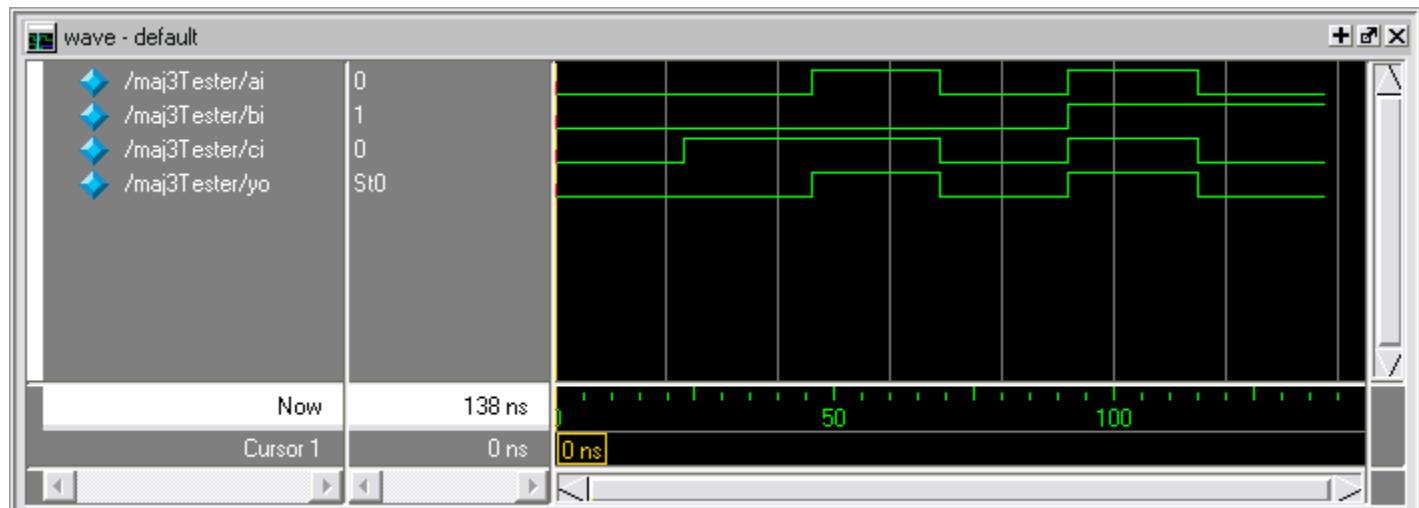

# Combinational Circuits

- Multiplexer Example

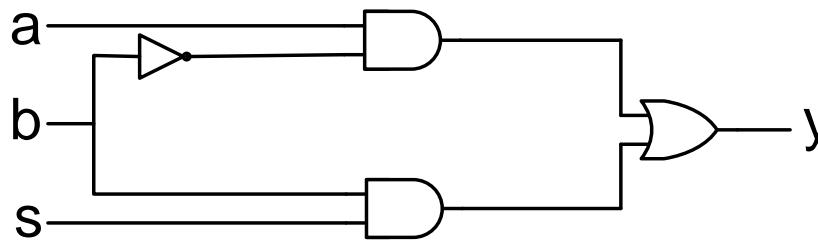


Multiplexer Schematic

```
'timescale 1ns/1ns

module mux_2to1 (a, b, s, y);
    input a, b, s;
    output y;
    wire is;
    wire aa, bb;

    not U1 (is, s);
    and U2 (aa, a, is),
        U3 (bb, b, s);
    or U4 (y, aa, bb);

endmodule
```

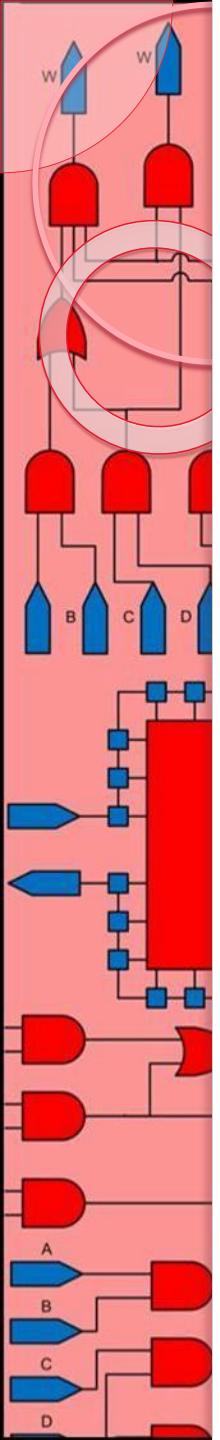

# Combinational Circuits


- Multiplexer Example

```
`timescale 1ns/1ns

module mux_2to1 (a, b, s, y);
    input a, b, s;
    output y;
    wire is;
    wire aa, bb;

    not U1 (is, s);
    and U2 (aa, a, is),
        U3 (bb, b, s);
    or U4 (y, aa, bb);

endmodule
```

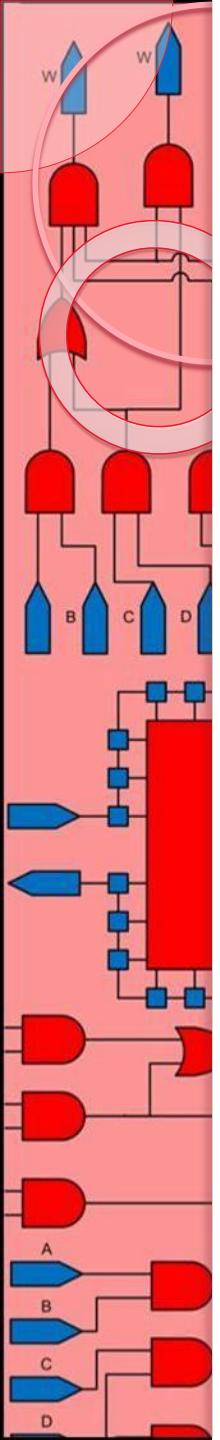

# Multiplexer Testbench


- Apply random test data to test mux

```
`timescale 1ns/1ns

module muxTester ();
    reg ai=0, bi=0, ci=0;
    wire yo;


    mux_2to1 MUT ( ai, bi, ci, yo );

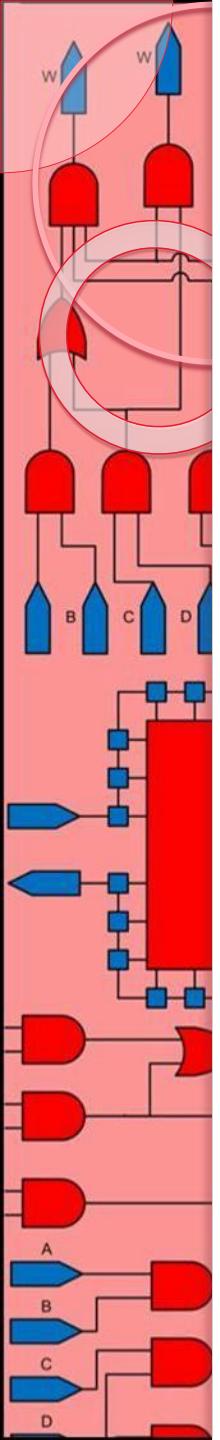    initial begin
        #23; ai=0; bi=0; ci=1;
        #23; ai=1; bi=0; ci=1;
        #23; ai=0; bi=0; ci=0;
        #23; ai=1; bi=1; ci=1;
        #23; ai=0; bi=1; ci=0;
        #23; $stop;
    end
endmodule
```


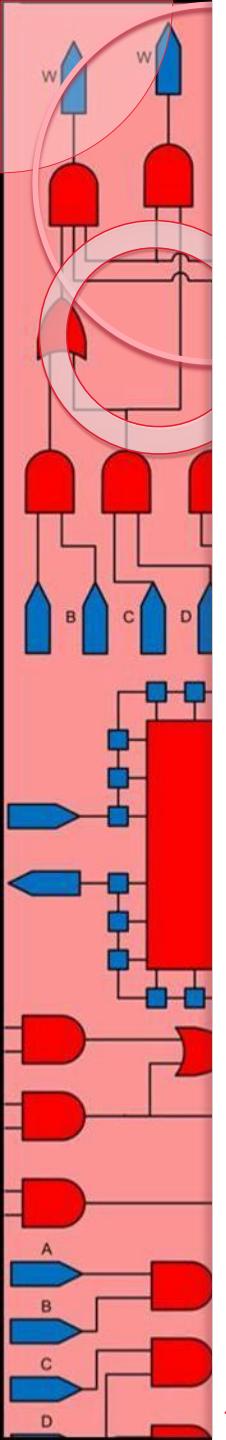
# Summary

- The focus of this lecture was on gate level in Verilog
- Some Basic Verilog concepts were presented
- We showed examples of levels of abstraction
- We used Verilog primitives
- Two examples were used, used somewhat different styles
- Simple testbenches were used
- ModelSim simulation run results were shown




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 3: Gate Delays

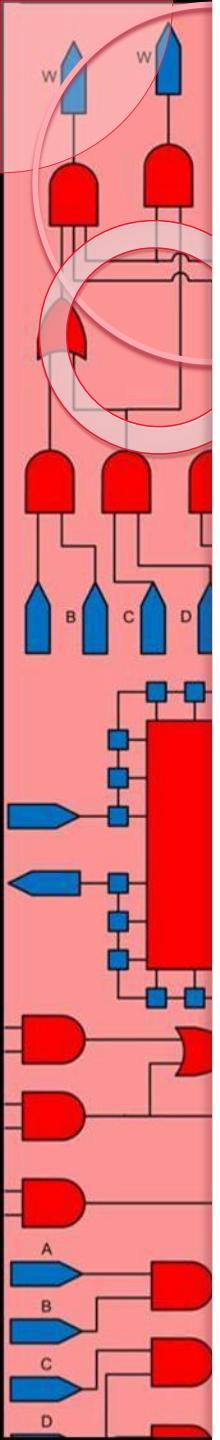
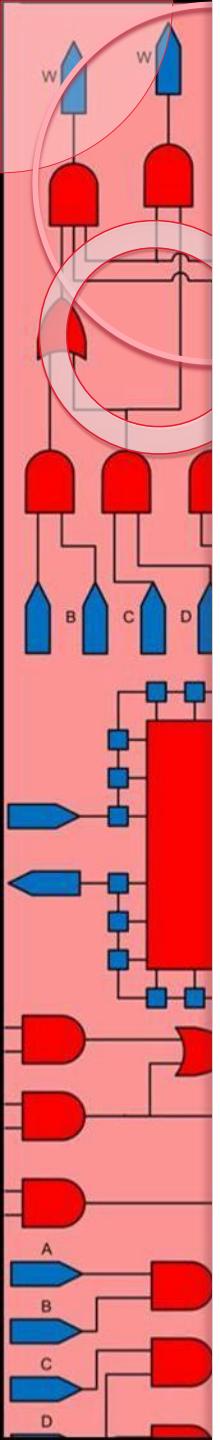
# Gate Delays

- Switch Level Primitives
- Logic Value System
- Transistor (Switch) Level Description
- Combinational Gates with Delay
- Three-state Logic
- Summary



# Gate Delays

- A module using transistors


Design File: design1.v

```
module design1
    .
    .
    .
endmodule
```
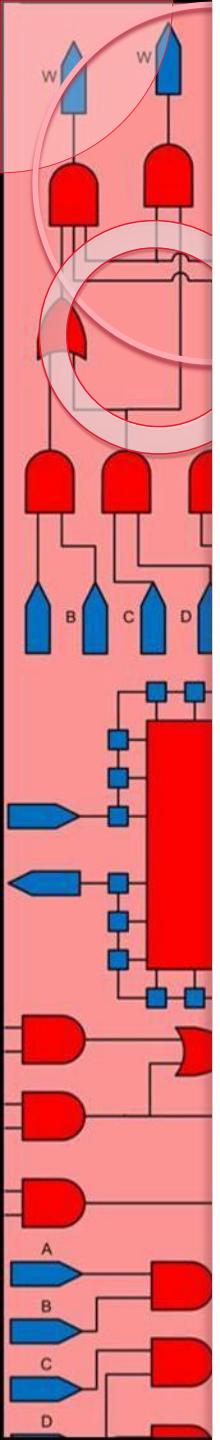
# Basic Structures of Verilog

- Module Ports

```
module acircuit (input a, b, output w);
    // a comment
    // wires and variable declarations
    // operation of the circuit using transistors
    . .
endmodule
```



# Basic Structures of Verilog

- Module Outline


```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```


```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @(i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

# Switch Level Primitives

- Switches and three-state gates

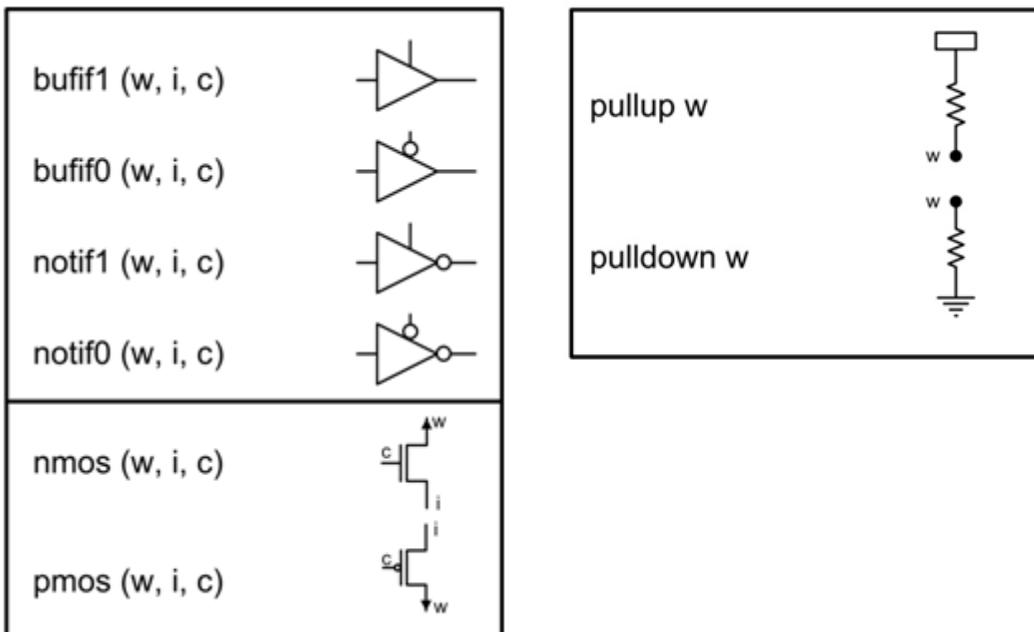

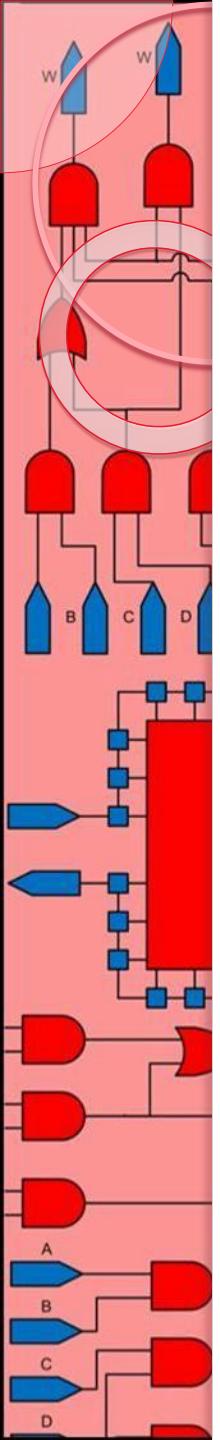


# Switch Level Primitives

- Logic Value System

- 0: forced low
- 1: forced high
- Z: open
- X: unknown

# Transistor (Switch) Level Description

- CMOS NAND Example

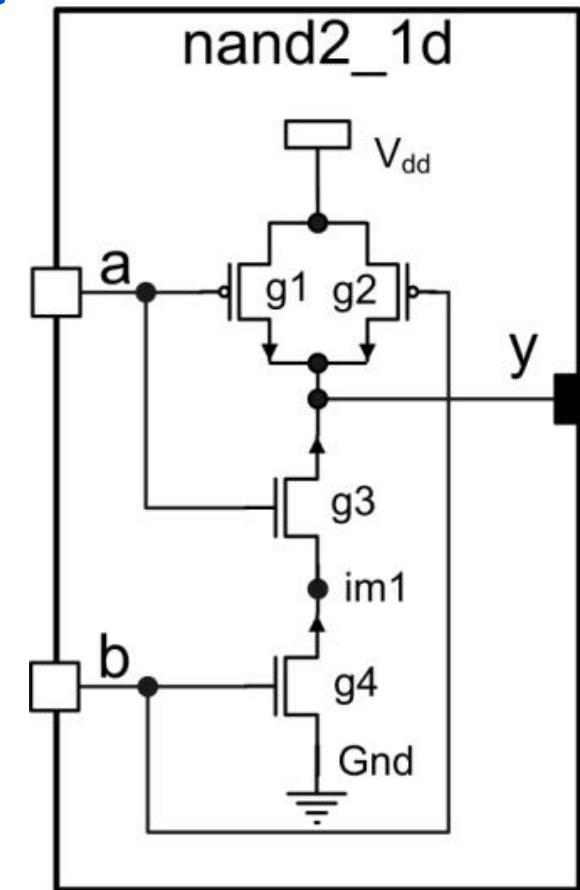

CMOS NAND at the Switch Level


# Transistor (Switch) Level Description

- CMOS NAND Example


```
`timescale 1ns/1ns

module nand2_1d ( input a, b, output y);
wire im1;
supply1 vdd;
supply0 gnd;
nmos #(3, 4)
    g4 (im1, gnd, b),
    g3 (y, im1, a);

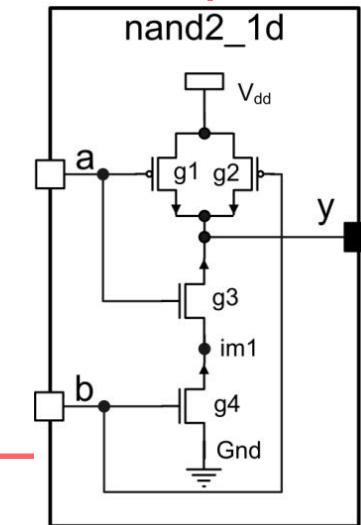pmos #(4, 5)
    g1 (y, vdd, a),
    g2 (y, vdd, b);
endmodule
```



CMOS NAND Verilog Description

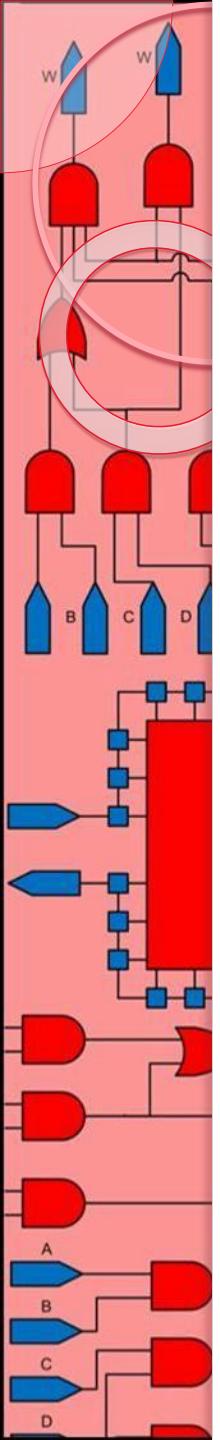

# Transistor (Switch) Level Description

- CMOS NAND Example

```
`timescale 1ns/1ns

module nand2Tester ();
    reg ai=0, bi=0;
    wire yo;

    nand2_1d MUT ( ai, bi, yo );

    initial begin
        #25; ai=0; #25; bi=0;
        #25; ai=0; #25; bi=1;
        #25; ai=1; #25; bi=0;
        #25; ai=1; #25; bi=1;
        #25; ai=0; #25; bi=1;
        #25; $stop;
    end
endmodule
```

```
`timescale 1ns/1ns


module nand2_1d ( input a, b, output y);
    wire im1;
    supply1 vdd;
    supply0 gnd;
    nmos #(3, 4)
        g4 (im1, gnd, b),
        g3 (y, im1, a);

    pmos #(4, 5)
        g1 (y, vdd, a),
        g2 (y, vdd, b);
endmodule
```

CMOS NAND Verilog Description

# Transistor (Switch) Level Description

- CMOS NAND Example

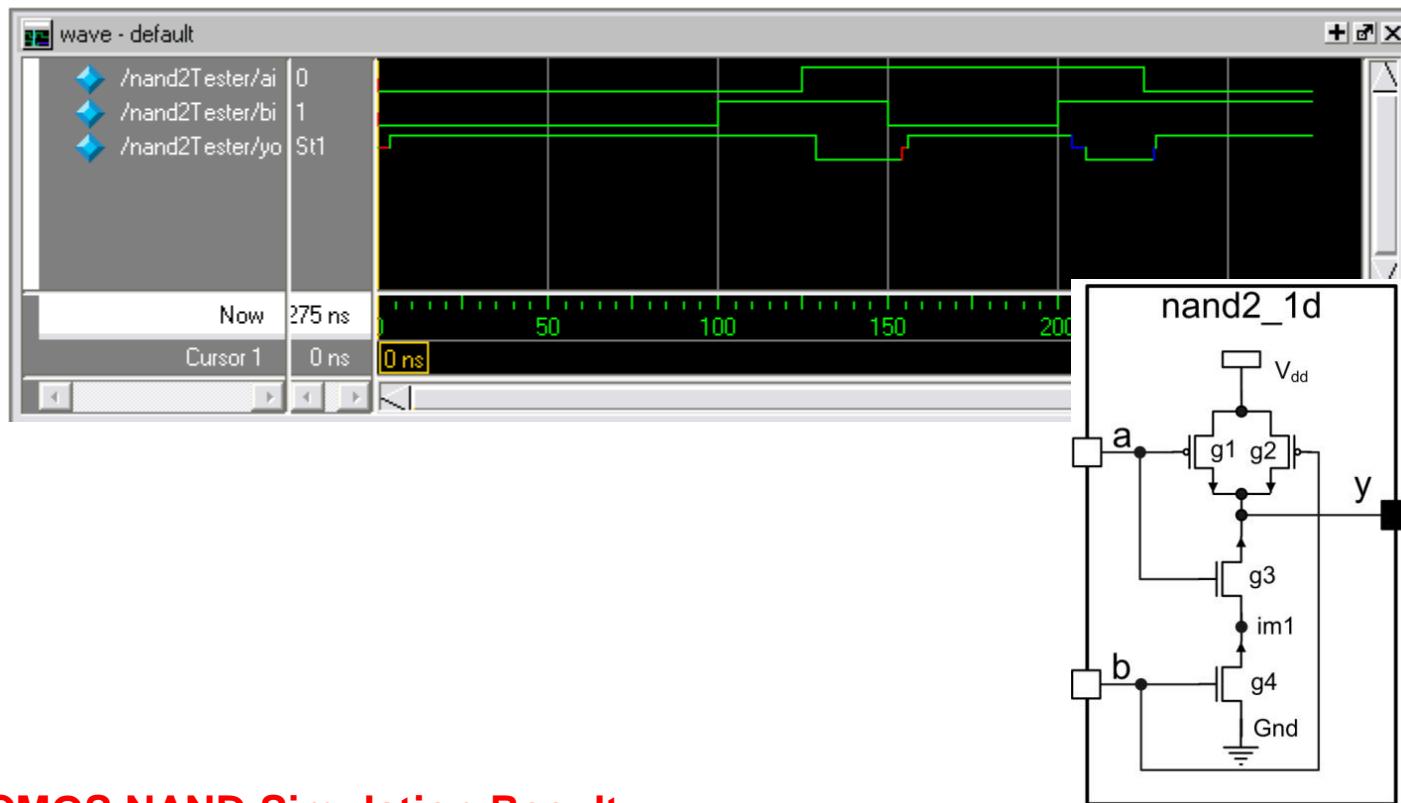



CMOS NAND Simulation Result

# Transistor (Switch) Level Description

- Timing analysis


CMOS NAND nmos #(3,4); pmos #(4,5)

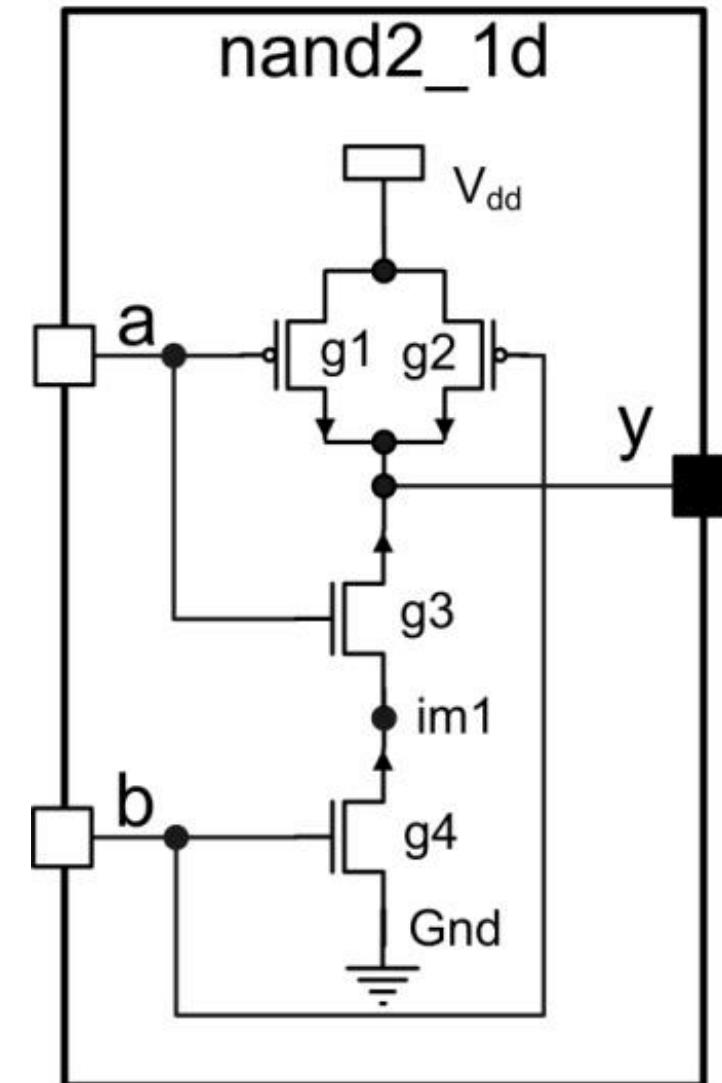

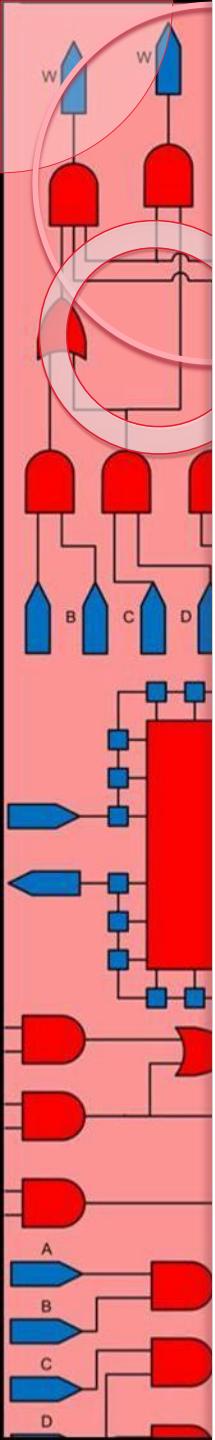

# Transistor (Switch) Level Description


- Timing analysis, gate equivalent

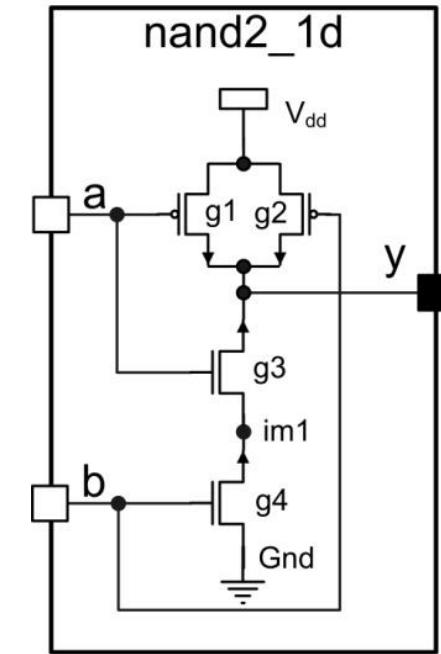

CMOS NAND nmos #(3,4); pmos #(4,5)

# Three-state Logic

- Multiplexer Example

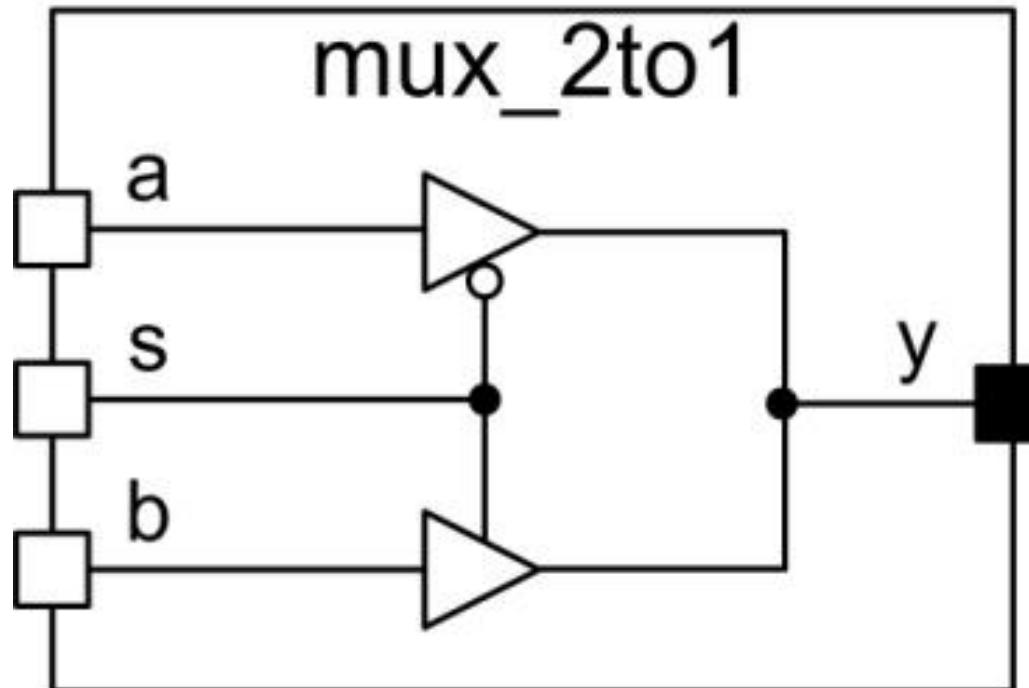

# Combinational Circuits

- Multiplexer Example – use three-state gates


```
`timescale 1ns/1ns


module mux_2to1 ( input a, b, s, output y );

bufif1 #(3) ( y, b, s );
bufif0 #(5) ( y, a, s );

endmodule
```

Multiplexer Verilog Code

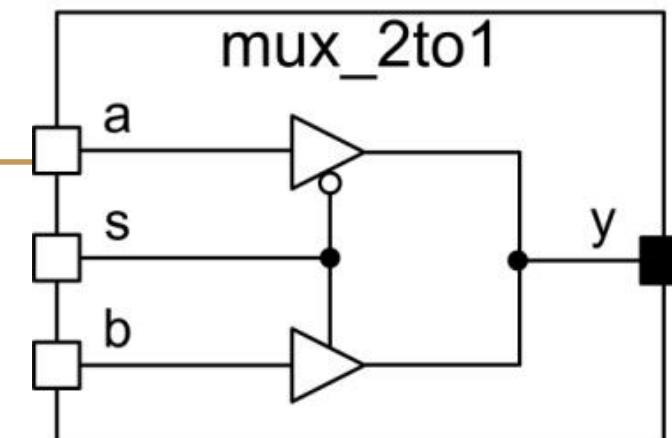

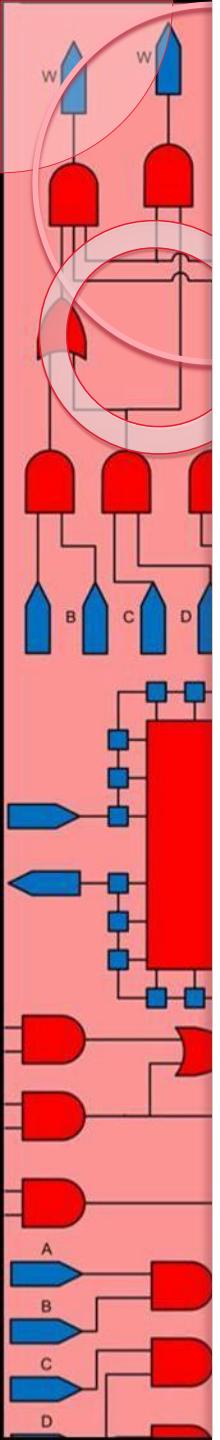

# Combinational Circuits

- Multiplexer Example

```
`timescale 1ns/1ns

module mux_2to1 (a, b, s, y);
    input a, b, s;
    output y;
    wire is;
    wire aa, bb;

    not U1 #(3,4) (is, s);
    and U2 #(3,4) (aa, a, is),
                  U3 #(3,4) (bb, b, is);
    or U4 #(3,4) (y, aa, bb);

endmodule
```

# Multiplexer Testbench

- Random data at some time intervals

```
`timescale 1ns/1ns


module muxTester ();
    reg ai=0, bi=0, ci=0;
    wire yo;


    mux_2to1 MUT ( ai, bi, ci, yo );

    initial begin
        #23; ai=0; bi=0; ci=1;
        #23; ai=1; bi=0; ci=1;
        #23; ai=0; bi=0; ci=0;
        #23; ai=1; bi=1; ci=1;
        #23; ai=0; bi=1; ci=0;
        #23; $stop;
    end
endmodule
```

# Multiplexer Testbench


- Multiplexer output waveform

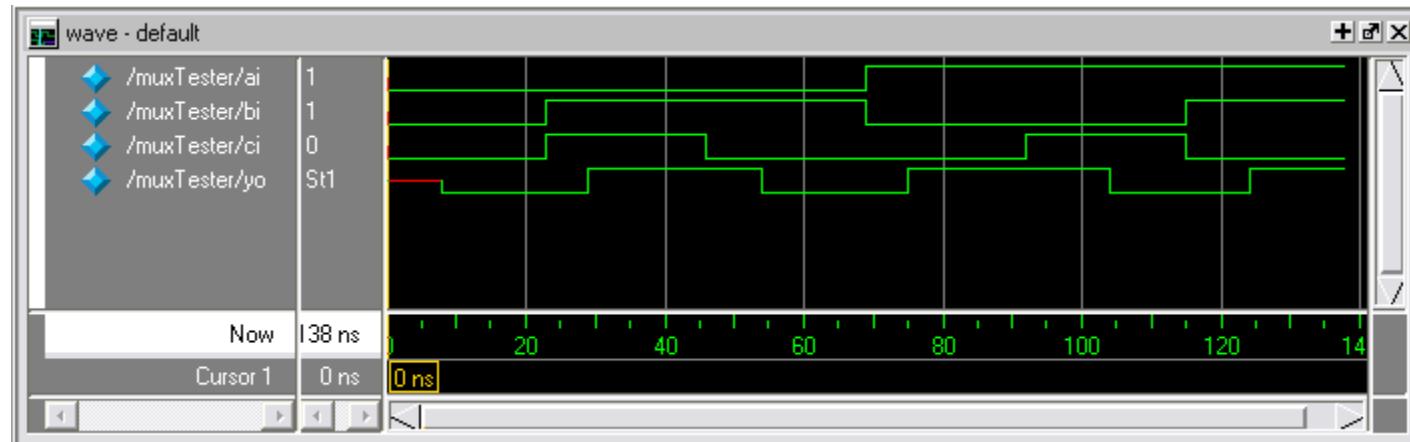

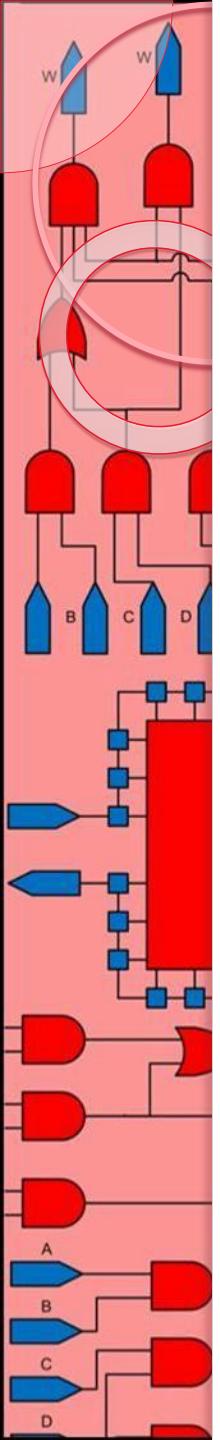
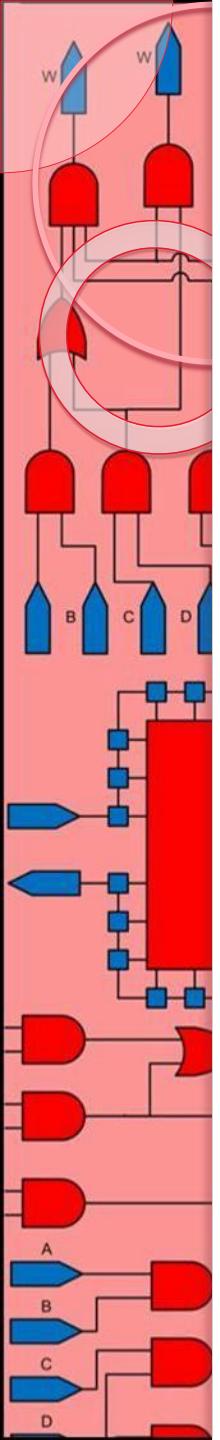
# Summary

- Discussed the origin of delays
- Showed 4-value logic value system
- Performed switch level simulation
- Simulated gates with delay values
- ModelSim simulation run results were shown




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog
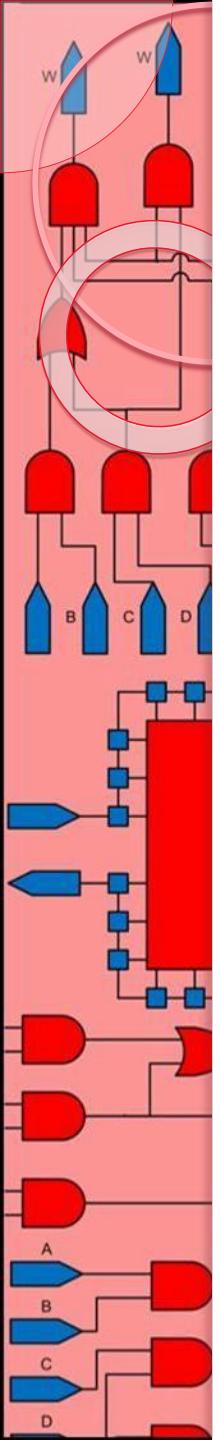
## Lecture 4: Hierarchical Gate Level Design





# Hierarchical Gate Level Design

- Gate Level Design
- Module Instantiation
- Top Level Module
- More on Testbenches
- Summary

# Hierarchical Gate Level Design

- Module Hierarchy

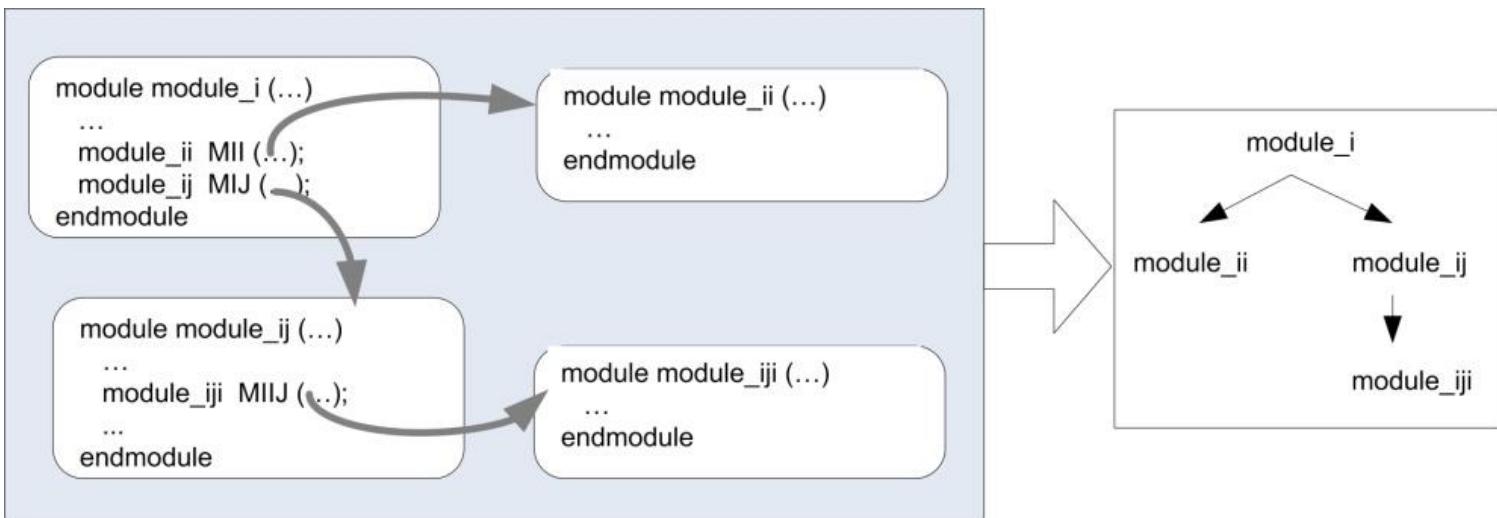

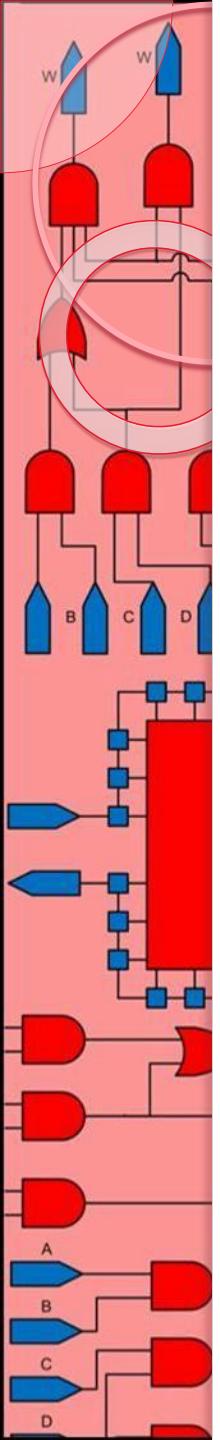


# Hierarchical Gate Level Design

- Module Outline

```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```

```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @(i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

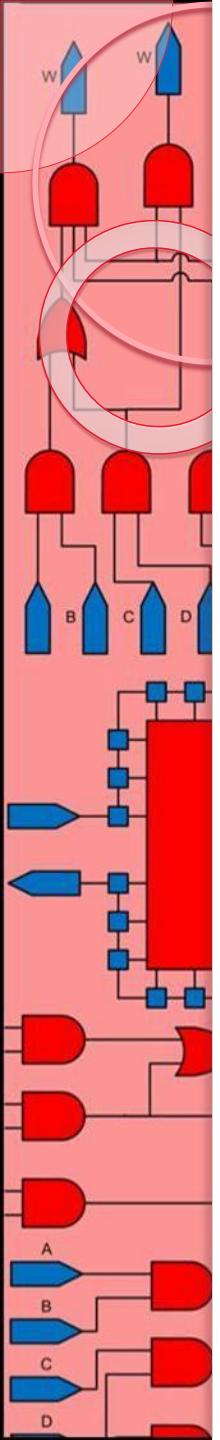


# Hierarchical Gate Level Design

- Module Instantiation

```
module a_hierarchical_circuit (input a, b, output w);
    // a comment
    // wires and variable declarations
    // operation of the circuit

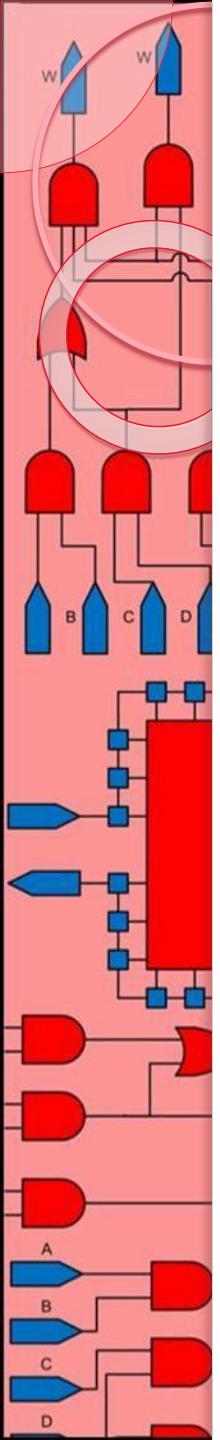    AnotherTestedModule UUT (port connection according to module being instantiated);
    // any number of the above
    .
    .
endmodule
```



# Basic Structures of Verilog

- Module Instantiation
  - Top level design instantiates Majority and Mux

# Combinational Circuits

- Majority Example

```
`timescale 1ns/1ns


module maj3 ( input a, b, c, output y );


    wire im1, im2, im3;

    and U1 #(4,5) ( im1, a, b );
    and U2 #(4,5) ( im2, b, c );
    and U3 #(4,5) ( im3, c, a );
    or  U4 #(4,5) ( y, im1, im2, im3 );

endmodule
```

Verilog Code for the Majority Circuit

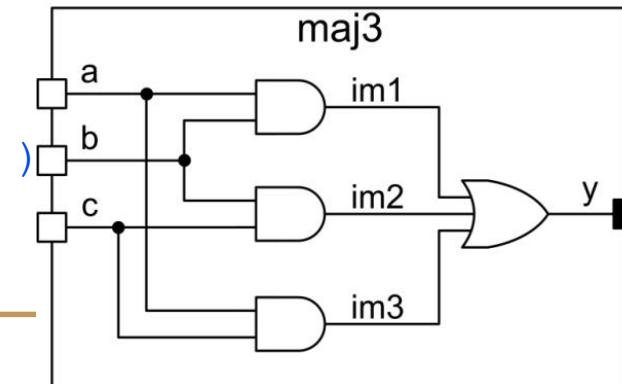

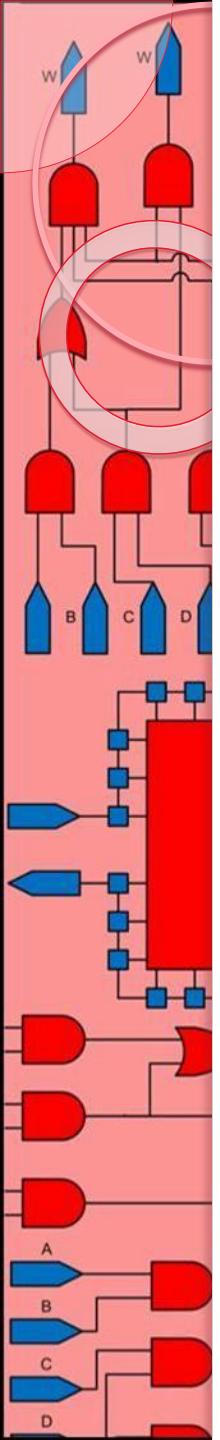

# Combinational Circuits

- Where delays come from

```
`timescale 1ns/1ns
module some_circuit ( input a, b, c, output y );
    . .
    nand2_1d U1 #(6,8) ( im1, a, b );
    . .
endmodule
```

```
`timescale 1ns/1ns

module nand2_1d ( input a, b, output y );
    wire im1;
    supply1 vdd;
    supply0 gnd;
    nmos #(3, 4)
        g4 (im1, gnd, b),
        g3 (y, im1, a);

    pmos #(4, 5)
        g1 (y, vdd, a),
        g2 (y, vdd, b);
endmodule
```

# Combinational Circuits

- Multiplexer Example – use three-state gates


```
`timescale 1ns/1ns

module mux_2to1 ( input a, b, s, output y );

bufif1 #(3) ( y, b, s );
bufif0 #(5) ( y, a, s );

endmodule
```

Multiplexer Verilog Code

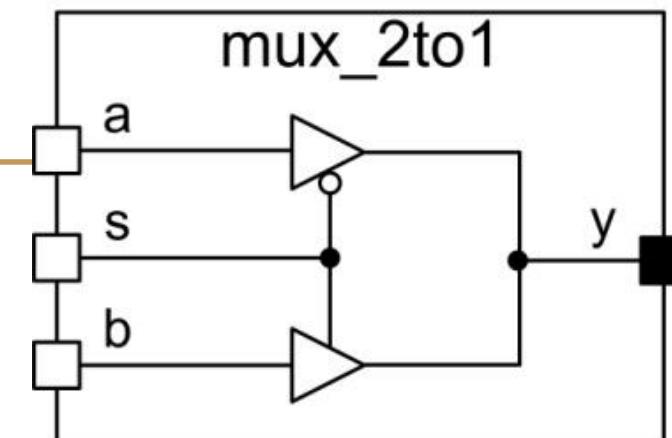

# Hierarchical Gate Level Design

- Multiplexer Example

```
`timescale 1ns/1ns

module RateSelector (input a, b, c, d, e, output w);


    wire mj;

    maj3 U1 (c, d, e, mj);

    mux_2to1 U2 (a, b, mj, w);

endmodule
```

**Top level module**

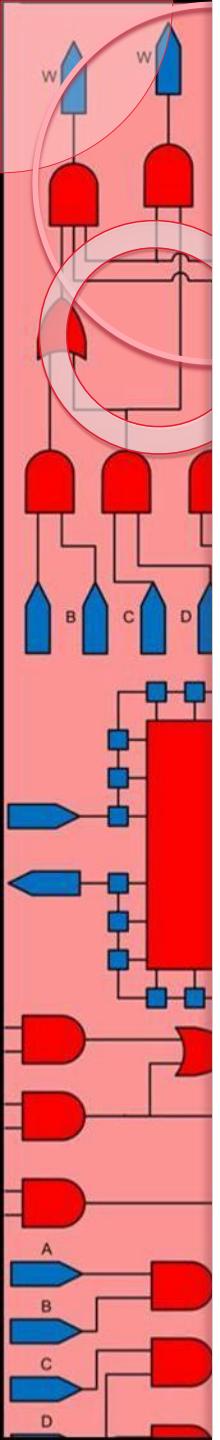

# Hierarchical Gate Level Design

- Multiplexer Example

```
`timescale 1ns/1ns

module RateSelector (input a, b, c, d, e, output w);


    wire mj;

    maj3 U1 (c, d, e, mj);

    mux_2to1 U2 (a, b, mj, w);

endmodule
```

Top level module

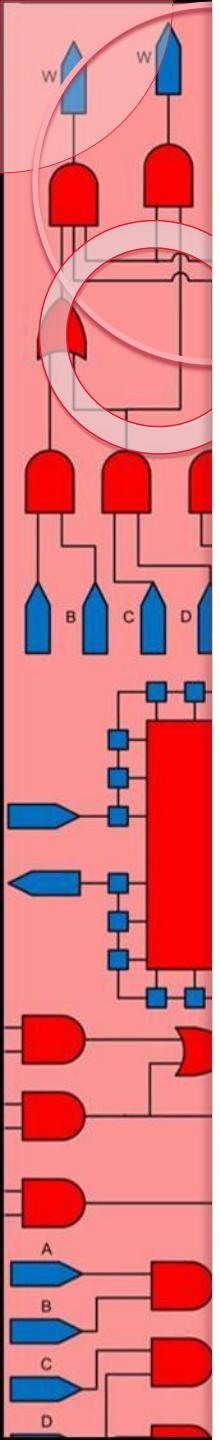

# Hierarchical Gate Level Design

- Periodic data application

```
`timescale 1ns/1ns


module RateSelectoreTester ();
    reg ai=0, bi=0, ci=0, di=0, ei=0;
    wire yo;


    RateSelector MUT ( ai, bi, ci, di, ei, yo );

    always #17 ai = ~ai;
    always #33 bi = ~bi;
    initial begin
        #97; ci=0; di=0; ei=1;
        #97; ci=1; di=0; ei=1;
        #97; ci=0; di=0; ei=0;
        #97; ci=1; di=1; ei=1;
        #97; ci=0; di=1; ei=0;
        #97; $stop;
    end
endmodule
```

# Hierarchical Gate Level Design


- Selecting one of the two frequencies

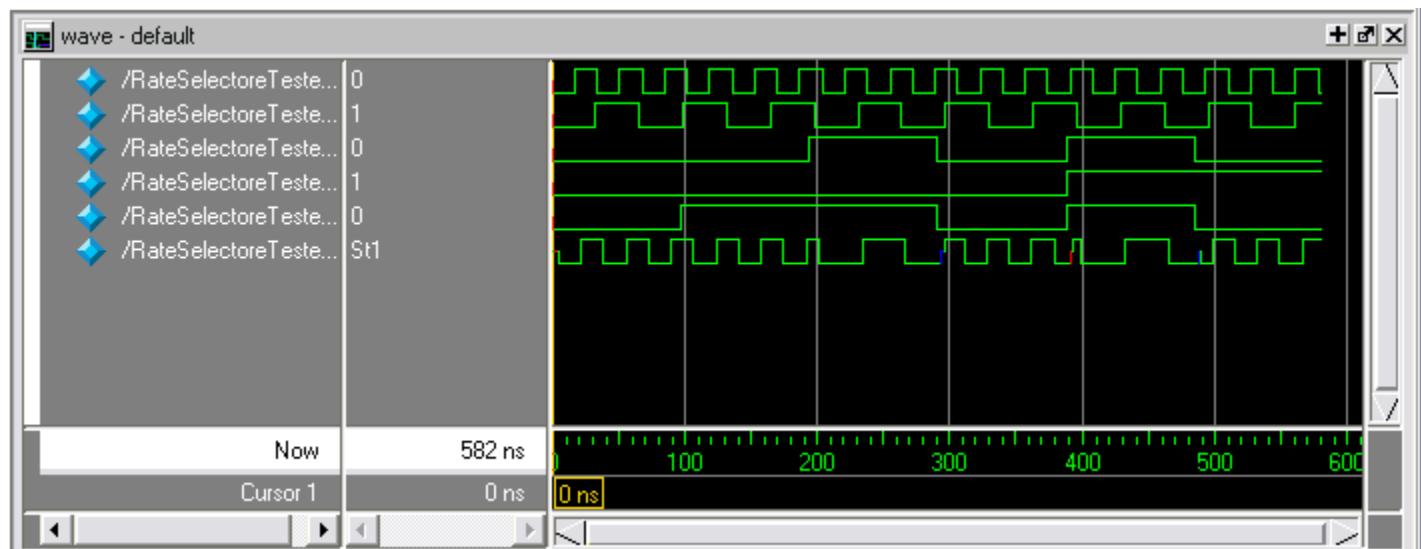

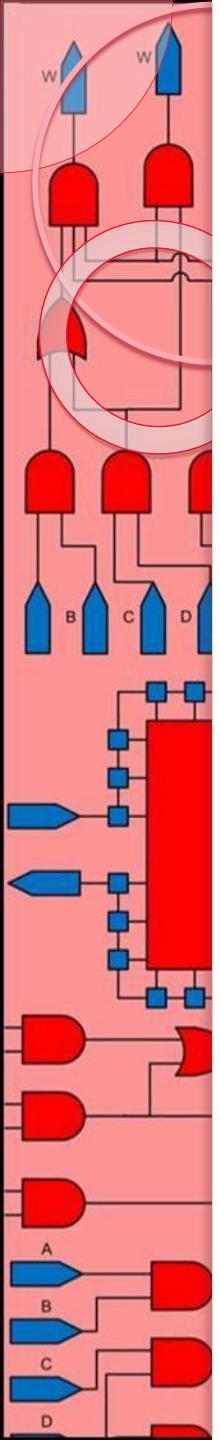
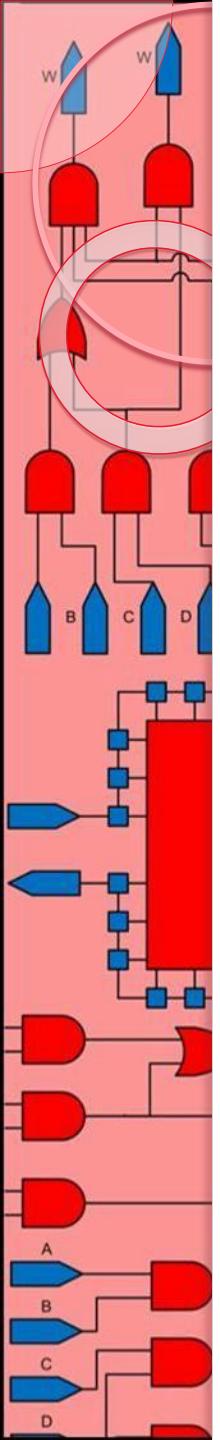
# Summary

- Talked about module hierarchy
- Any design can have a hierarchy and instantiation of other modules
- The design remains at the gate level
- Talked about more constructs to use in a testbench




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog
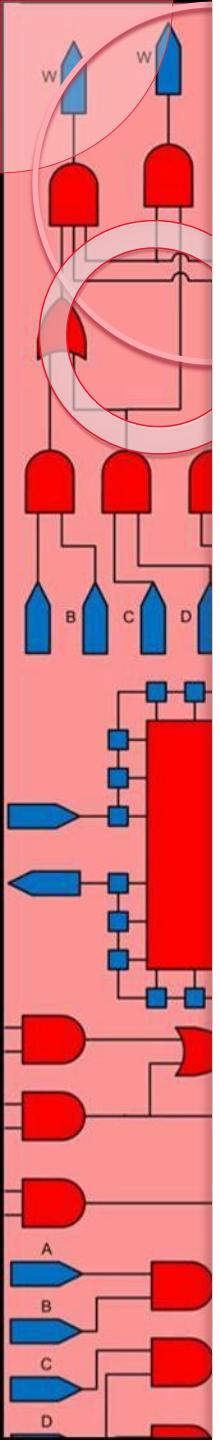
## Lecture 5: Using Expressions in Modules




# Using Expressions in Modules

- Boolean expressions
- Two familiar examples
- Module Instantiation
- Top Level Module
- More on Testbenches
- Summary


# Boolean Expressions

- Use Verilog **assign** statement
- **assign** statements in a module are considered as logic blocks
- Position in module code is irrelevant
- Use the following notations:
  - For AND use:      &
  - For OR use:      |
  - For NOT use:      ~
  - For XOR use:      ^
  - Use parenthesis for enforcing precedence

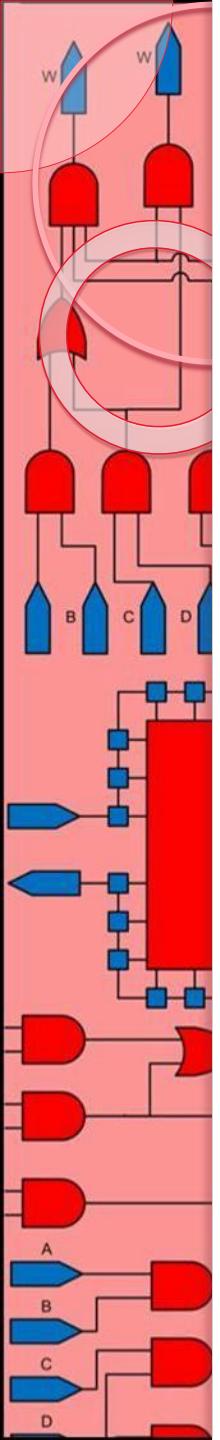
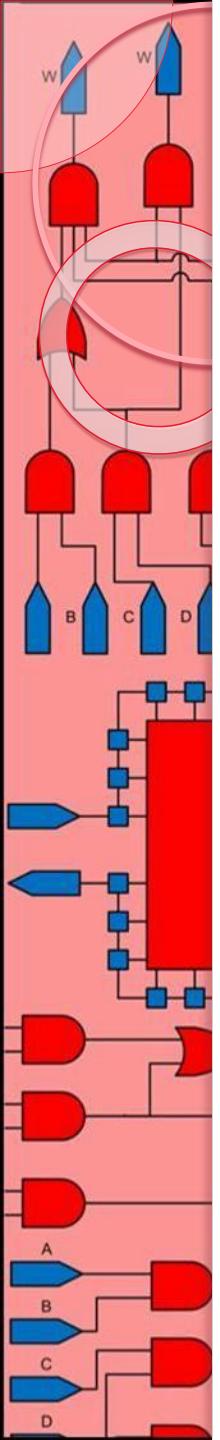
# Boolean Expressions

- Use Verilog **assign** statement
- Format:  
`assign #(0 to l_Delay, lto0_Delay) w = a & b & c;`  
`assign #(Delay) w = a & b & c;`  
`assign #Delay w = a & b & c;`  
`assign w = a & b & c;`
- Optional delay parameters
- Output is **w**
- Inputs are **a, b, c**



# Boolean Expressions

- Module Outline

```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```

```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @ (i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

# Boolean Expressions

- From KM
  - A circuit that produces a 1 if  $abcd$  is divisible by 3 or 4
  - Input is  $abcd$  and treated as a 4-bit binary number
  - Assume non-zero input

c,d \ a,b	00	01	11	10
00	-	1	1	1
01				1
11	1		1	
10		1		

$$w = c'.d' + a.b'.c' + a'.b'.c.d + a'.b.d' + a.b.c.d$$

$$w = (\sim c \ \& \ \sim d) \mid (a \ \& \ \sim b \ \& \ \sim c) \mid (\sim a \ \& \ \sim b \ \& \ c \ \& \ d) \mid (\sim a \ \& \ b \ \& \ \sim d) \mid (a \ \& \ b \ \& \ c \ \& \ d);$$

# Boolean Expressions

$$w = c'd' + a'b'c' + a'b'cd + a'b'd' + a'bc'd$$

$$w = (\neg c \wedge \neg d) \mid (a \wedge \neg b \wedge \neg c) \mid (\neg a \wedge \neg b \wedge c \wedge d) \mid (\neg a \wedge b \wedge \neg d) \mid (a \wedge b \wedge c \wedge d);$$

```
module div3or4 (input a, b, c, d, output w);

    assign w = (\neg c & \neg d) \mid
                (a & \neg b & \neg c) \mid
                (\neg a & \neg b & c & d) \mid
                (\neg a & b & \neg d) \mid
                (a & b & c & d);

endmodule
```

# Boolean Expressions

- From KM
  - A circuit that produces a 1 if  $abcd$  is divisible by 3 or 5
  - Input is  $abcd$  and treated as a 4-bit binary number
  - It turns out that output is 1 if even number of 1's are in  $abcd$

c,d \ a,b	00	01	11	10
00	1		1	
01		1		1
11	1		1	
10		1		1

$$w = a' \oplus b \oplus c \oplus d$$

$$w = \sim a \wedge b \wedge c \wedge d$$

# Boolean Expressions

- Module Description


$$w = c'.d' + a.b'.c' + a'.b'.c.d + a'.b.d' + a.b.c.d$$

$$w = (\sim c \& \sim d) | (a \& \sim b \& \sim c) | (\sim a \& \sim b \& c \& d) | (\sim a \& b \& \sim d) | (a \& b \& c \& d);$$

```
module div3or5 (input a, b, c, d, output w);


  assign #(68,70) w = ~a ^ b ^ c ^ d;

endmodule
```

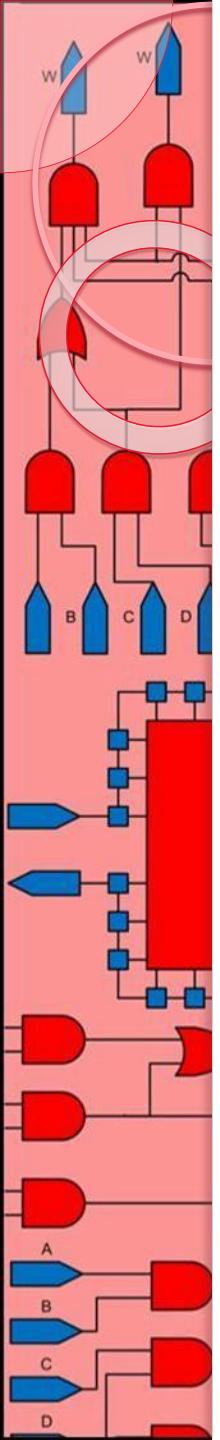


# Boolean Expressions

- Where delays come from?

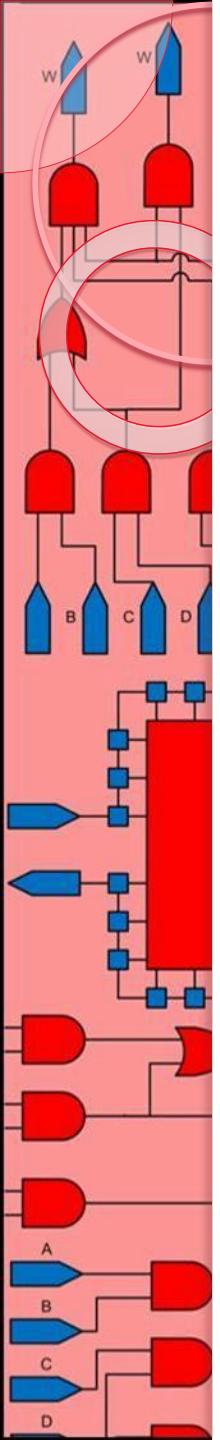
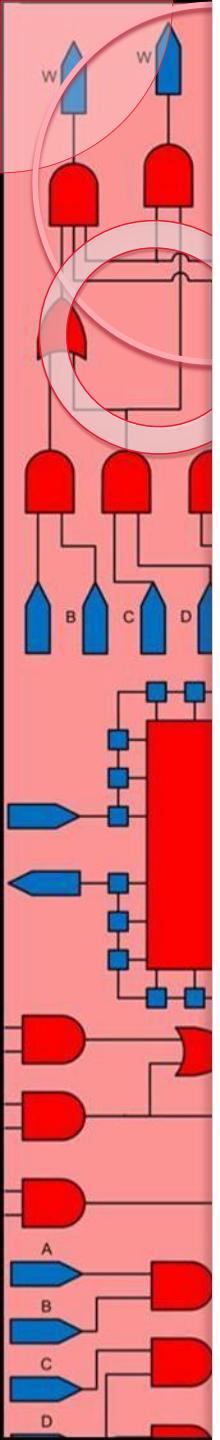
## Two Familiar Examples

- Module Instantiation
  - Top level design instantiates Majority and Mux



# Two Familiar Examples

- Majority Example


```
`timescale 1ns/1ns

module maj3 ( input a, b, c, output y );

    assign y = (a & b) | (a & c) | (b & c);

endmodule
```

Verilog Code for the Majority Circuit

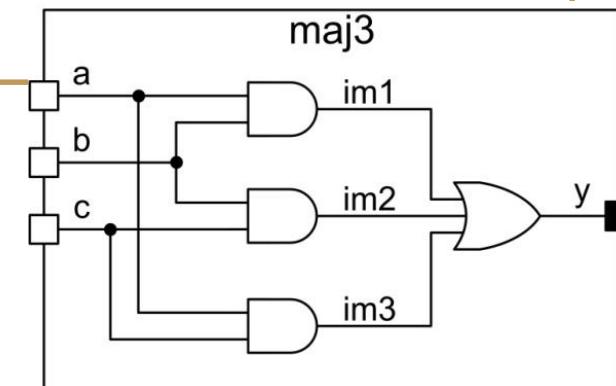


# Two Familiar Examples

- Multiplexer Example – Use AND OR gates

```
`timescale 1ns/1ns

module mux_2to1 ( input a, b, s, output y );
    assign #(5) y = (a & ~s) | (b & s);
endmodule
```

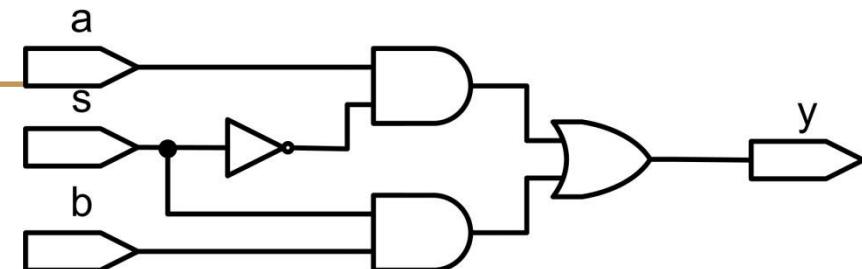

Verilog Code for the Multiplexer


# Two Familiar Examples


- Multiplexer Example – Use three-state gates

```
`timescale 1ns/1ns

module mux_2to1 ( input a, b, s, output y );
    assign #(5) y = ~s ? a : b;
endmodule
```

Multiplexer Verilog Code

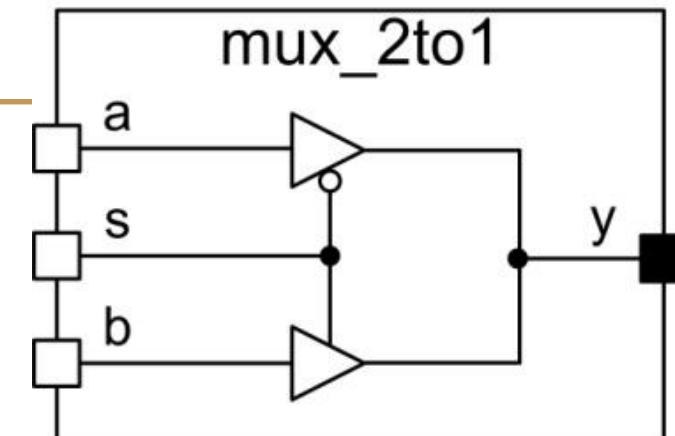

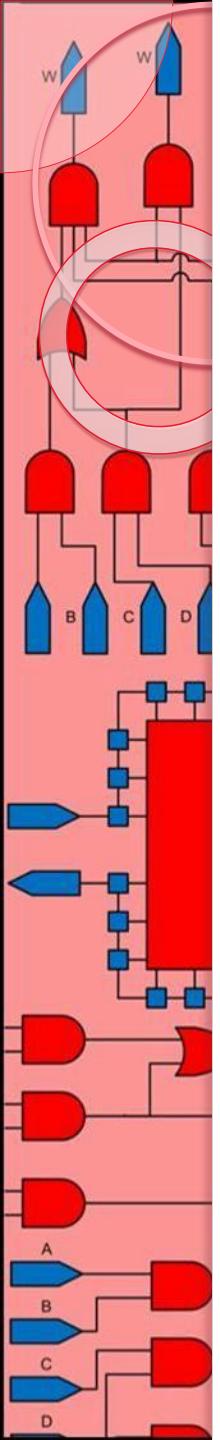

# Hierarchical Expression Level Design

- Rate Selector Example

```
`timescale 1ns/1ns

module RateSelector (input a, b, c, d, e, output w);


    wire mj;

    maj3 U1 (c, d, e, mj);

    mux_2to1 U2 (a, b, mj, w);

endmodule
```

**Top level module**

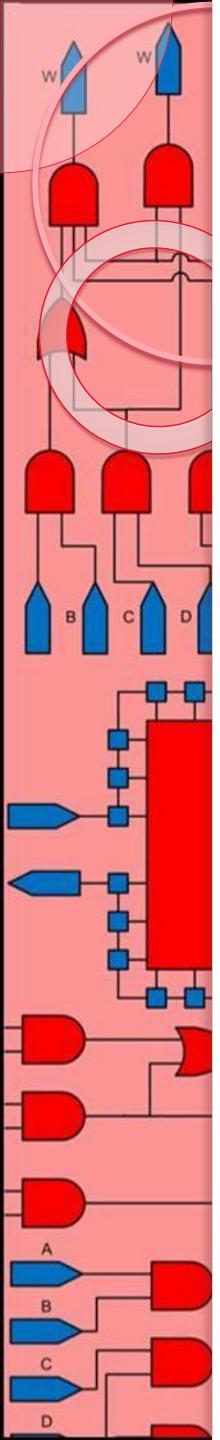

# Multiple Expressions

- Rate Selector Example

```
`timescale 1ns/1ns

module RateSelector (input a, b, c, d, e, output w);


    wire mj;

    assign mj = (c & d) | (c & e) | (d & e);

    assign #(5) w = (a & ~mj) | (b & mj);

endmodule
```

## Module with two expressions

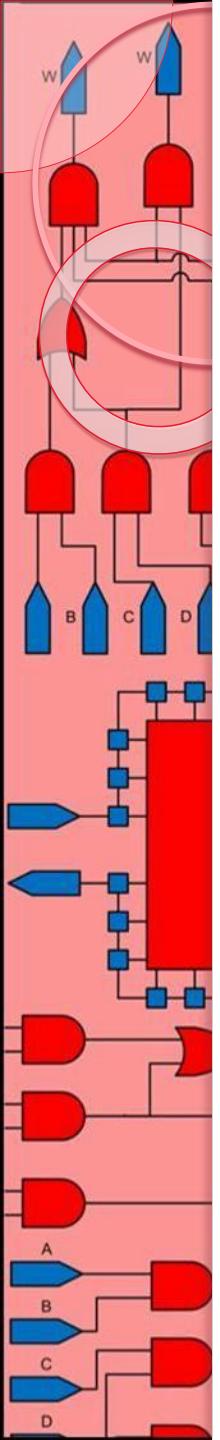

# Hierarchical Expression Level Design


- Periodic data application

```
`timescale 1ns/1ns

module RateSelectoreTester ();
    reg ai=0, bi=0, ci=0, di=0, ei=0;
    wire yo;


    RateSelector MUT ( ai, bi, ci, di, ei, yo );

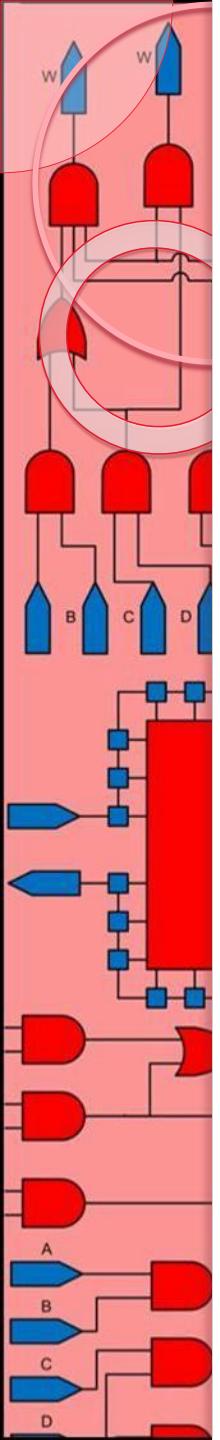    always #17 ai = ~ai;
    always #33 bi = ~bi;
    initial begin
        #97; ci=0; di=0; ei=1;
        #97; ci=1; di=0; ei=1;
        #97; ci=0; di=0; ei=0;
        #97; ci=1; di=1; ei=1;
        #97; ci=0; di=1; ei=0;
        #97; $stop;
    end
endmodule
```


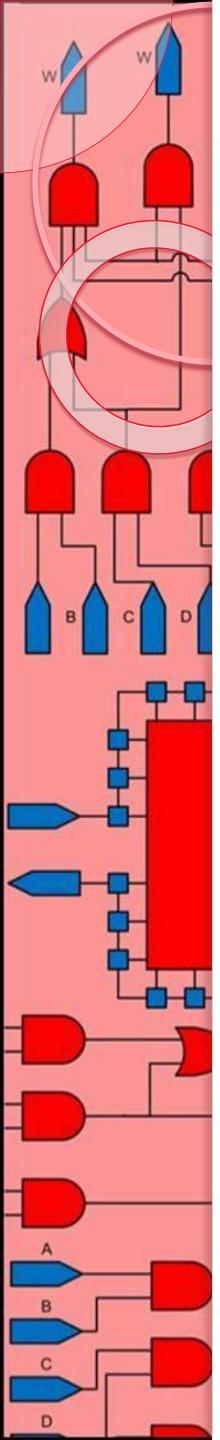
# Summary

- Expression in Verilog
- Assignments from Boolean
- Use of assign statements
- Multiple assignments
- Delay values
- Two versions of Rate Selector




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 6: Timing and Dynamic Hazards

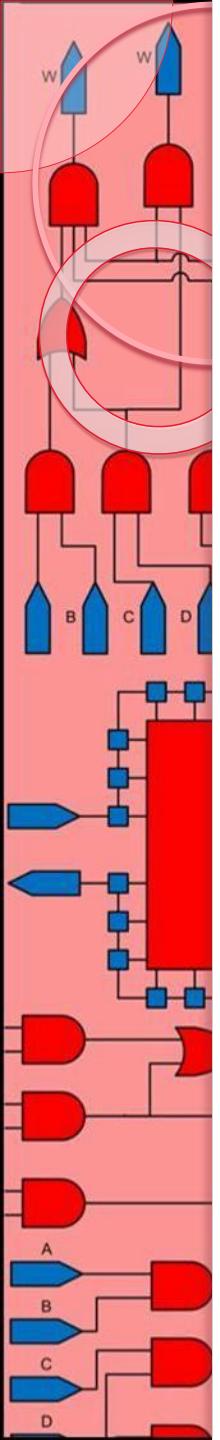
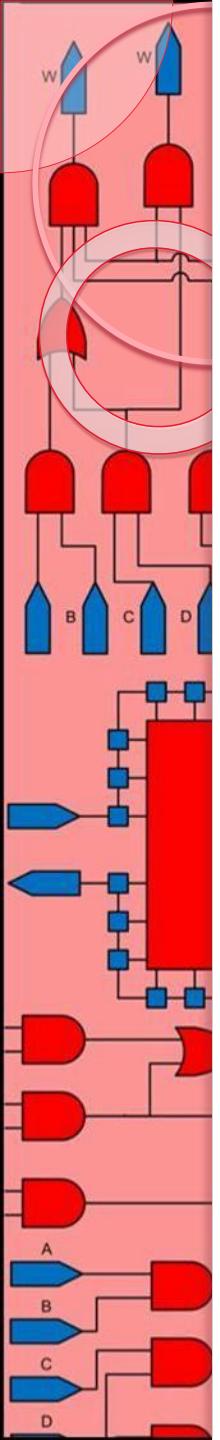
# Timing and Static Hazards

- Hazards
- Multiplexer Example
- Hazards on Karnaugh Maps
- Preventing Hazards
- Four Variable Example
- Summary



# Hazards

- Change in one input
- I-Hazard
  - Should be 1, but a 0-glitch
- 0-Hazard
  - Should be 0, but a 1-glitch

# Multiplexer Example


- Multiplexer Example – Using AND OR gates

```
`timescale 1ns/1ns

module mux2to1 ( input a, b, s, output y );
    wire sn, asn, bs;

    not #7 (sn, s);
    and #4 (asn, a, sn);
    and #4 (bs, b, s);
    or #3 (y, asn, bs);

endmodule
```

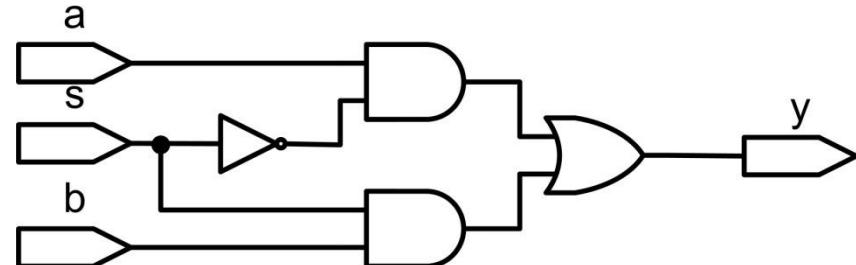

Verilog Code for the Multiplexer

# Multiplexer Example


- Multiplexer Testbench

```
`timescale 1ns/1ns


module mux2to1Tester ();
    reg ai=0, bi=0, si=0;
    wire yo;

    mux_2to1 MUT ( ai, bi, si, yo );

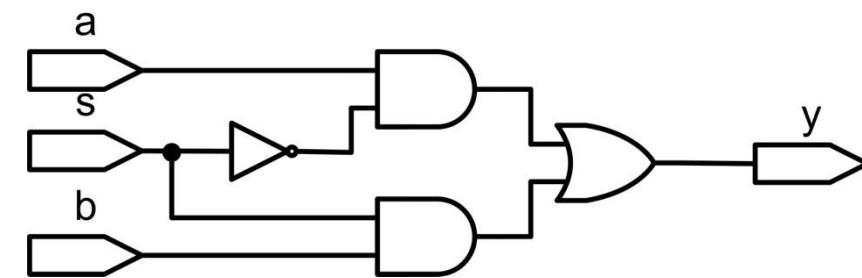    initial begin
        #29; ai=1; bi=0; si=0;
        #29; ai=1; bi=1; si=0;
        #29; ai=1; bi=1; si=1;
        #29; ai=1; bi=1; si=0;
        #29; ai=1; bi=1; si=1;
        #29; $stop;
    end
endmodule
```




# Multiplexer Example

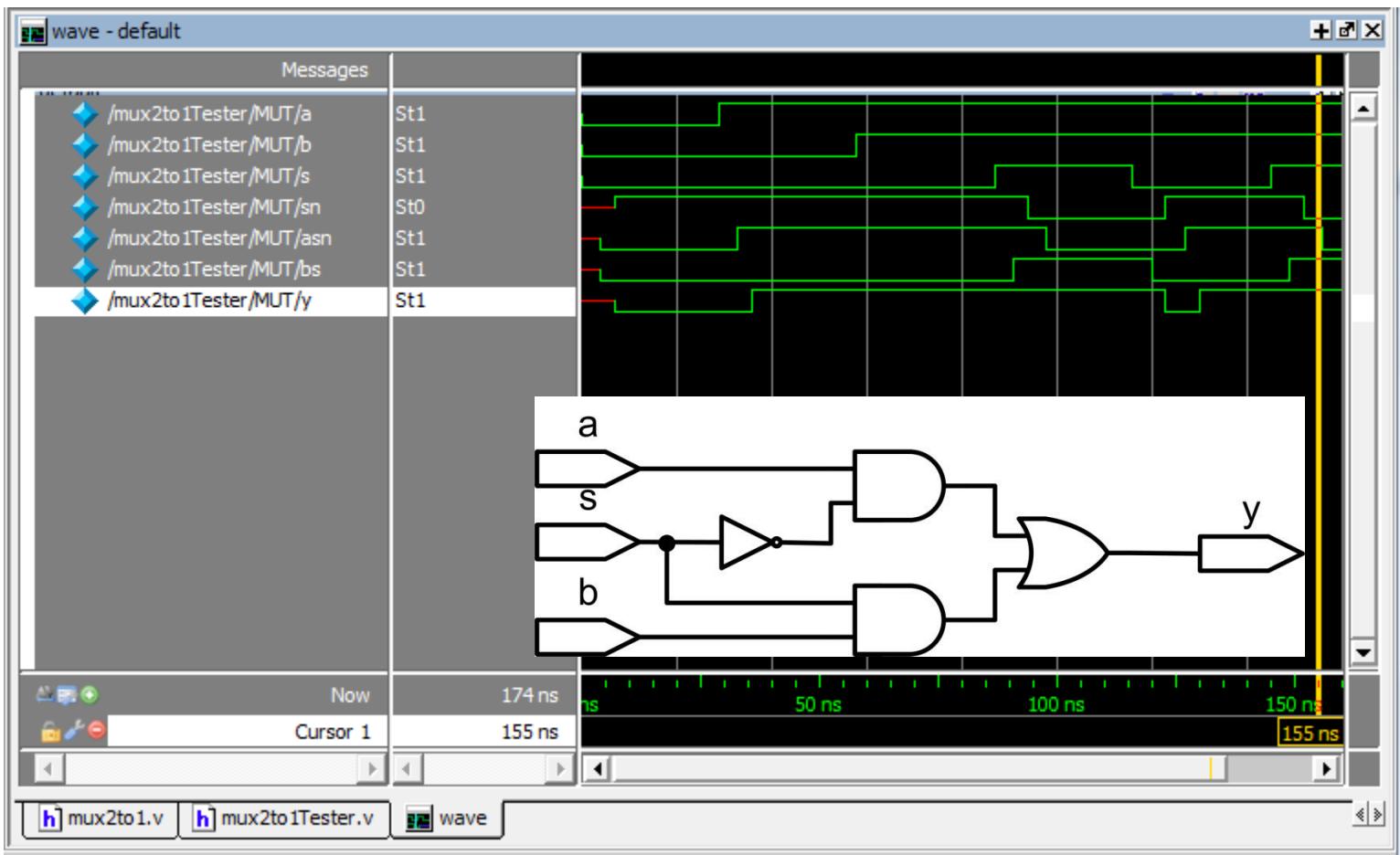


# Multiplexer Example

- Hazard Correction K-Map

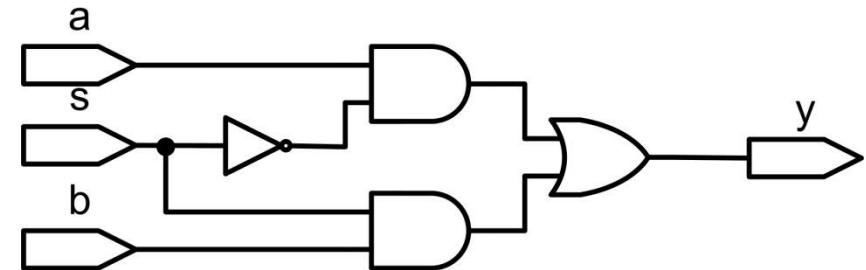
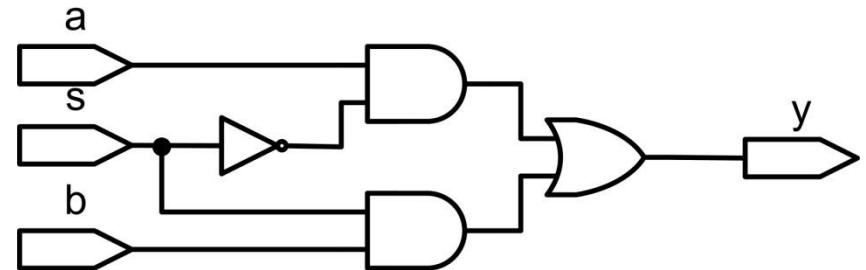
# Preventing Hazards

- Map adjacent 1's in AND-OR circuits
- Map adjacent 0's in OR-AND circuits



# Four Variable Maps

- From KM
  - Show circuit
  - Add gates to remove hazards

a,b \ c,d	00	01	11	10
00	1	1	1	1
01			1	1
11		1	1	1
10	1			


# Four Variable Maps

- From KM
  - Show circuit
  - Add gates to remove hazards

a,b \ c,d	00	01	11	10
00	1	1	1	1
01			1	1
11		1	1	1
10	1			


# Four Variable Maps

```
module HazardNotSeen (input a, b, c, d, output w);  
  
    assign w = (~c & ~d) |  
              (a & d) |  
              (~a & b & c);  
  
endmodule
```

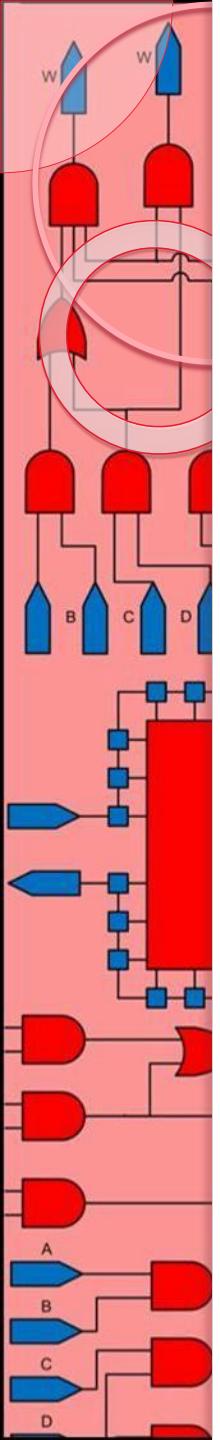
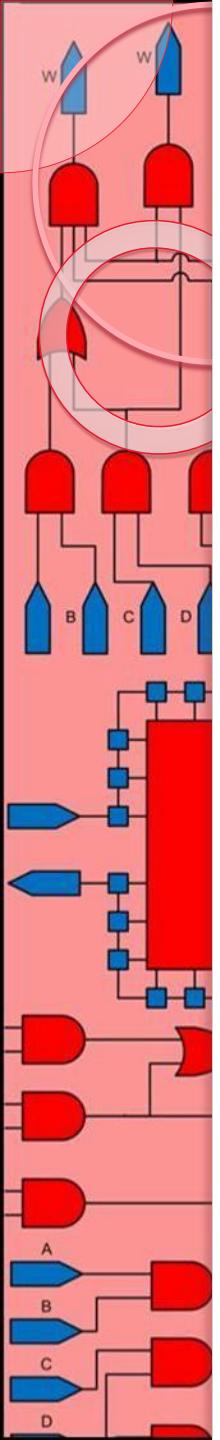
# Summary

- Hazards
- Multiplexer Example
- Hazards on Karnaugh Maps
- Preventing Hazards
- Four Variable Example
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 7: Arithmetic Circuits

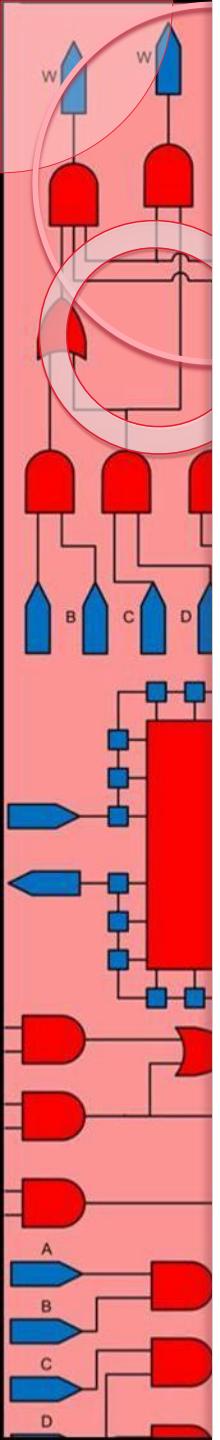
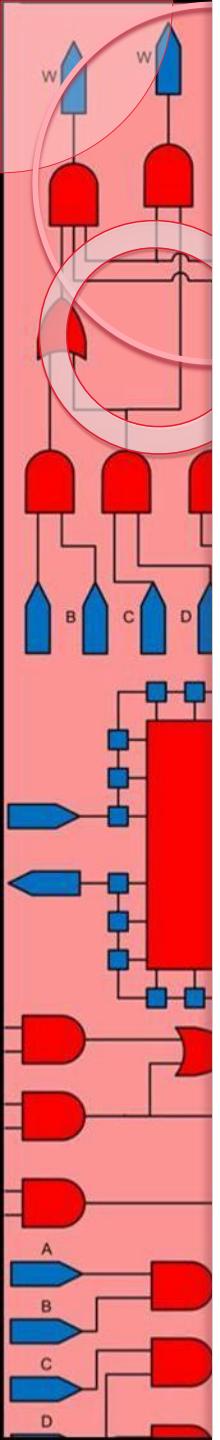
# Arithmetic Circuits

- New operations
- Full adder
- Vector inputs
- Structural adder
- Adder using expressions
- A multi-function module
- More on Testbenches
- Summary




# New Operations

- Use Verilog **assign** statement
- Position in module code is irrelevant
- Use the following notations:
  - For Adding use: +
  - For Subtracting use: -
  - For Comparing use: < > <= >= ==
  - For Condition use: ?:
  - For Concatenation use: { }
  - Use parenthesis for enforcing precedence
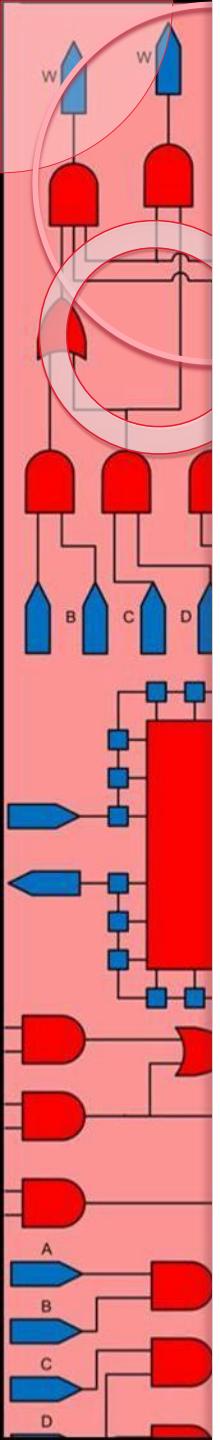
# New Operation

- Use Verilog **assign** statement
- Format:  
**assign w = a + b;**  
**assign w = a - b**  
**assign w = (f==1) ? y : z;**  
**assign w = (a > b) ? a : b;**
- Vector format [7:0]
- Output is w and is a vector, e.g., w[7:0]
- Inputs are a, b, f
  - a and b are vectors
  - f is a scalar



# New Operations

- Module Outline

```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```

```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @ (i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

# Full Adder

- Descriptions by Use of Equations
  - Sum output

```
`timescale 1ns/1ns

module xor3 ( input a, b, c, output y );
    assign y = a ^ b ^ c;
endmodule
```

## XOR Verilog Code


# Full Adder

- Descriptions by Use of Equations
  - Carry output

```
`timescale 1ns/1ns

module maj3 ( input a, b, c, output y );
    assign y = (a & b) | (a & c) | (b & c);
endmodule
```

## Majority Verilog Code

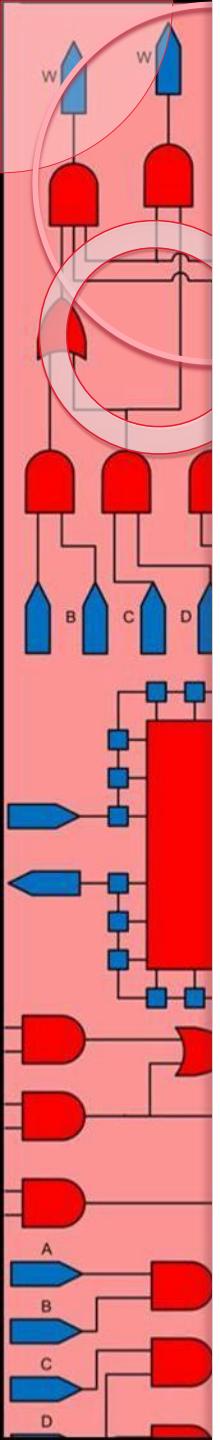

# Full Adder

- Descriptions by Use of Equations
  - Full-Adder Example

```
`timescale 1ns/1ns





module fulladder ( input a, b, ci, output s, co );
    assign #(10) s = a ^ b ^ ci;
    assign #(8) co = ( a & b ) | ( b & ci ) | ( a & ci );
endmodule
```

## Full Adder Verilog Code

# Structural Adder

- A simpler design of full-adder
- Using 8 full-adders to build an 8-bit adder

a	b	c <sub>i</sub>	c <sub>0</sub>	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

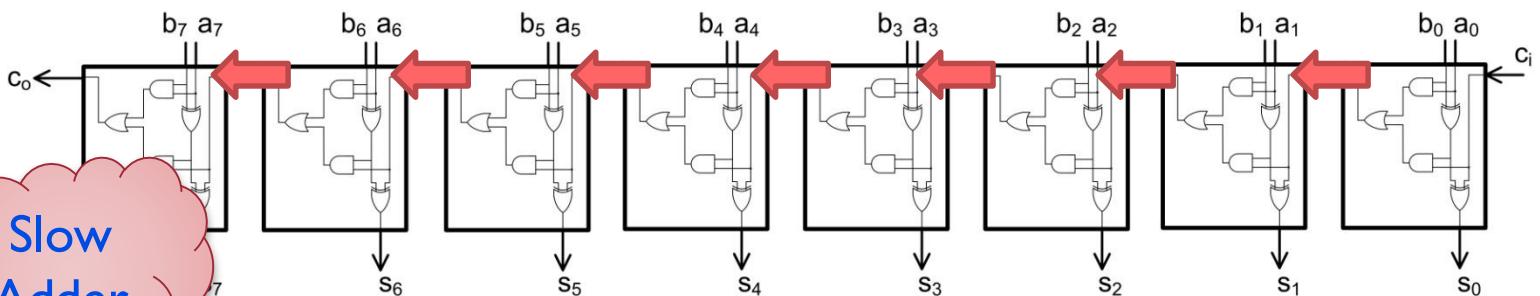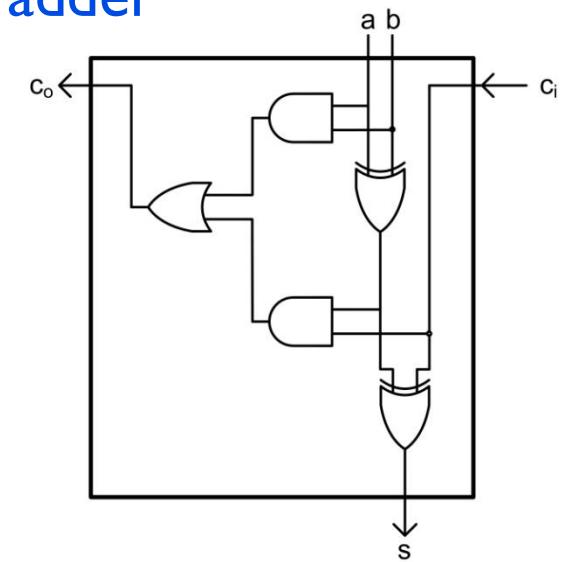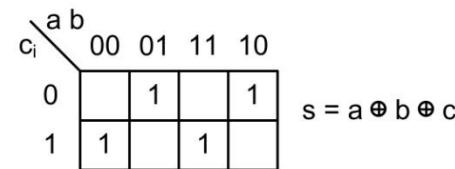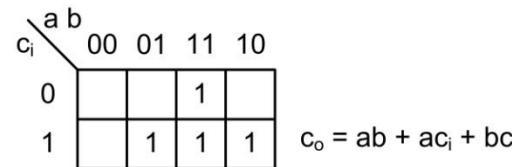

Slow  
Adder


July 2014

# Structural Adder

- Descriptions by Use of Equations
  - Full-Adder using fewer gates

```
`timescale 1ns/1ns

module fulladder ( input a, b, ci, output s, co );
    wire axb;
    assign axb = a ^ b;
    assign s = axb ^ ci;
    assign co = ( a & b ) | ( axb & ci );
endmodule
```

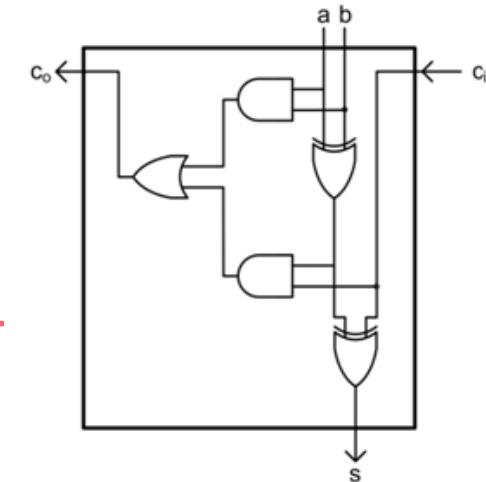


## Full Adder Verilog Code

# Structural Adder


- Instantiate 8 full-adders

```
`timescale 1ns/1ns

module adder8 ( input [7:0] a, b, input ci,
                  output [7:0] s, output co );
    wire [7:0] c;
    assign c[0] = ci;
    fulladder FA0 (a[0], b[0], c[0], s[0], c[1]);
    fulladder FA1 (a[1], b[1], c[1], s[1], c[2]);
    fulladder FA2 (a[2], b[2], c[2], s[2], c[3]);
    fulladder FA3 (a[3], b[3], c[3], s[3], c[4]);
    fulladder FA4 (a[4], b[4], c[4], s[4], c[5]);
    fulladder FA5 (a[5], b[5], c[5], s[5], c[6]);
    fulladder FA6 (a[6], b[6], c[6], s[6], c[7]);
    fulladder FA7 (a[7], b[7], c[7], s[7], co);
endmodule
```

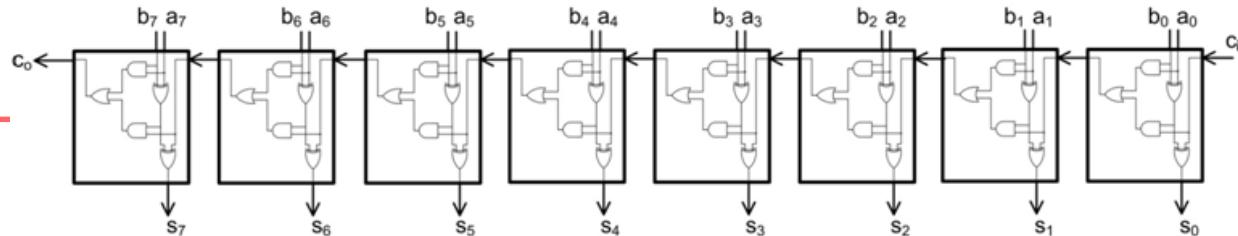

Eight-bit Adder Verilog Code

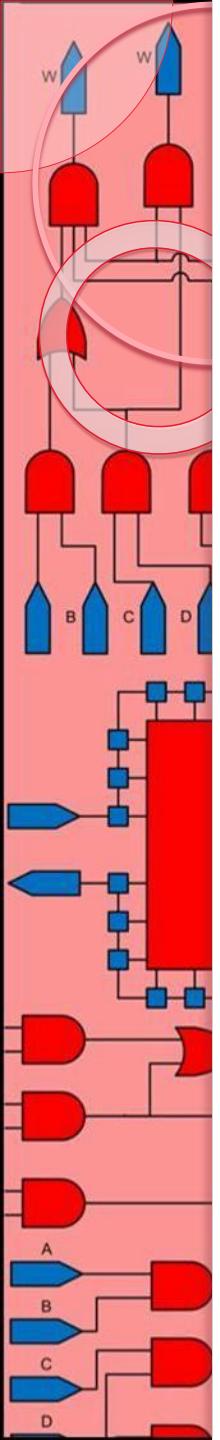

# Adder Using Expressions

- Use assign statement and concatenation


```
`timescale 1ns/1ns

module adder8 ( input [7:0] a, b, input ci,
                  output [7:0] s, output co );

    assign {co, s} = a + b + ci;

endmodule
```

Eight-bit Functional Adder Verilog Code

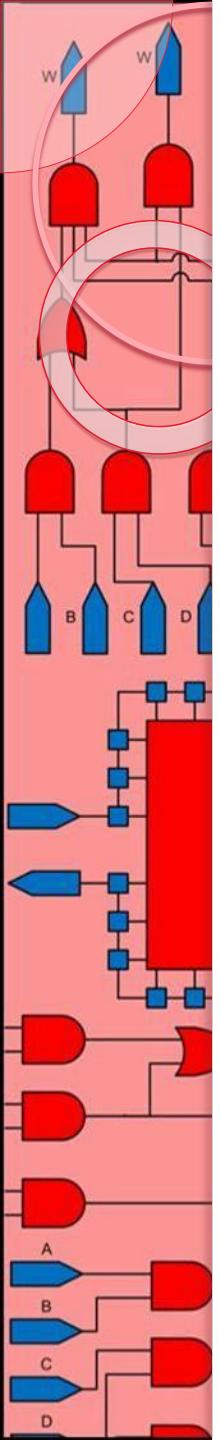


# Multi Function Modules

- Descriptions by Use of Equations
  - ALU Example

```
module ALU ( input [7:0] a, b, input addsub,
              output gt, zero, co, output [7:0] r );

    assign {co, r} = addsub ? (a + b) : (a - b);
    assign gt = (a>b);
    assign zero = (r == 0);
endmodule
```

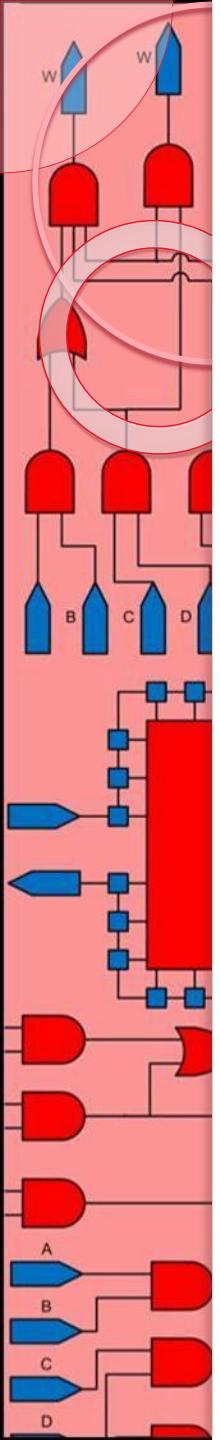**ALU Verilog Code Using a Mix of Operations**



# Testbenches

- Use initial repeat

```
`timescale 1ns/1ns

module adder8testbench ();
    reg [7:0] ai, bi;
    reg ci=0;
    wire [7:0] so;
    wire co;


    adder8 UUT (ai, bi, ci, so, co);
    initial repeat (20) #17 ai = $random;
    initial repeat (16) #23 bi = $random;


endmodule
```

## Eight-bit Adder Verilog Testbench

# Testbenches


- Simulation results

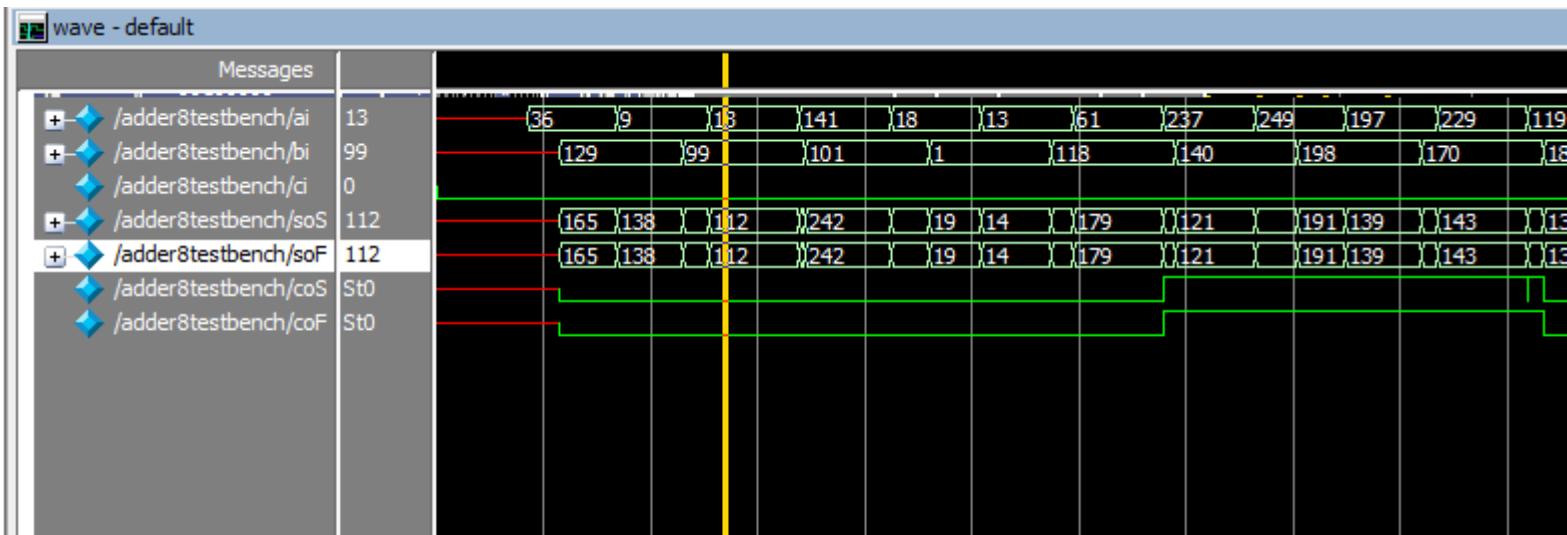

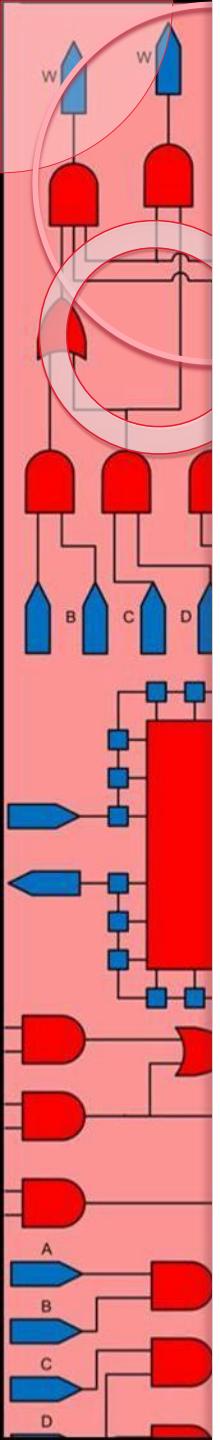
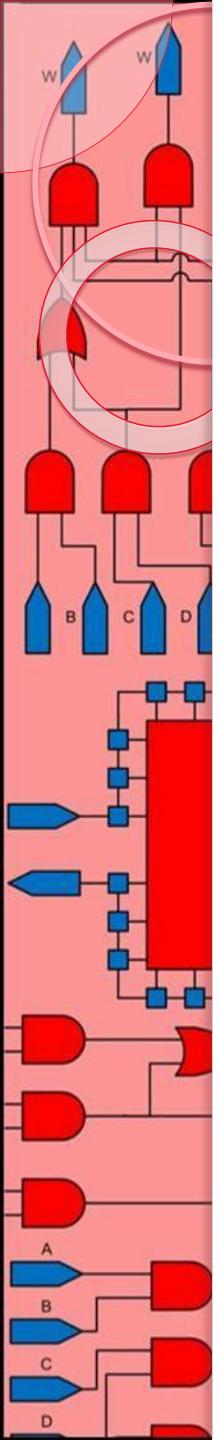
# Summary

- New operations
- Full adder
- Vector inputs
- Structural adder
- Adder using expressions
- A multi-function module
- More on Testbenches
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog

## Lecture 8: Behavioral Modeling

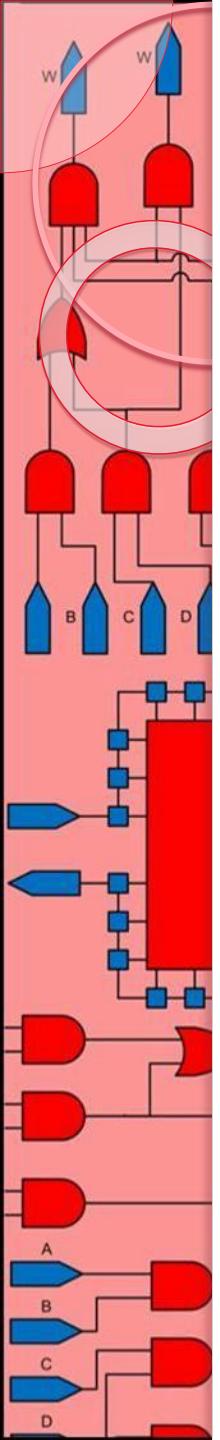

# Behavioral Modeling


- New constructs
  - Procedural blocks
  - Procedural statements
- Procedural always block
  - Majority circuit
  - Full adder
- Delay options
- Procedural statements
- A behavioral ALU
- Summary

# New Constructs

- Use Verilog **always** statement
- Position of various **always** statements in module code is irrelevant
- Position of statements within an **always** statements is important
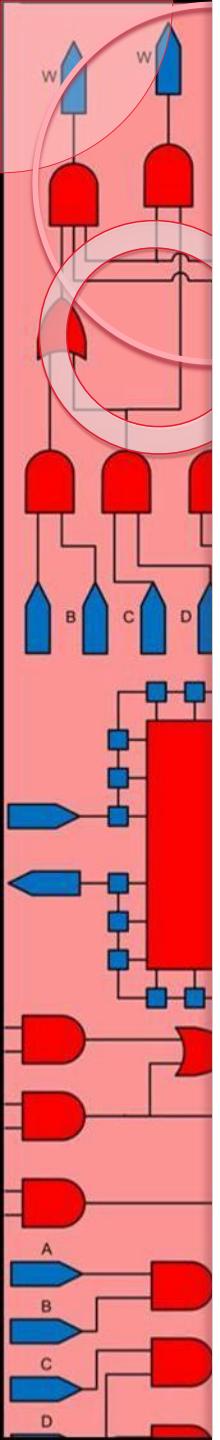
# New Constructs

- Use the following constructs:
  - Procedural if:      `if (a==b) DoThis else DoThat;`
  - Procedural if:      `if (a==b) begin ... end`  
                              `else begin ... end`
  - Procedural case:     `case (expr)`  
                              `0: ...`  
                              `1: ...`  
                              `2: ...`  
                              `endcase`



# New Operations

- Module Outline

```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```

```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @(i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```

# Procedural always Block

- XOR example

```
`timescale 1ns/1ns

module xor3 ( input a, b, c,
                output reg y );

    always @ (a, b, c) y = a ^ b ^ c;

endmodule
```

## XOR Verilog Code

# Procedural always Block

- Majority Example

```
module maj3 ( input a, b, c, output reg y );  
  
    always @ ( a or b or c )  
    begin  
        y = (a & b) | (b & c) | (a & c);  
    end  
  
endmodule
```

Procedural Block Describing a Majority Circuit

# Delay Options

- Majority example with delay


```
'timescale 1ns/100ps

module maj3 ( input a, b, c, output reg y );

    always @ (a, b, c )
        #5 y = (a & b) | (b & c) | (a & c);

endmodule
```

## Majority Gate with Delay

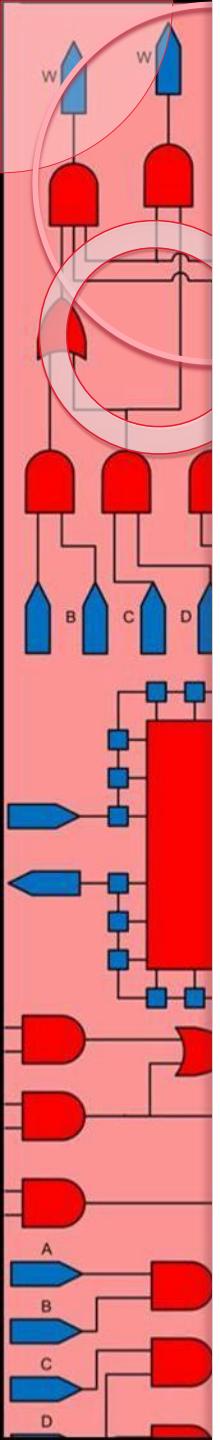


# Delay Options

- Descriptions with procedural statements
  - Full-Adder example

```
`timescale 1ns/100ps
module add_1bit ( input a, b, ci,
                   output reg s, co );
  always @( a, b, ci )
    begin
      s = #5 a ^ b ^ ci;
      co = #3 (a & b) | (b & ci) | (a & ci);
    end
endmodule
```
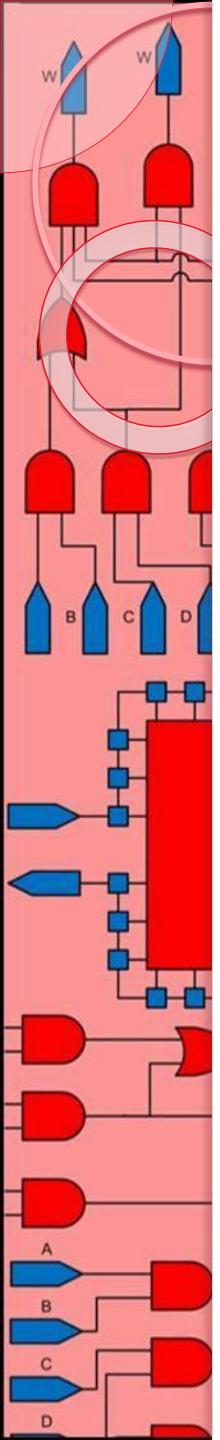
## Full-Adder Using Procedural Assignments



# Delay Options

- Descriptions with procedural statements
  - Full-Adder example

```
`timescale 1ns/100ps
module add_1bit ( input a, b, ci,
                   output reg s, co );
  always @( a, b, ci )
    begin
      s <= #5 a ^ b ^ ci;
      co <= #8 (a & b) | (b & ci) | (a & ci);
    end
endmodule
```


## Full-Adder Using Procedural Assignments

# Procedural Statements

- Descriptions with Procedural Statements
  - Procedural Multiplexer Example

```
module mux2_1 (input i0, i1, s, output reg y );
    always @( i0 or i1 or s ) begin
        if ( s==1'b0 )
            y = i0;
        else
            y = i1;
    end
endmodule
```

## Procedural Multiplexer

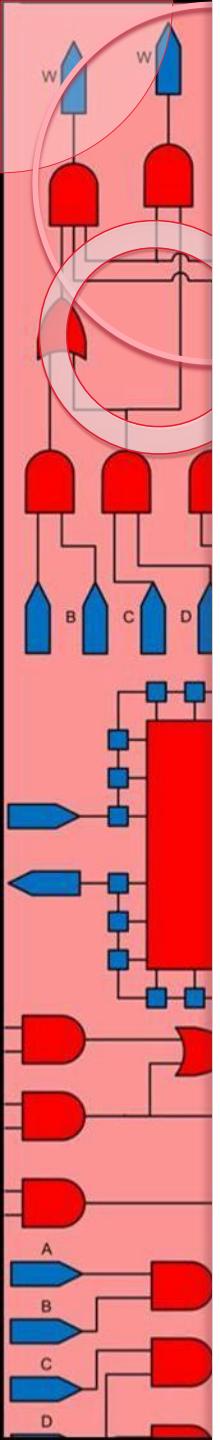


# Procedural Statements

- Descriptions with Procedural Statements
  - Procedural ALU Example


```
module alu_4bit (input [3:0] a, b, input [1:0] f,
                  output reg [3:0] y );
    always @ ( a or b or f ) begin
        case ( f )
            2'b00 : y = a + b;
            2'b01 : y = a - b;
            2'b10 : y = a & b;
            2'b11 : y = a ^ b;
            default: y = 4'b0000;
        endcase
    end
endmodule
```

## Procedural ALU

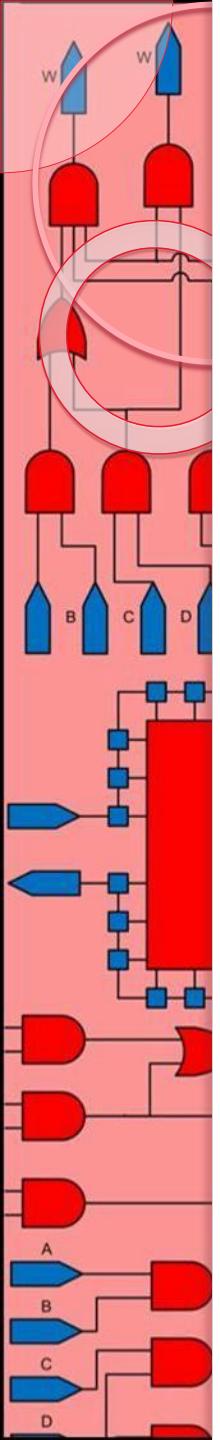
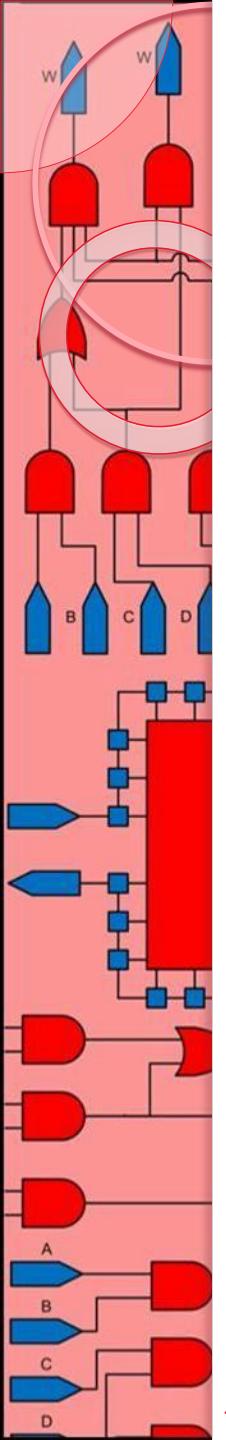
# Summary

- New constructs
  - Procedural blocks
  - Procedural statements
- Procedural always block
  - Majority circuit
  - Full adder
- Delay options
- Procedural statements
- A behavioral ALU
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog

## Lecture 9: Flip-Flop Modeling

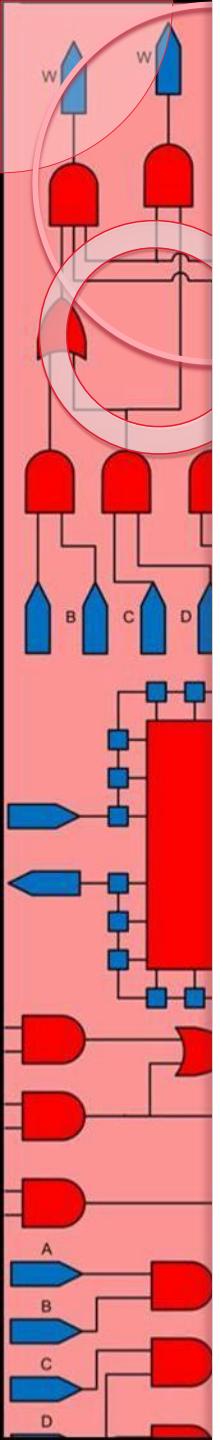


# Flip-flop Modeling

- New constructs
  - Procedural blocks
  - Posedge
  - Nonblocking assignment
- Edge sensitive **always** block
  - Clock edge
  - Asynchronous control
  - Clock enable
- Delay options
- D-type flip-flop
- More on Testbenches
- Summary
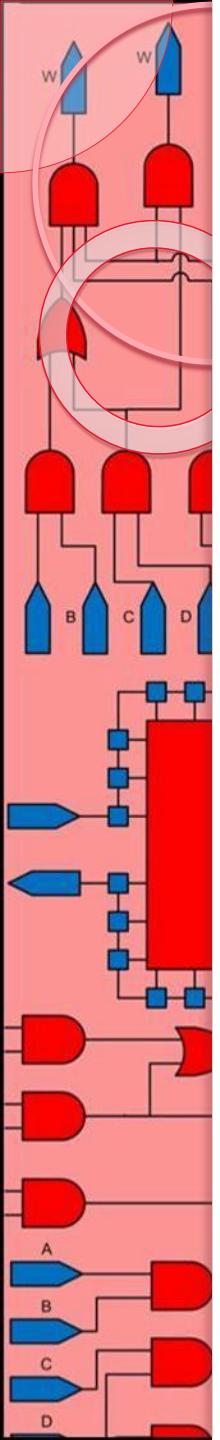
# New Constructs


- Use Verilog **always** statement
- Position of various **always** statements in module code is irrelevant
- Use **posedge** or **negedge** for edge
- Position of statements within an **always** statements is important
- Check for flip-flop functions according to their priority
- Assign flip-flop output using **<=**


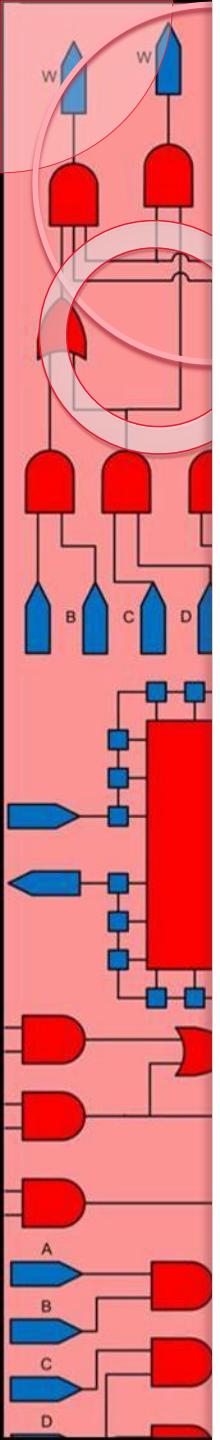
# Edge Sensitive **always** Block

- Use in the following forms:

- Clock detection:    `always @(posedge C) begin`  
                               `Q <= D;`  
                               `end`
  - Clock detection:    `always @(posedge C) Q <= D;`
  - Asynch reset:        `always @(posedge C, posedge R) begin`  
                               `if (R) Q <= 0;`  
                               `...`  
                               `end`
  - Clock enable:        `always @(posedge C) if (E) Q <= D;`



# Flip-flop Modeling

- Module Outline


```
module simple_1a (input i1, i2, i3, output w1, w2);
    wire c1;
    nor g1 (c1, i1, i2);
    and g2 (w1, c1, i3);
    xor g3 (w2, i1, i2, i3);
endmodule
```

```
module simple_1b (input i1, i2, i3, output w1, w2);
    assign w1 = i3 & ~ (i1 | i2);
    assign w2 = i1 ^ i2 ^ i3;
endmodule
```

```
module simple_1c (input i1, i2, i3, output w1, w2);
    reg w1, w2;
    always @(i1, i2, i3) begin
        if (i1 | i2) w1 = 0; else w1 = i3;
        w2 = i1 ^ i2 ^ i3;
    end
endmodule
```
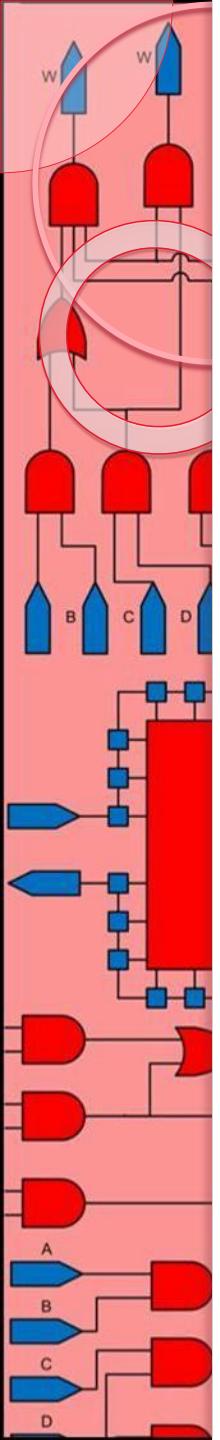
# Delay Options

- Delay after edge of C, before reading D, before scheduling into Q  
 $\#6 Q \leq D$
- Delay after edge of C, does not affect reading D, delay scheduling D into Q  
 $Q \leq \#5 D$
- After edge of C, wait 5, read D, wait 6, Q gets D  
 $\#6 Q \leq \#5 D$




# D-type flip-flop

- Basic D-type flip-flop

```
`timescale 1ns/1ns

module basic_dff ( input d, clk,
                     output reg q, output q_b );
    begin
        assign #3 q_b = ~q;
    end
endmodule
```

A Positive-Edge D Flip-Flop

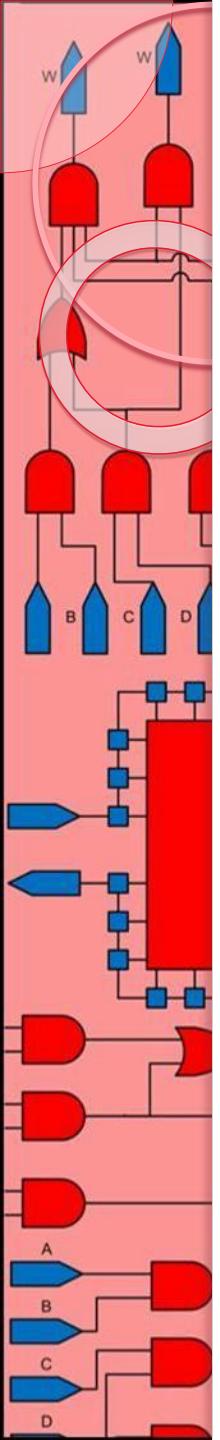

# D-type flip-flop

- D-type flip-flop with reset input


```
`timescale 1ns/1ns

moduledff_reset ( input d, clk, reset
                  output reg q);

    always @ (posedge clk, posedge reset) begin
        if (reset) q <= 1'b0;
        else q <= d;
    end

endmodule
```

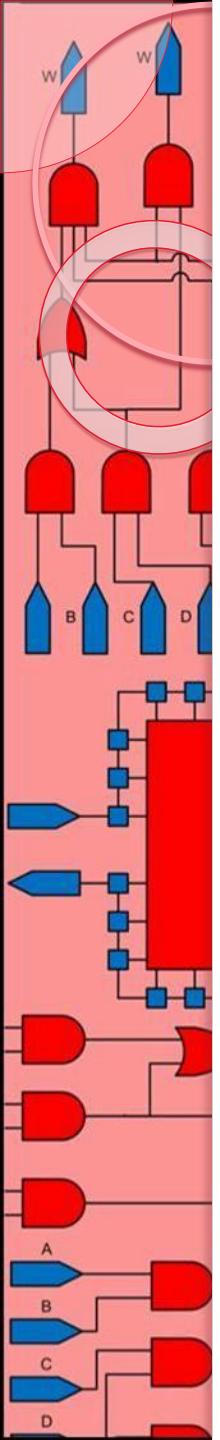A Positive-Edge D Flip-Flop with active high reset



# D-type flip-flop

- D-type flip-flop with reset input

```
`timescale 1ns/1ns

moduledff_reset ( input d, clk, reset
                  output reg q);



    always @( posedge clk, negedge reset ) begin
        if (~reset) q <= 1'b0;
        else q <= d;
    end

endmodule
```

A Positive-Edge D Flip-Flop with active low reset
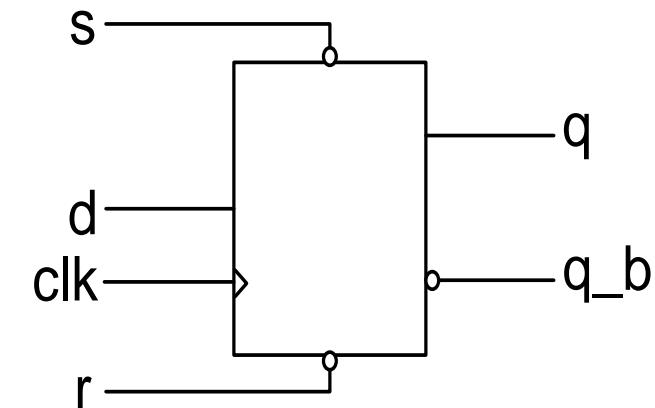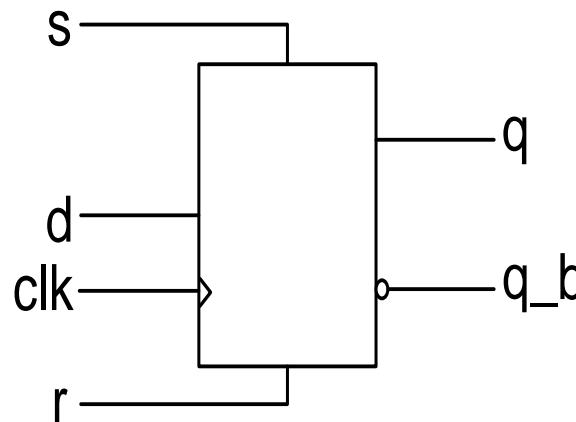
# D-type flip-flop

- Memory Elements Using Procedural Statements
  - Asynchronous Control



# D-type flip-flop

- D-type flip-flop with set and reset input


```
`timescale 1ns/1ns

moduledff_reset ( input d, clk, set, reset
                  output reg q);

    always @ (posedge clk, posedge reset, posedge set)
        if (reset) q <= 1'b0;
        else if (set) q <= 1'b1;
        else q <= d;

endmodule
```

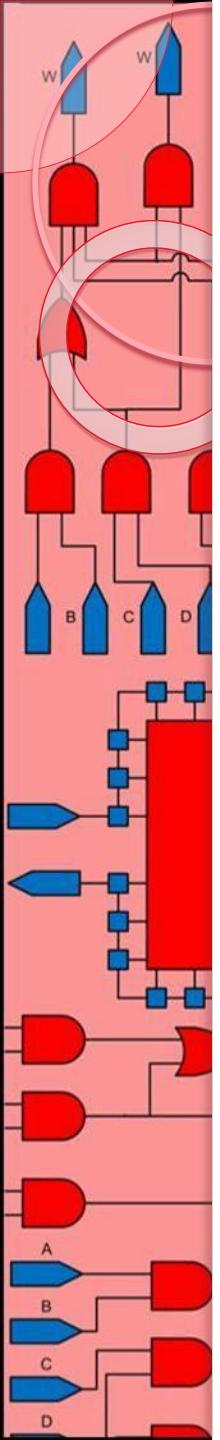A Positive-Edge D Flip-Flop with active high set and reset



# D-type flip-flop

- D-type flip-flop with clock enable


```
`timescale 1ns/1ns

moduledff_enable ( input d, clk, en,
                    output reg q);

    always @ (posedge clk)
        if (en) q <= d;

endmodule
```

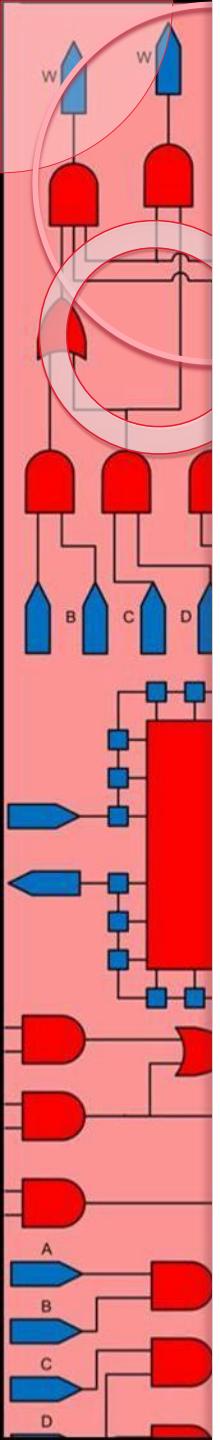A Positive-Edge D Flip-Flop with active high enable



# More on Testbenches

- Apply periodic clock

```
`timescale 1ns/1ns

module dffTester ();
    reg di=0, clk_i=0, eni=0;
    wire qo;

dff_enable MUT ( di, clk_i, eni, qo );

always #29 clk_i = ~ clk_i;

initial begin
    #23 di=0; #37 di=1; #23 di=0; #37 di=1;
    #23 di=0; #37 di=1; #23 di=0; #37 di=1;
    $stop;
end


initial begin #37 eni=1; #187 eni=0; end
endmodule
```

```
`timescale 1ns/1ns

module dff_enable (input d, clk, en,
                    output reg q);


    always @ (posedge clk)
        if (en) q <= d;

endmodule
```

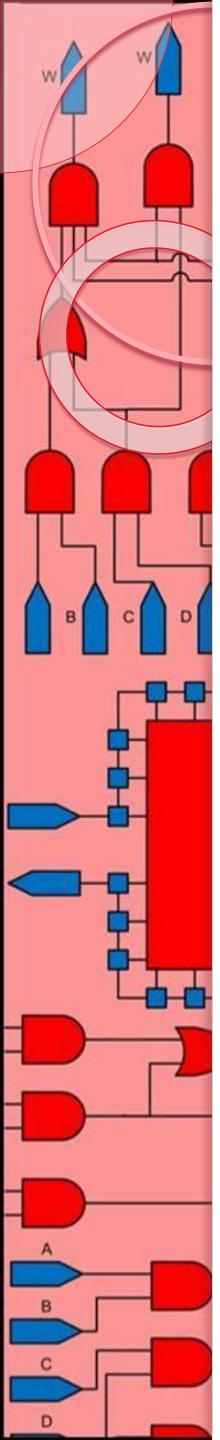
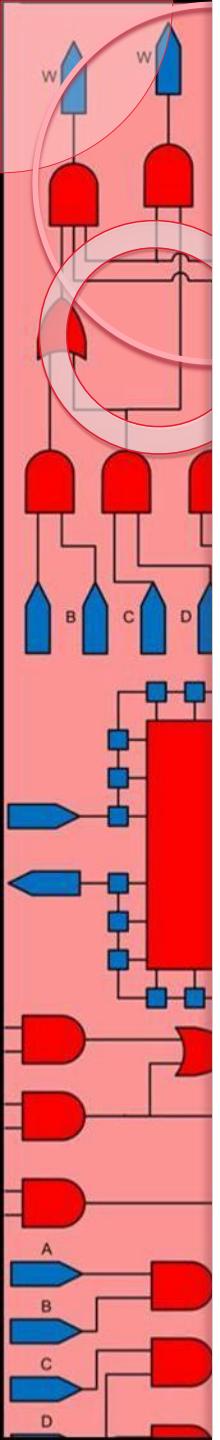
# Summary

- New constructs
  - Procedural blocks
  - Posedge
  - Nonblocking assignment
- Edge sensitive **always** block
  - Clock edge
  - Asynchronous control
  - Clock enable
- Delay options
- D-type flip-flop
- More on Testbenches
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog
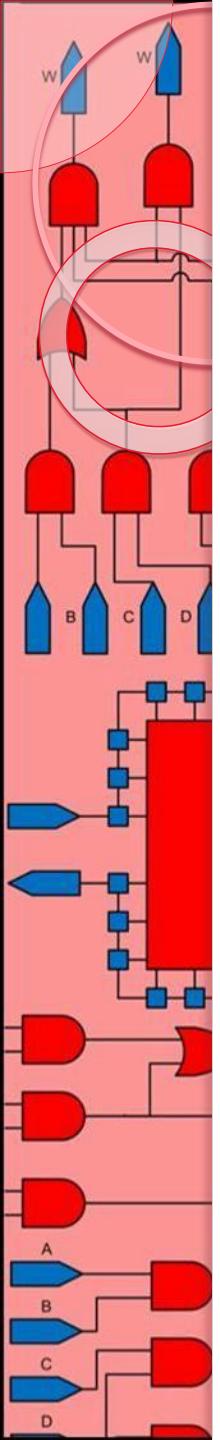
## Lecture 10: Elements of RT Level Design




# Outline

- RTL Big Picture View
- Processing Elements
- Bussing System
- Controller
- Summary

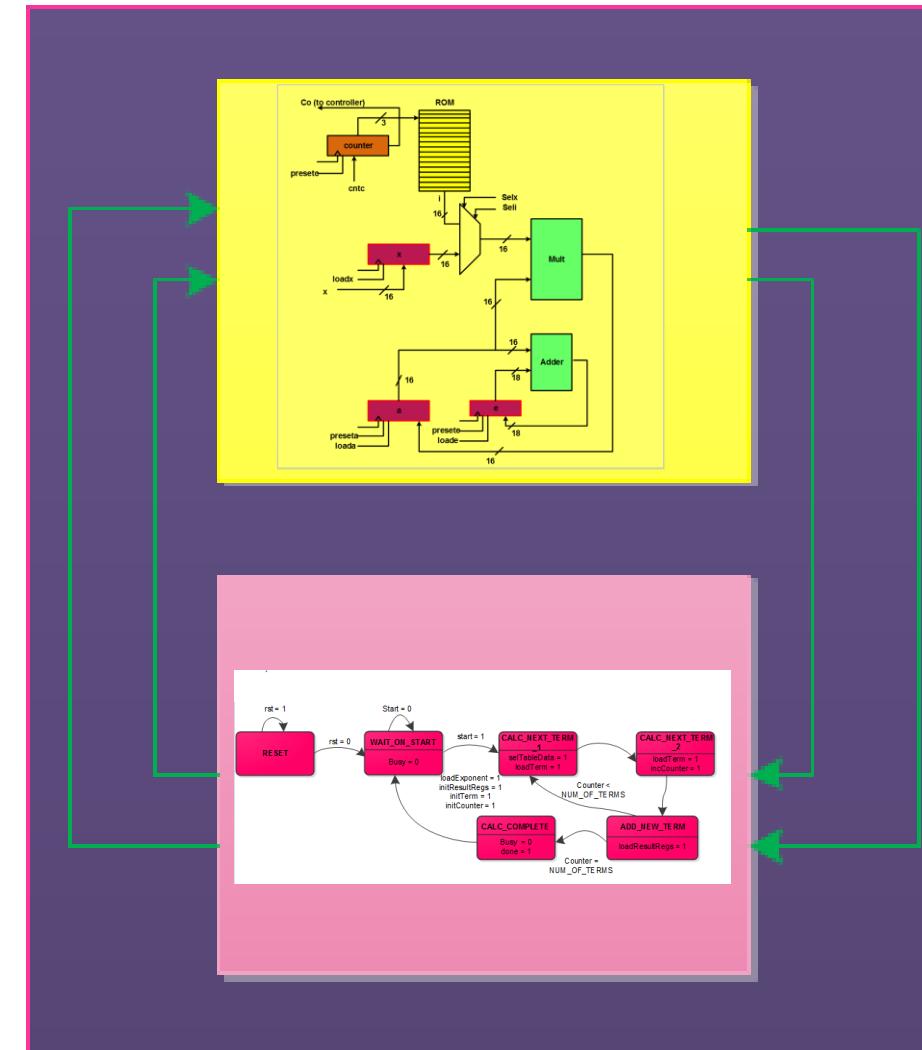
# RTL Big Picture View

- Datapath
  - Combinational elements
  - Sequential elements
  - Bussing structure
- Controller
  - State machines






# Processing Elements

- Combinational elements

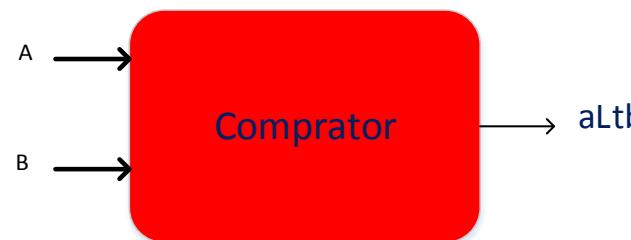



- Sequential elements

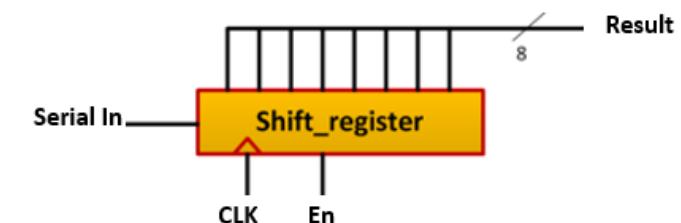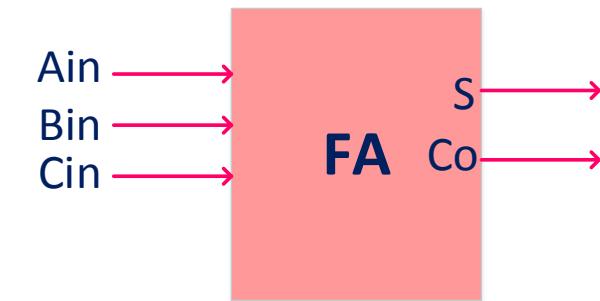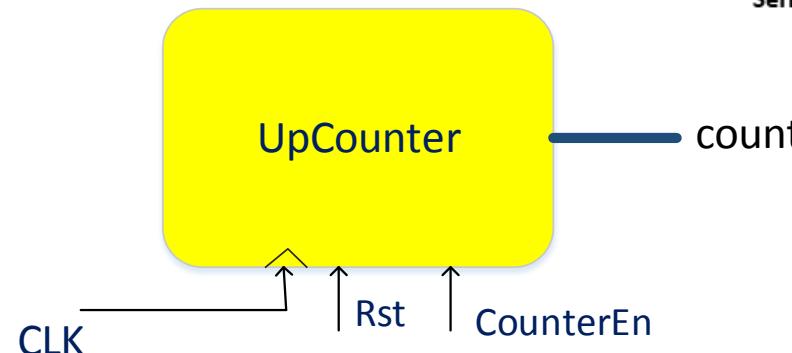

# Bussing System: Intra RTL Communication



- Bussing structure

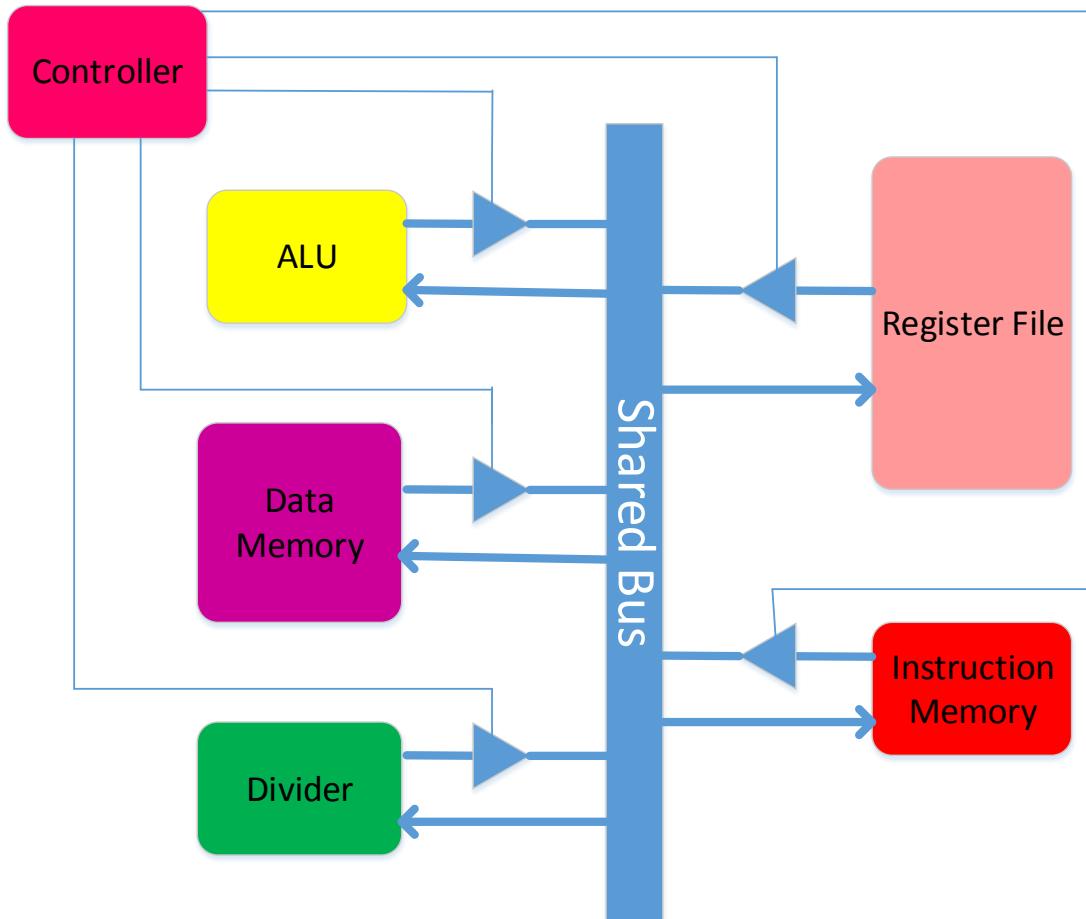


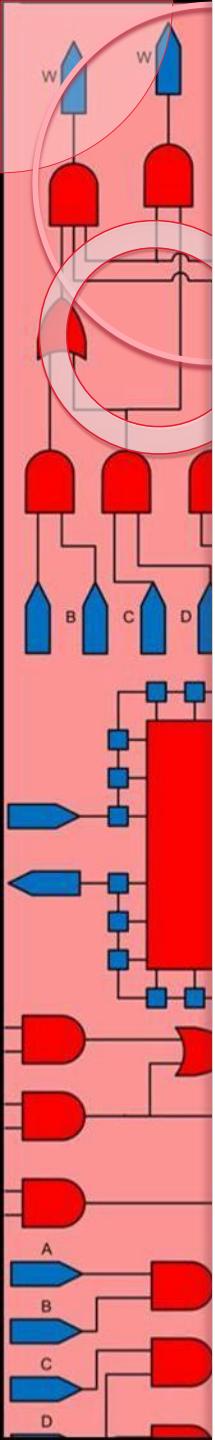
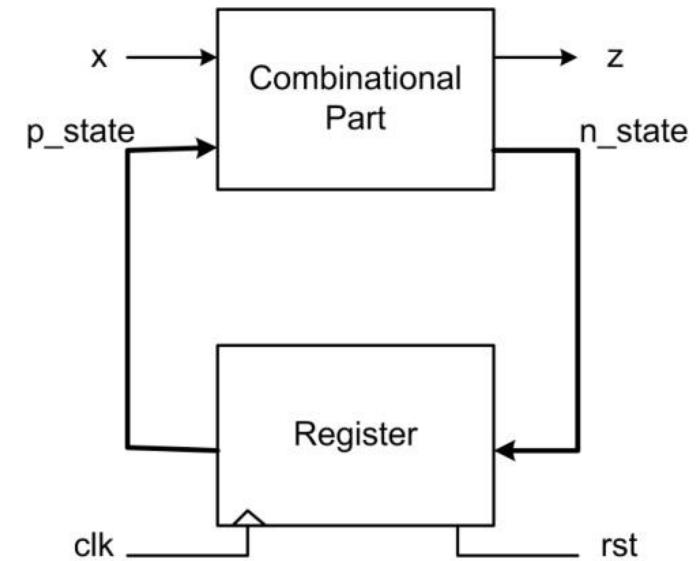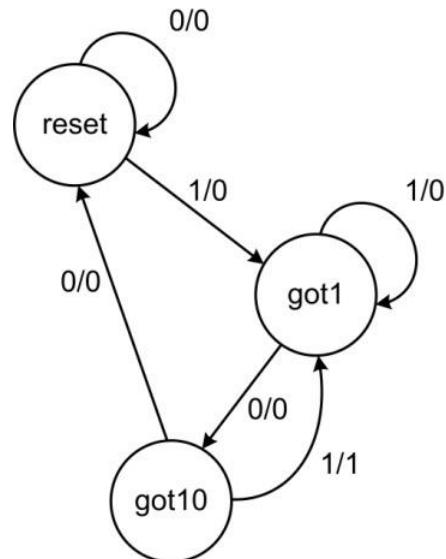
# Controller:


- State machines
  - Mealy/ Moore
  - Huffman coding style



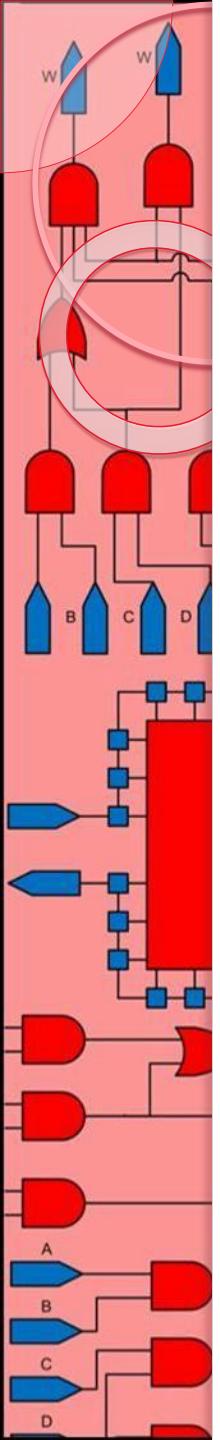
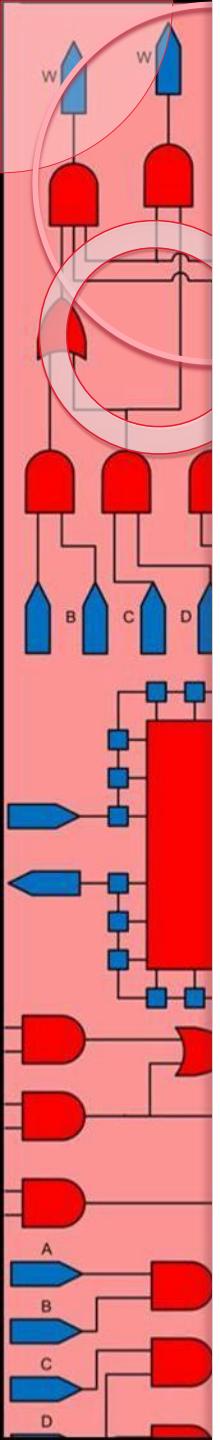
# Outline

- RTL Big Picture View
- Processing Elements
- Bussing System
- Controller
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog
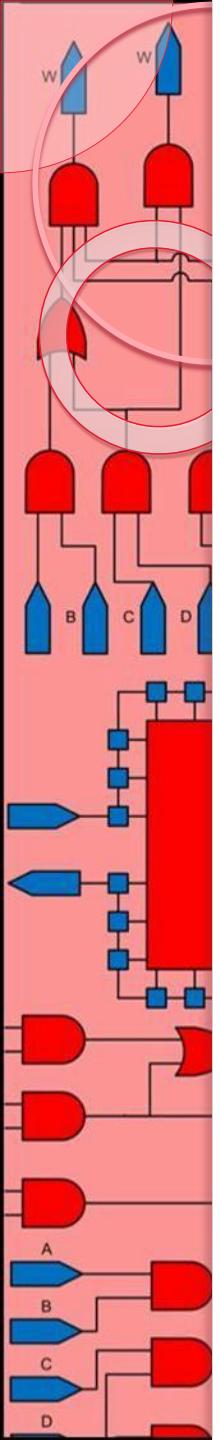
## Lecture 11: Combinational Elements of RTL Design (Datapath building blocks)


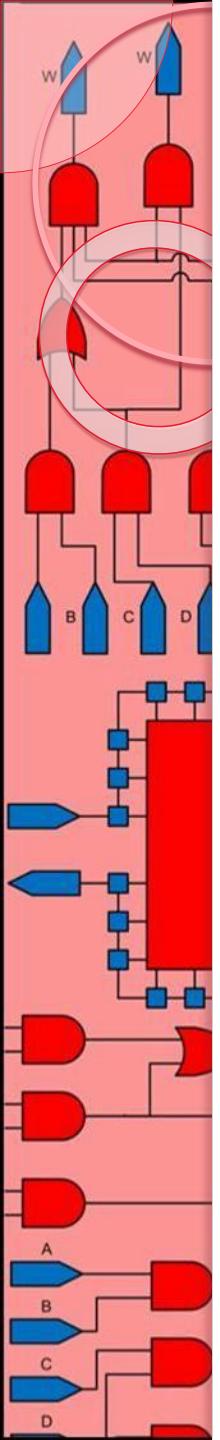
# Combinational Elements of RTL Design

- Logic units, arithmetic units, busses
  - Random logic
  - Iterative hardware
  - Bussing system
  - General logic units




# Random logic

- A Boolean expression example

```
module someLogic ( input a, b, c, d, output y );  
  
    assign y = ((a&b) | (b&c) | (a&c)) ^ d;  
  
endmodule
```

## A concurrent assign statement

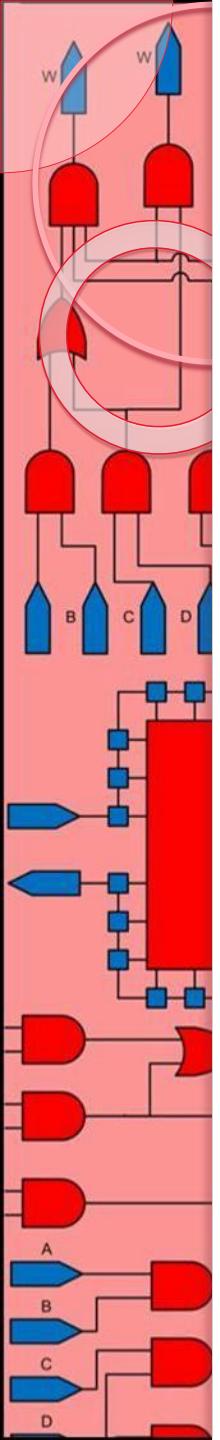


# Random logic

- A conditional expression example


```
module sameLogic ( input a, b, c, d, output y );  
  
assign y = d ? ~((a&b) | (b&c) | (a&c)) :  
          ((a&b) | (b&c) | (a&c));  
  
endmodule
```


## A concurrent assign statement

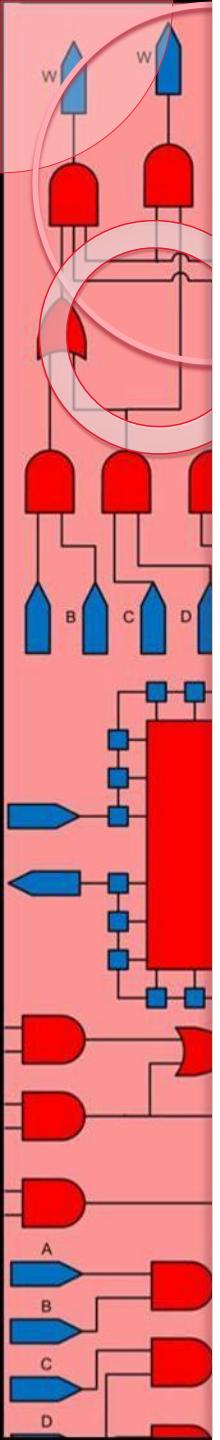

# Iterative logic

- 32-bit ripple carry adder

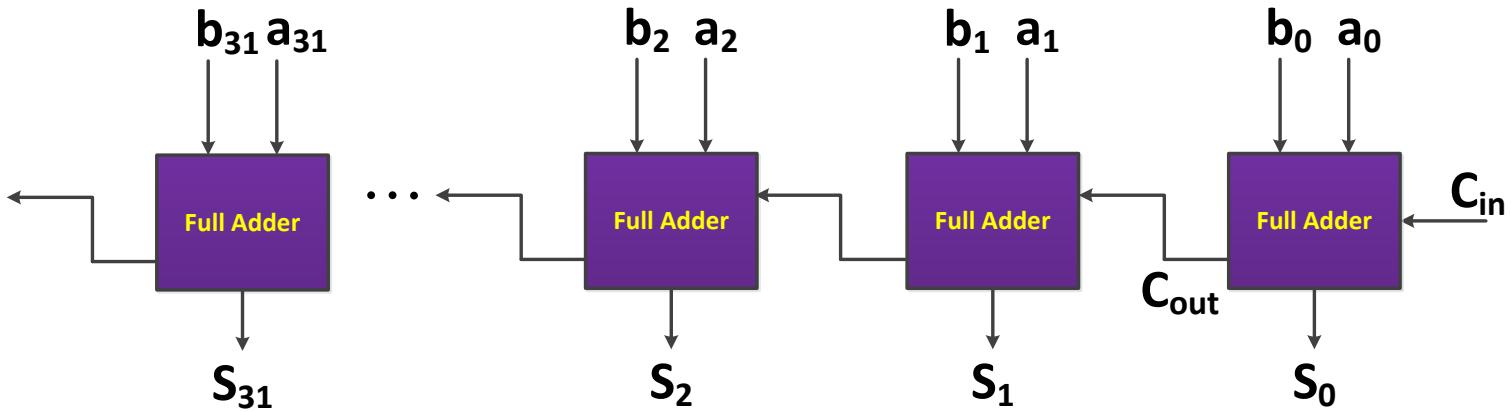


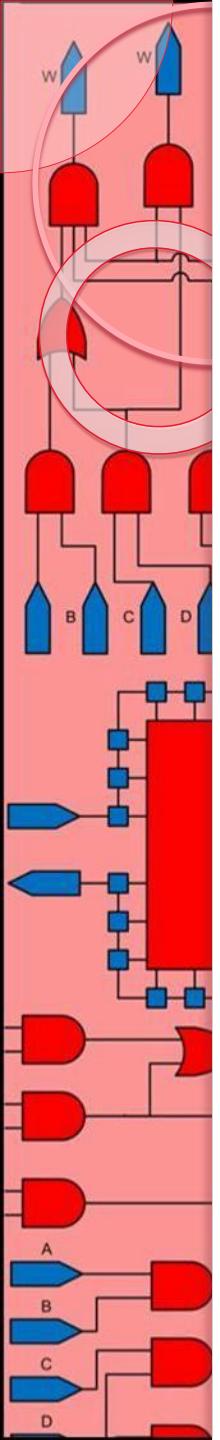
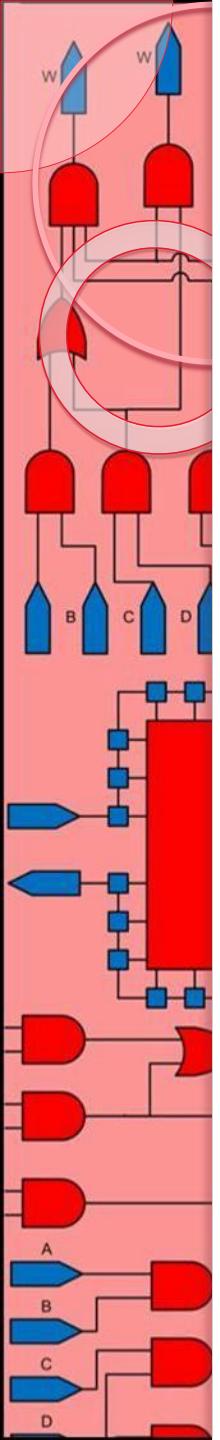
# Iterative logic

- 8-bit ripple carry adder, 8 instantiations


```
module RippleCarryAdder (a, b, c0, sum, carry);
    input [7:0] a, b;
    input c0;
    output [7:0] sum;
    output carry;
    wire [7:0] c;
    FullAdder FA0(a[0],b[0],c0 ,sum[0],c[0]);
    FullAdder FA1(a[1],b[1],c[0],sum[1],c[1]);
    FullAdder FA2(a[2],b[2],c[1],sum[2],c[2]);
    FullAdder FA3(a[3],b[3],c[2],sum[3],c[3]);
    FullAdder FA4(a[4],b[4],c[3],sum[4],c[4]);
    FullAdder FA5(a[5],b[5],c[4],sum[5],c[5]);
    FullAdder FA6(a[6],b[6],c[5],sum[6],c[6]);
    FullAdder FA7(a[7],b[7],c[6],sum[7],c[7]);
    assign carry = c[7];
endmodule
```


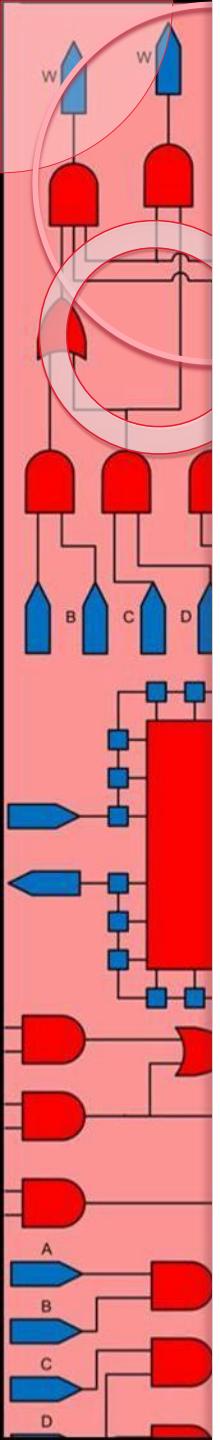
# Iterative logic

- 32-bit ripple carry adder, generate

```
module GenericRippleCarryAdder32(a,b,c0,sum,carry);
    parameter BIT = 32;
    input [BIT-1:0] a, b;
    input c0 ;
    output [BIT-1:0] sum;
    output carry;
    wire [BIT-1:0] c;
    FullAdder FA0(a[0],b[0],c0 ,sum[0],c[0]);
    genvar i ;
    generate
        for(i = 1; i < BIT; i = i+1)
            FullAdder FA1(a[i],b[i],c[i-1],sum[i],c[i]);
    endgenerate
    assign carry = c[BIT-1];
endmodule
```




# Bussing system

- A three-bus system

```
module bussingSystem (input [7:0] abus, bbus, cbus,  
                      input sa, sb, sc,  
                      output [7:0] ybus );  
  
    assign ybus = sa ? abus : 8'bz;  
    assign ybus = sb ? bbus : 8'bz;  
    assign ybus = sc ? cbus : 8'bz;  
  
endmodule
```


## Using assign statements

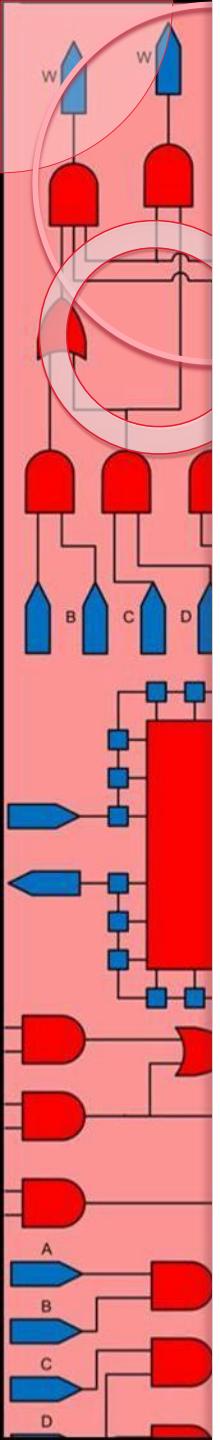
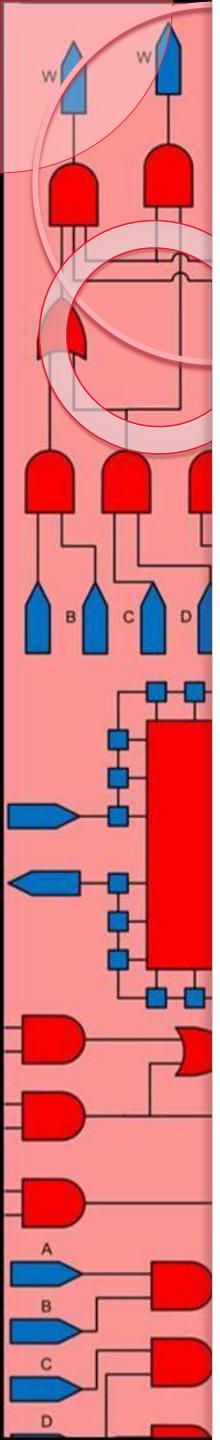
# General logic units


- An ALU with flags

```
module alu_8bit (input [7:0] a, b, input [1:0] f,
                  output gt, zero,
                  output reg [7:0] y );
    always @ ( a, b, f ) begin
        case ( f )
            2'b00 : y = a + b;
            2'b01 : y = a>b ? a : b;
            2'b10 : y = a & b;
            2'b11 : y = a ^ b;
            default: y = 4'b0000;
        endcase
    end
    assign gt = a > b;
    assign zero = (y==8'b0) ? 1'b1 : 1'b0;
endmodule
```


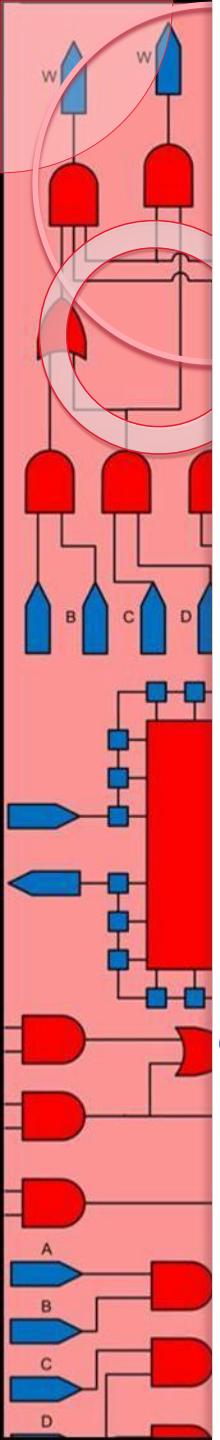
# Summary

- Logic units, arithmetic units, busses
- Random logic
- Iterative hardware
- Bussing system
- General logic units




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog
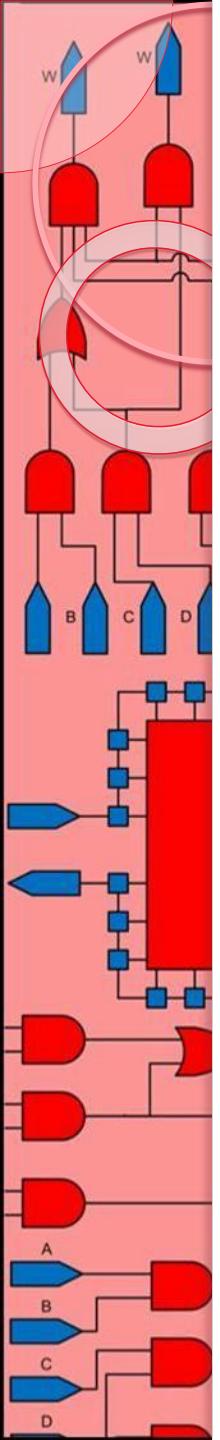
## Lecture 12: Sequential Elements of RTL Design


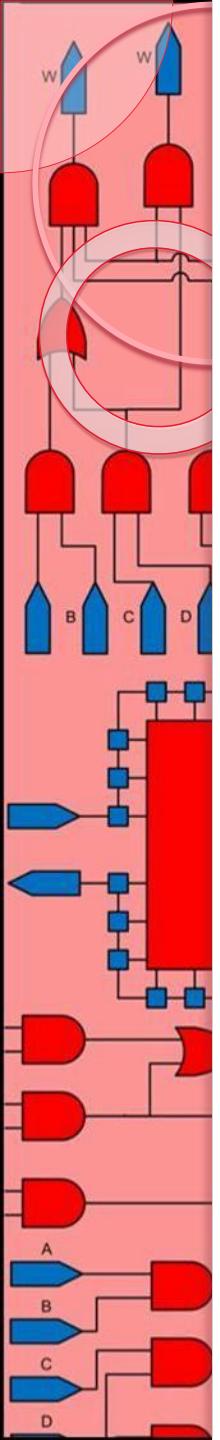
# Sequential Elements of RTL Design

- Registers, Shifters and Counters
  - Registers
  - Shift-Register
  - Counters




# Sequential Elements of RTL Design

- Registers, Shifters and Counters - Registers

```
module register (input [7:0] d, input clk, set, reset,
                  output reg [7:0] q);
    always @ ( posedge clk ) begin
        if ( set )
            #5 q <= 8'b1;
        else if ( reset )
            #5 q <= 8'b0;
        else
            #5 q <= d;
    end
endmodule
```

An 8-bit Register

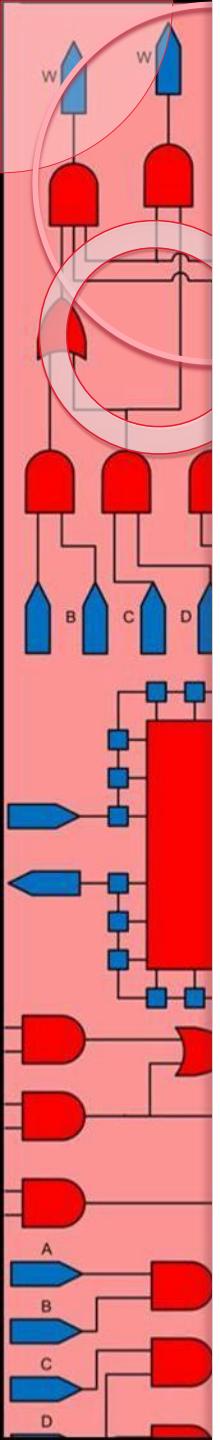


# Sequential Elements of RTL Design

- Registers, Shifters and Counters - Shift-Registers


```
module shift_reg (input [3:0] d, input clk, ld, rst,
                  l_r, s_in, output reg [3:0] q);
    always @ (posedge clk) begin
        if (rst)
            #5 q <= 4'b0000;
        else if (ld)
            #5 q <= d;
        else if (l_r)
            #5 q <= {q[2:0], s_in};
        else
            #5 q <= {s_in, q[3:1]};
    end
endmodule
```


A 4-bit Shift Register

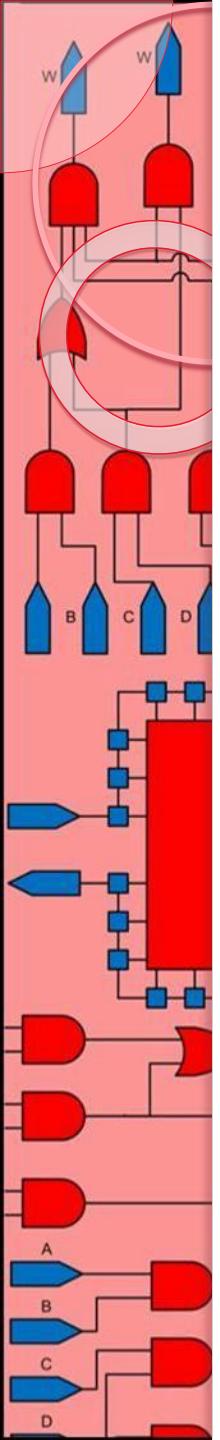
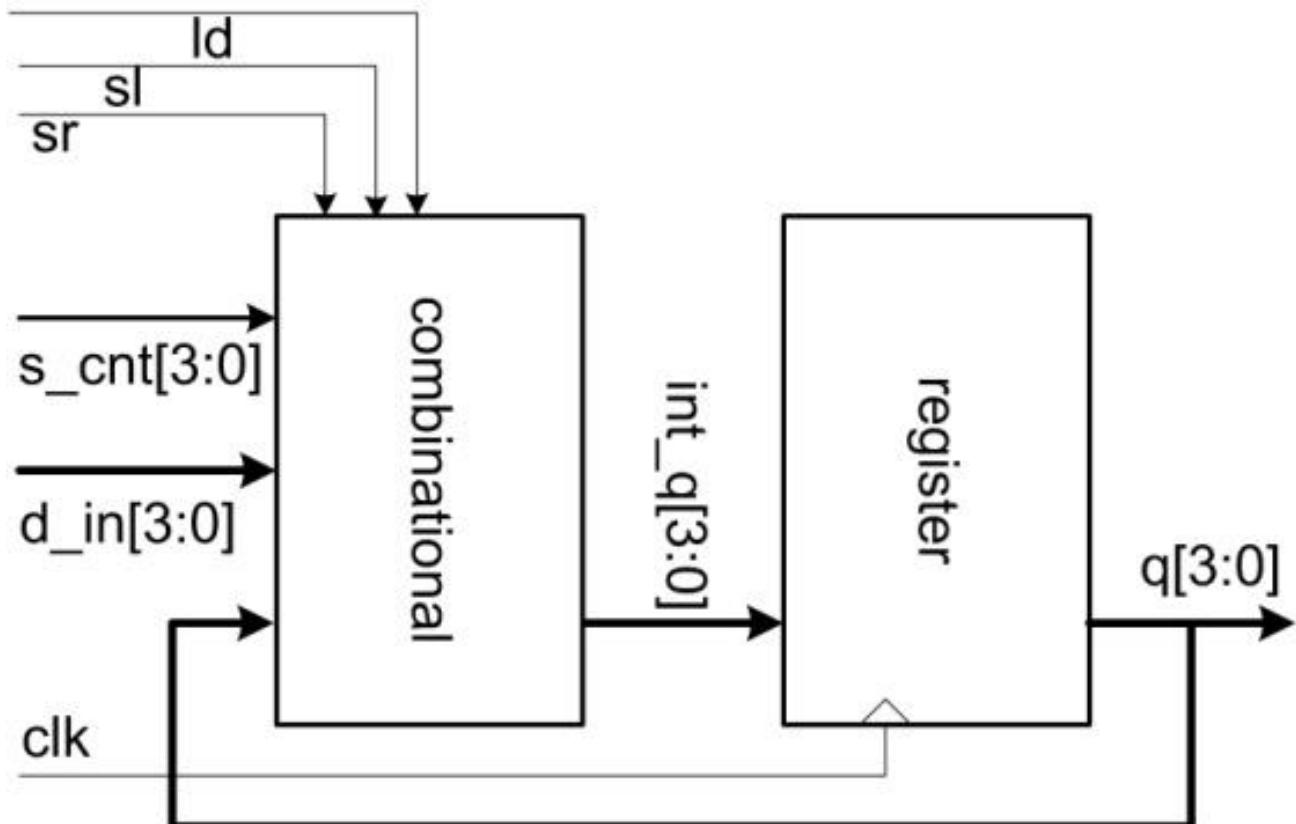
# Sequential Elements of RTL Design

- Registers, Shifters and Counters - Shift-Registers



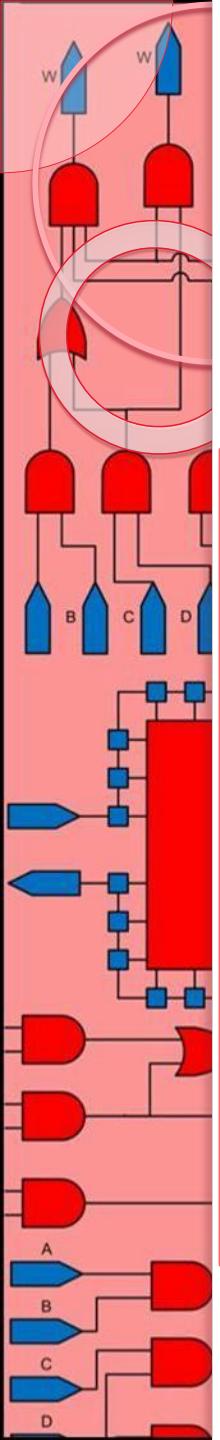


# Sequential Elements of RTL Design

- Registers, Shifters and Counters - Shift-Registers

```
module shift_reg (input [3:0] d_in, input clk, input [1:0]
                  s_cnt, sr, sl, ld, output reg [3:0] q );
  reg [3:0] int_q;
  always @ (d_in, s_cnt, sr, sl, ld, q) begin:combinational
    if ( ld ) int_q = d_in;
    else if ( sr ) int_q = q >> s_cnt;
    else if ( sl ) int_q = q << s_cnt;
    else int_q = q;
  end
  always @ ( posedge clk ) begin:register
    q <= int_q;
  end
endmodule
```
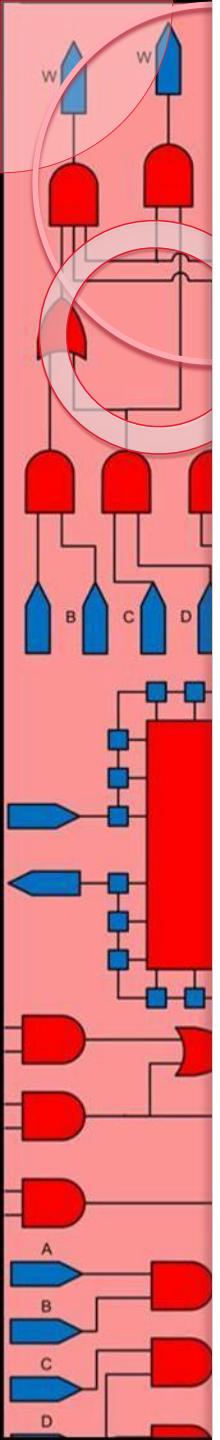
## Shift-Register Using Two Procedural Blocks



# Sequential Elements of RTL Design


- Registers, Shifters and Counters - Counters


```
module counter (input [3:0] d_in, input clk, rst, ld,
                 u_d, output reg [3:0] q );
    always @ ( posedge clk ) begin
        if ( rst )
            q <= 4'b0000;
        else if ( ld )
            q <= d_in;
        else if ( u_d )
            q <= q + 1;
        else
            q <= q - 1;
    end
endmodule
```

An Up-Down Counter

# Sequential Elements of RTL Design


- Synthesis of Shifters and Counters

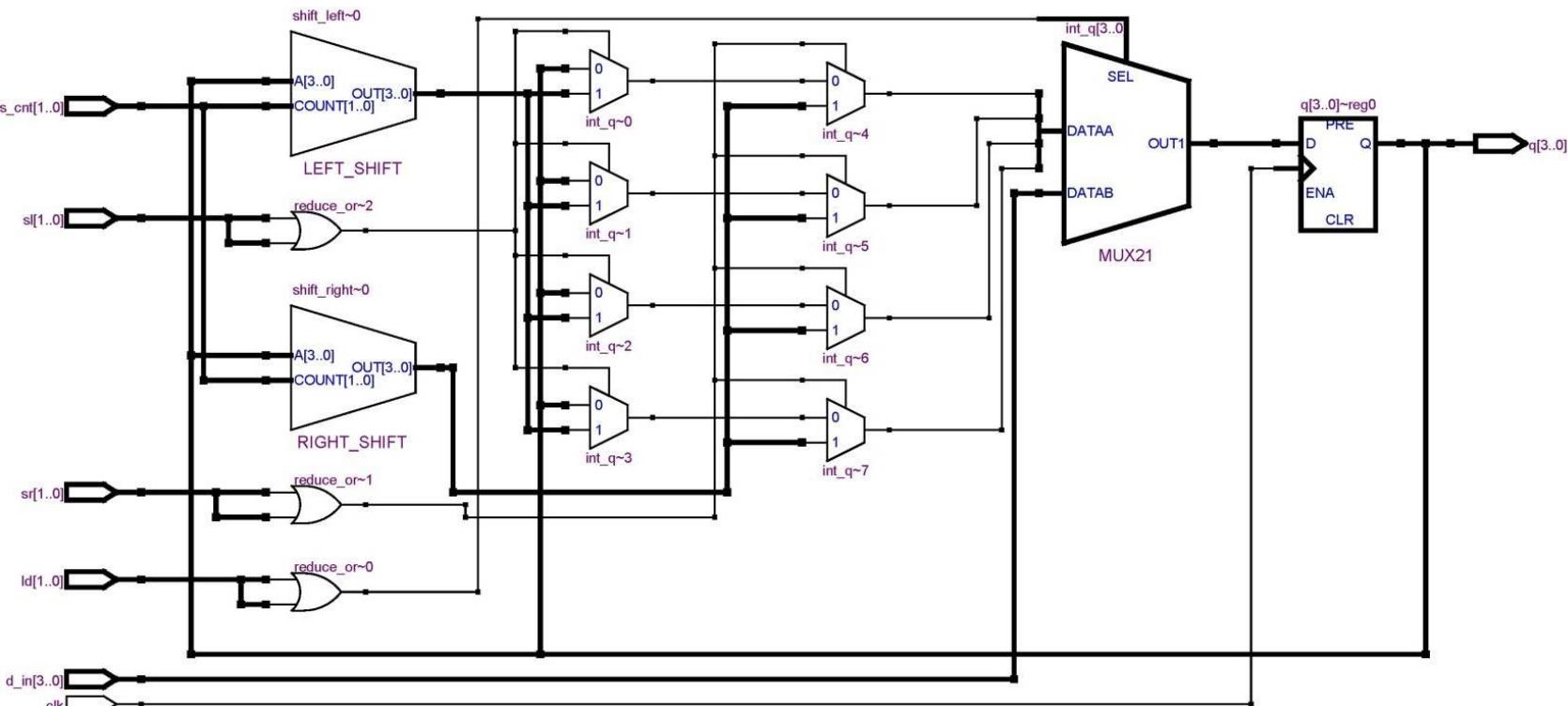

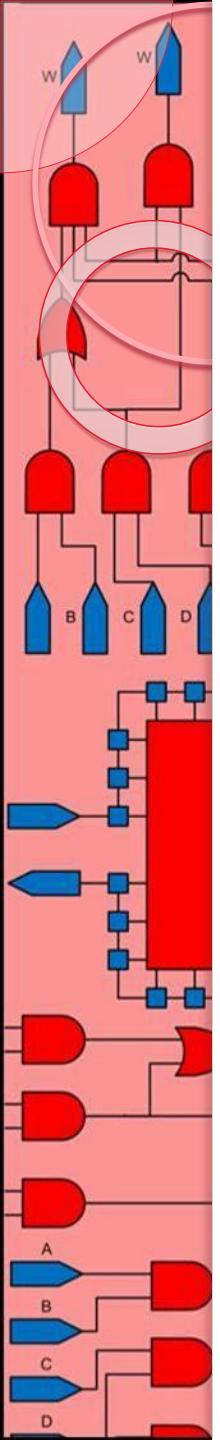
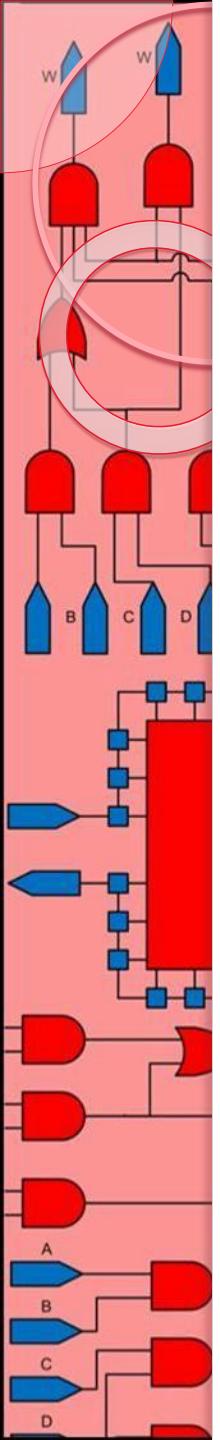
# Summary

- Sequential Elements
- Registers
- Counters
- Shift registers




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog
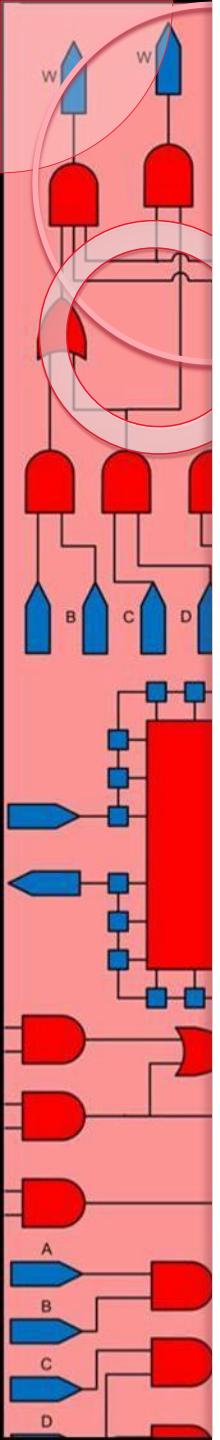
## Lecture 13: State Machines (Controller building blocks)



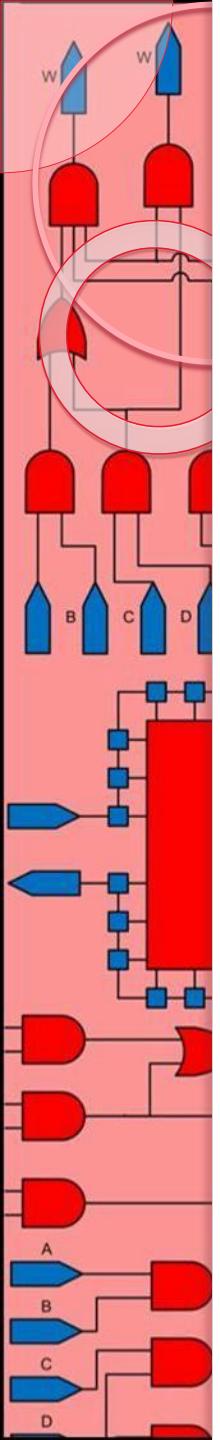
# State Machines


- State Machine Coding
  - Moore Detector
  - A Mealy Machine Example
  - Huffman Coding Style
  - More Complex Outputs



# State Machines

- State Machine Coding

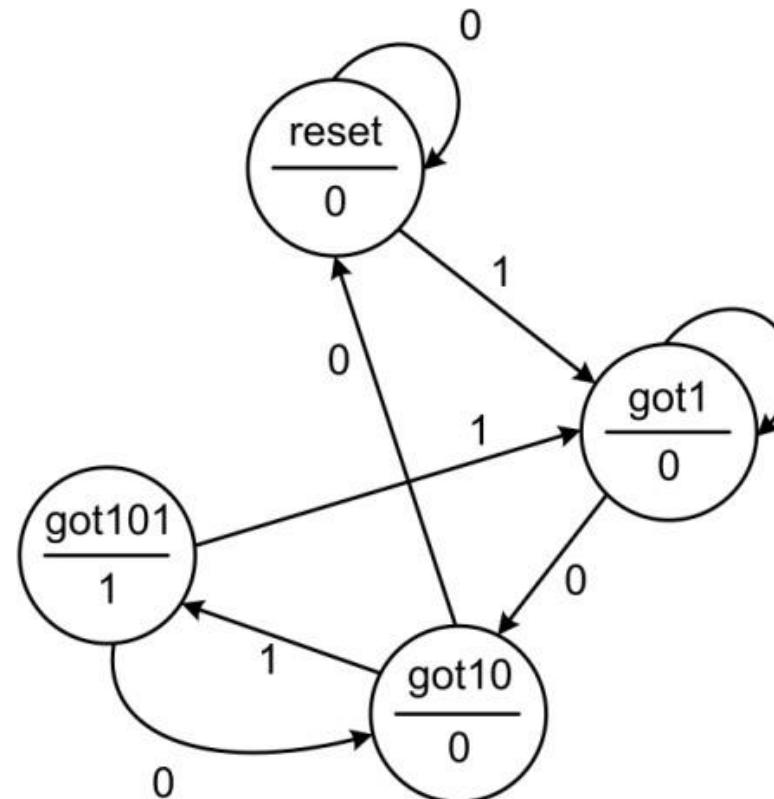

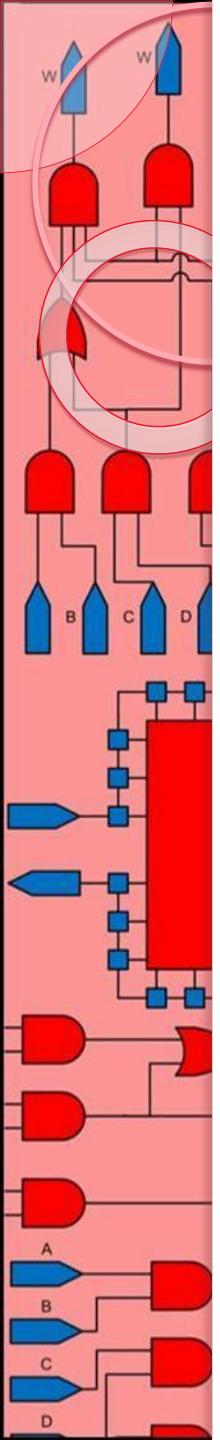


# State Machines

- State Machine Coding - Moore Detector

```
module moore_detector (input x, rst, clk, output z);
parameter [1:0] reset = 0, got1 = 1, got10 = 2, got101 = 3;
reg [1:0] current;
always @ ( posedge clk ) begin
  if ( rst ) begin
    current <= reset;
  end
  else case ( current )
    reset: begin
      if ( x==1'b1 ) current <= got1;
      else current <= reset;
    end
    got1: begin
      if ( x==1'b0 ) current <= got10;
      else current <= got1;
    end
  endcase
end
endmodule
```

Moore Machine Verilog Code . . .

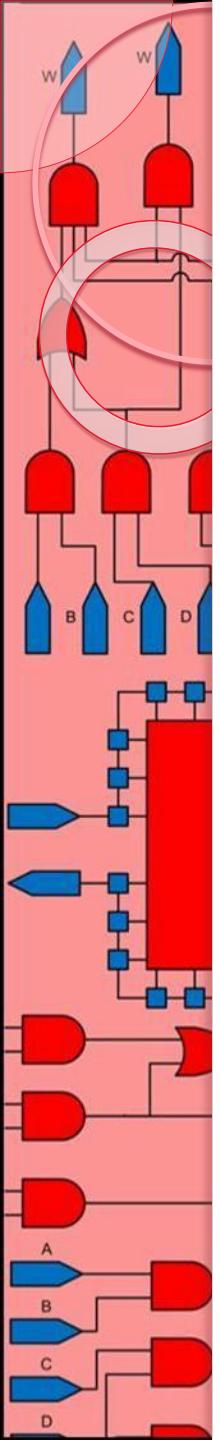


# State Machines

- State Machine Coding - Moore Detector

```
got10: begin
    if ( x==1'b1 ) begin
        current <= got101;
    end else begin
        current <= reset;
    end
end
got101: begin
    if ( x==1'b1 ) current <= got1;
    else current <= got10;
end
default: current <= reset;
endcase
end
assign z = (current == got101) ? 1 : 0;
endmodule
```

... Moore Machine Verilog Code

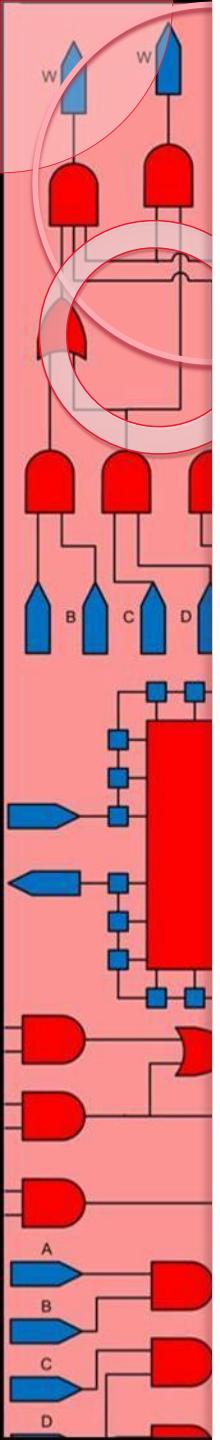

# State Machines


- State Machine Coding
  - Moore Detector


```
case ( current )
    reset: begin . . . end
    got1: begin . . . end
    got10: begin . . . end
    got101: begin . . . end
    default: begin . . . end
endcase
```

## case-Statement Outline
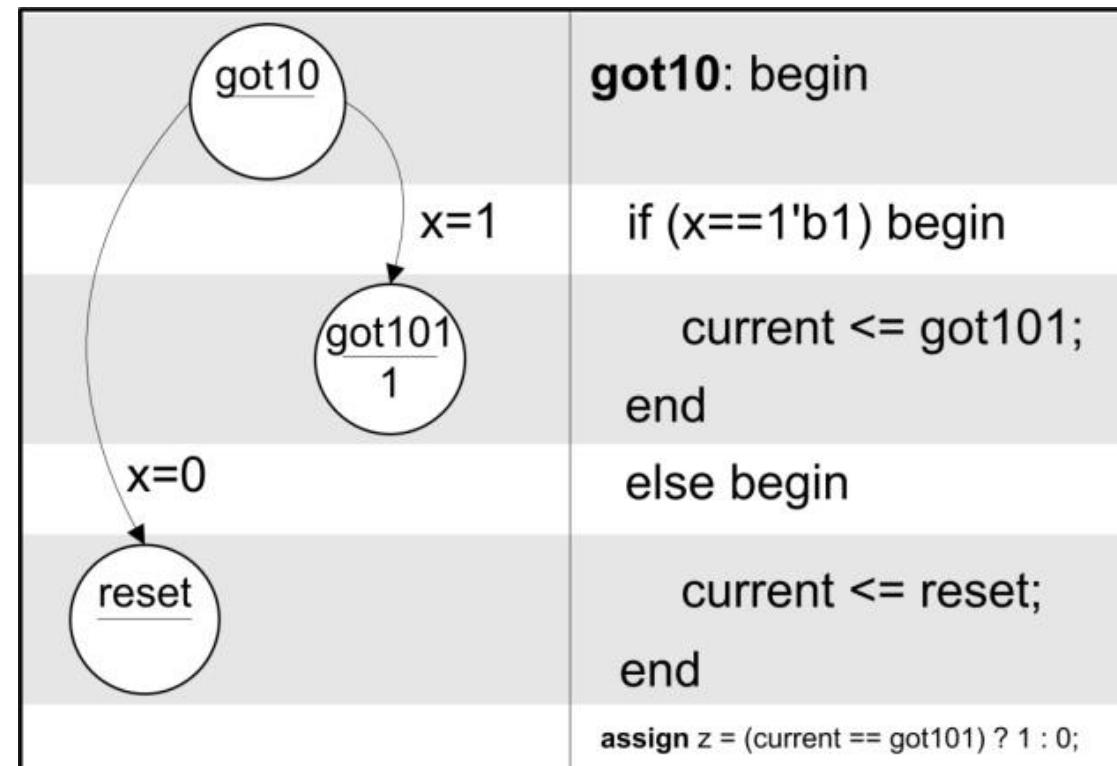
# State Machines


- State Machine Coding
  - Moore Detector




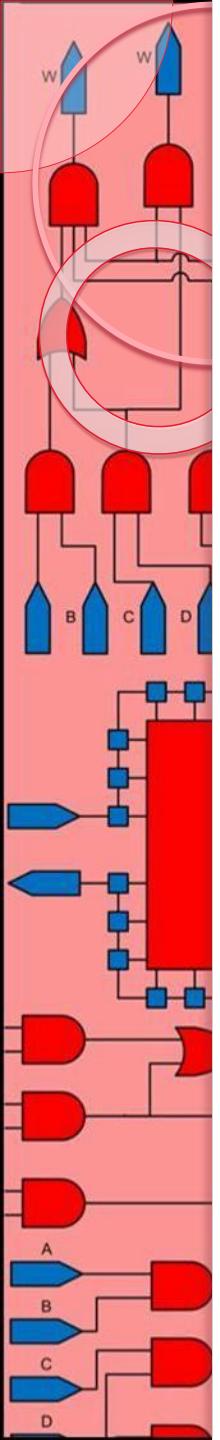
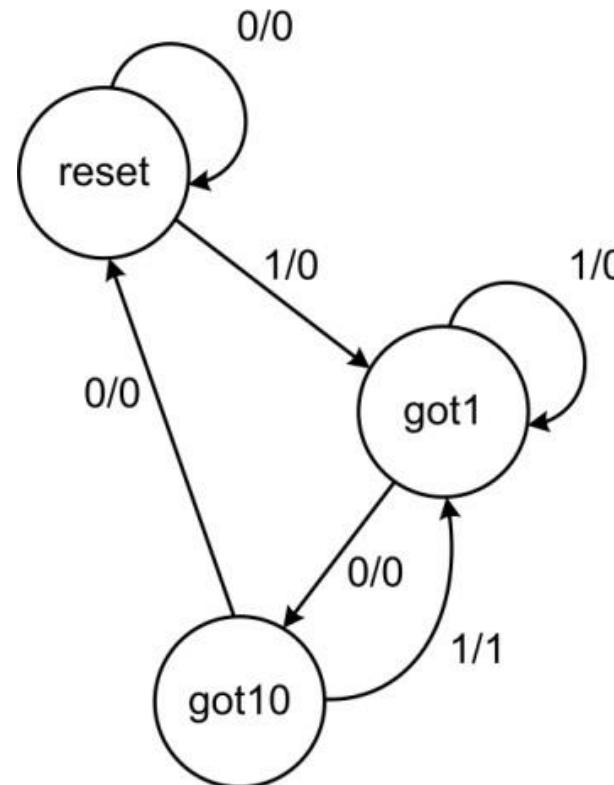
# State Machines

- State Machine Coding
  - A Mealy Machine Example



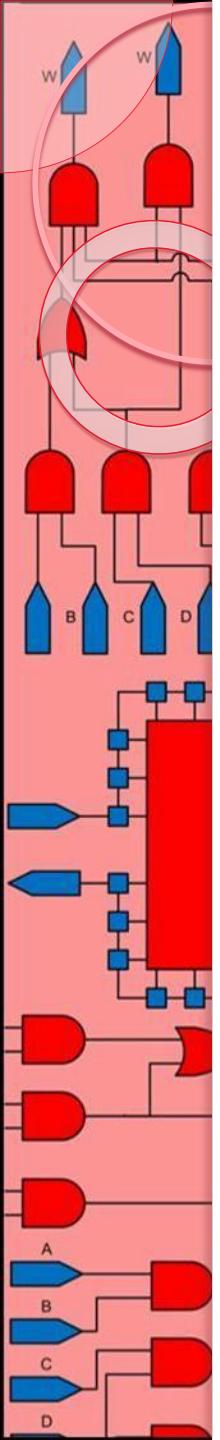


# State Machines

- State Machine Coding - A Mealy Machine Example

```
module mealy_detector ( input x, clk, output z );
parameter [1:0]
    reset      = 0, // 0 = 0 0
    got1       = 1, // 1 = 0 1
    got10      = 2; // 2 = 1 0
reg [1:0] current;
initial current = reset;
always @ ( posedge clk )
begin
    case ( current )
        reset:
            if( x==1'b1 ) current <= got1;
            else current <= reset;
        got1:
            if( x==1'b0 ) current <= got10;
            else current <= got1;
end
endmodule
```

Verilog Code of 101 Mealy Detector . . .

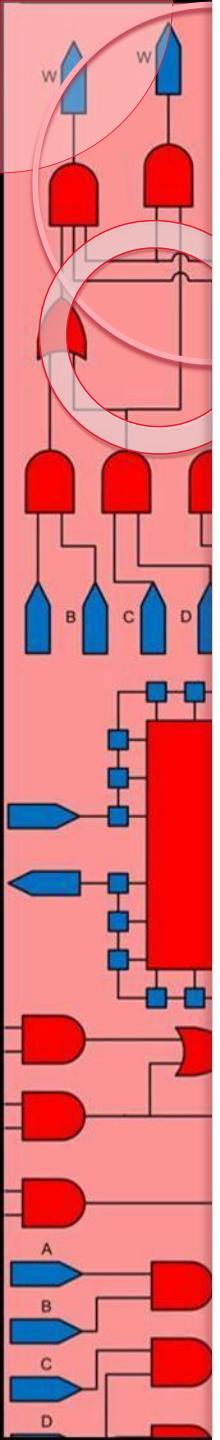

# State Machines


- State Machine Coding - A Mealy Machine Example

```
got10:  
    if( x==1'b1 ) current <= got1;  
    else current <= reset;  
    default: current <= reset;  
    endcase  
end  
assign z= ( current==got10 && x==1'b1 ) ? 1'b1 : 1'b0;  
endmodule
```

... Verilog Code of 101 Mealy Detector

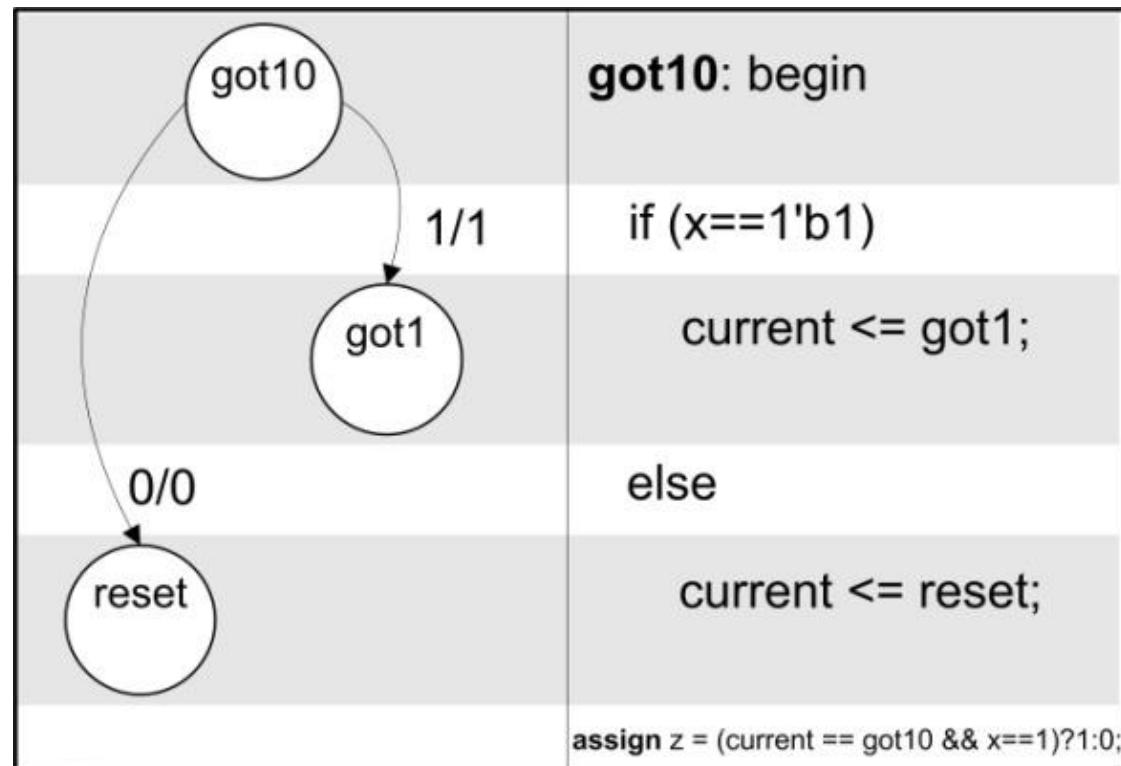
# State Machines


- State Machine Coding
  - Huffman Coding Style


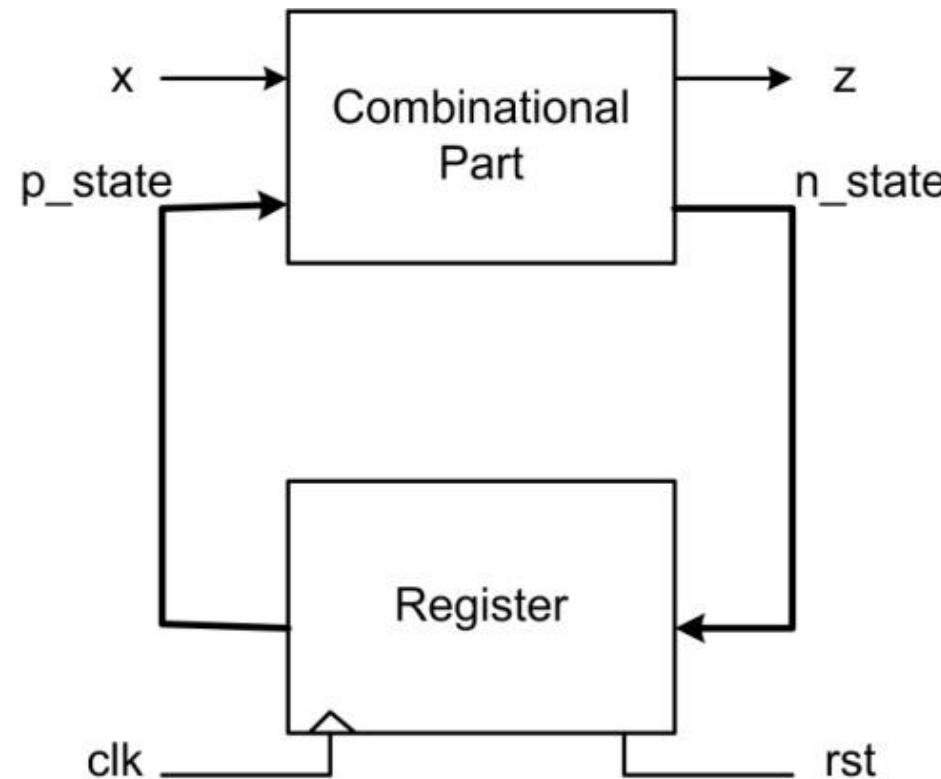
# State Machines

- State Machine Coding
  - Huffman Coding Style



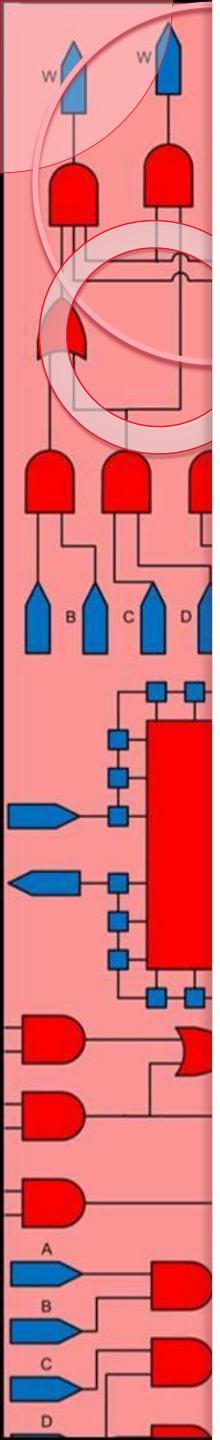


# State Machines

- State Machine Coding - More Complex Outputs

```
module moore_detector ( input x, rst, clk, output z );
    parameter [1:0] reset = 2'b00, got1 = 2'b01,
                    got10 = 2'b10, got101 = 2'b11;
    reg [1:0] p_state, n_state;

    always @ ( p_state or x ) begin : combinational
        n_state = 0;
        case ( p_state )
            reset: begin
                if( x==1'b1 ) n_state = got1;
                else n_state = reset;
            end
            got1: begin
                if( x==1'b0 ) n_state = got10;
                else n_state = got1;
            end
    end
```

Verilog Huffman Coding Style . . .

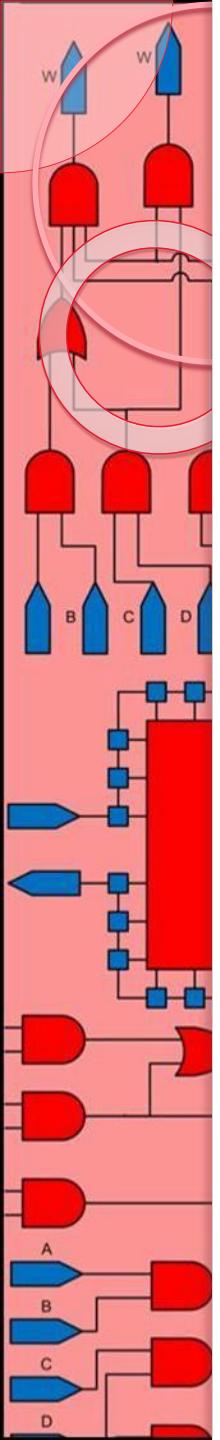


# State Machines

- State Machine Coding - More Complex Outputs

```
got101: begin
    if( x==1'b1 ) n_state = got1;
    else n_state = got10;
end
default: n_state = reset;
endcase
end
```

... Verilog Huffman Coding Style ...

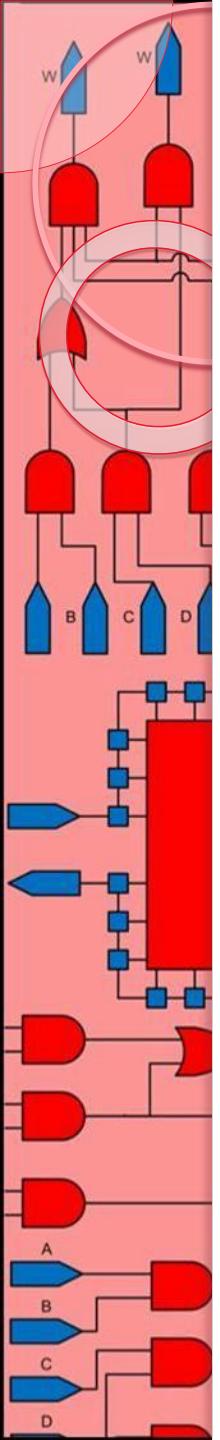

# State Machines


- State Machine Coding - More Complex Outputs

```
always @( posedge clk ) begin : register
    if( rst ) p_state = reset;
    else p_state = n_state;
end

assign z = (current == got101) ? 1 : 0;

endmodule
```

... Verilog Huffman Coding Style

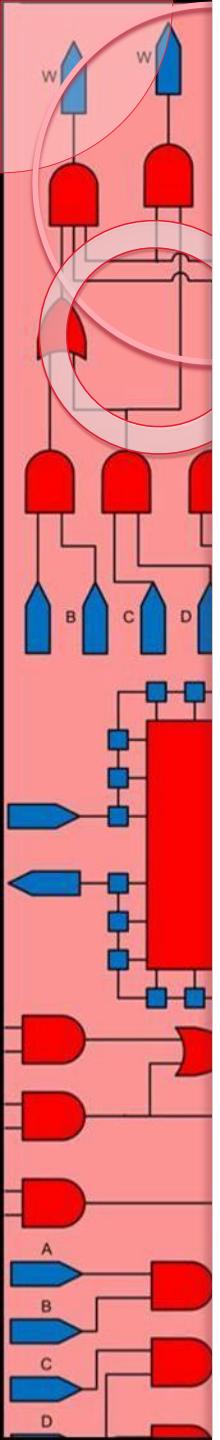


# State Machines

- State Machine Coding - More Complex Outputs

```
module mealy_detector ( input x, en, clk, rst, output reg z );
    parameter [1:0] reset = 0,
                    got1 = 1, got10 = 2, got11 = 3;
    reg [1:0] p_state, n_state;

    always @( p_state or x ) begin : Transitions
        . .
    end
    always @( p_state or x ) begin: Outputting
        . .
    end
    always @ ( posedge clk ) begin: Registering
        . .
    end
endmodule
```

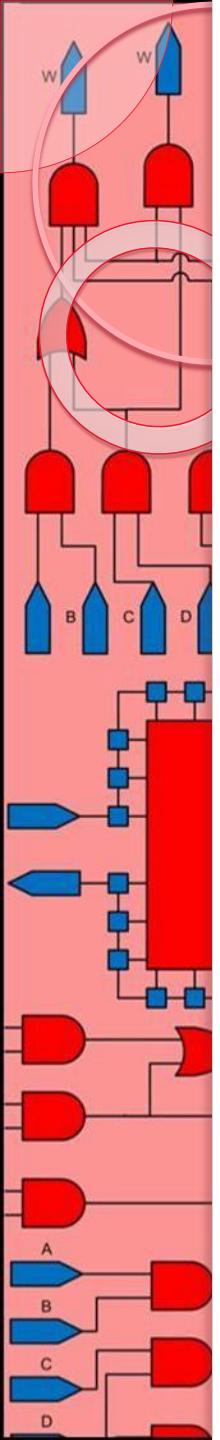Separate Transition and Output Blocks . . .




# State Machines

- State Machine Coding - More Complex Outputs

```
always @( p_state or x ) begin : Transitions
    n_state = reset;
    case ( p_state )
        reset:
            if ( x == 1'b1 ) n_state = got1;
            else n_state = reset;
        got1:
            if ( x == 1'b0 ) n_state = got10;
            else n_state = got11;
        got10:
            if ( x == 1'b1 ) n_state = got1;
            else n_state = reset;
        got11:
            if ( x == 1'b1 ) n_state = got11;
            else n_state = got10;
        default: n_state = reset;
    endcase
end
```

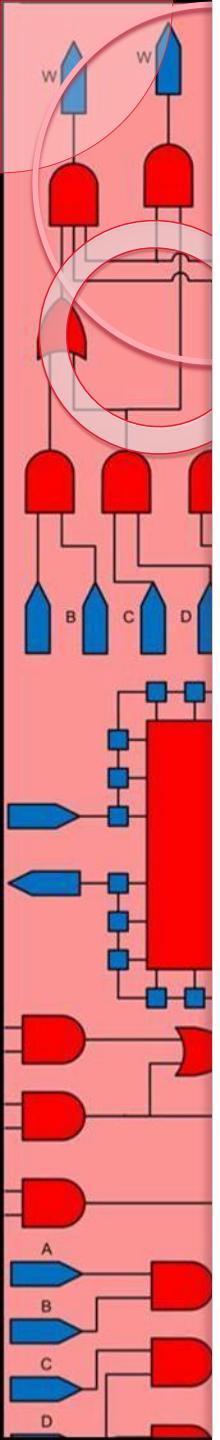... Separate Transition and Output Blocks ...




# State Machines

- State Machine Coding - More Complex Outputs

```
always @( p_state or x ) begin: Outputting
    z = 0;
    case ( p_state )
        reset: z = 1'b0;
        got1: z = 1'b0;
        got10: if ( x == 1'b1 ) z = 1'b1;
            else z = 1'b0;
        got11: if ( x==1'b1 ) z = 1'b0;
            else z = 1'b1;
        default: z = 1'b0;
    endcase
end
```

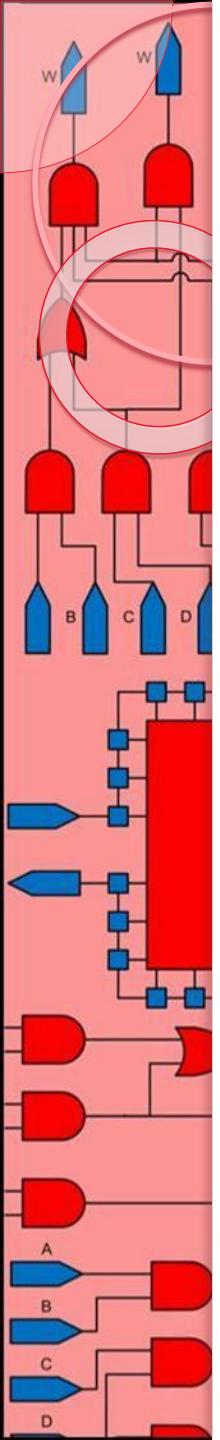... Separate Transition and Output Blocks ...



# State Machines


- State Machine Coding - More Complex Outputs


```
always @ ( posedge clk ) begin: Registering
    if( rst ) p_state <= reset;
    else if( en ) p_state <= n_state;
end
```

... Separate Transition and Output Blocks

# State Machines


- State Machine Synthesis

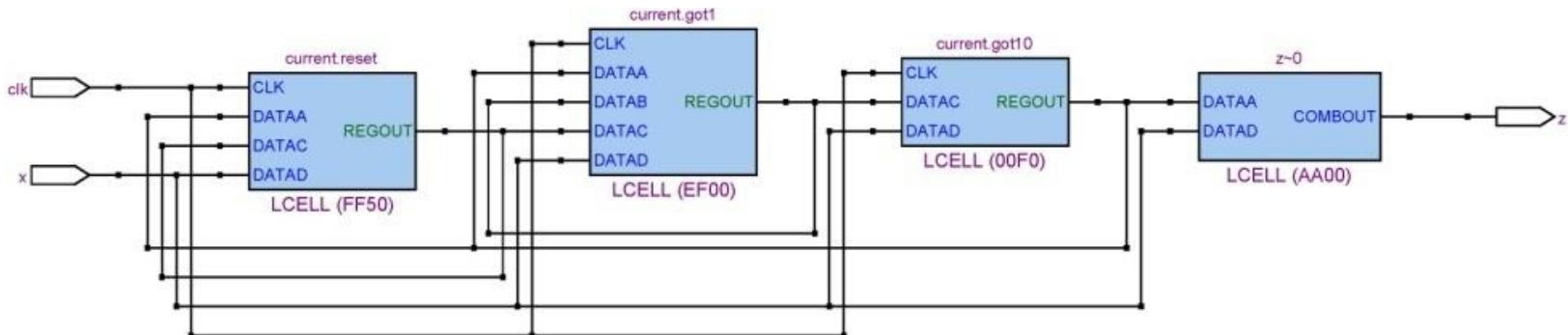

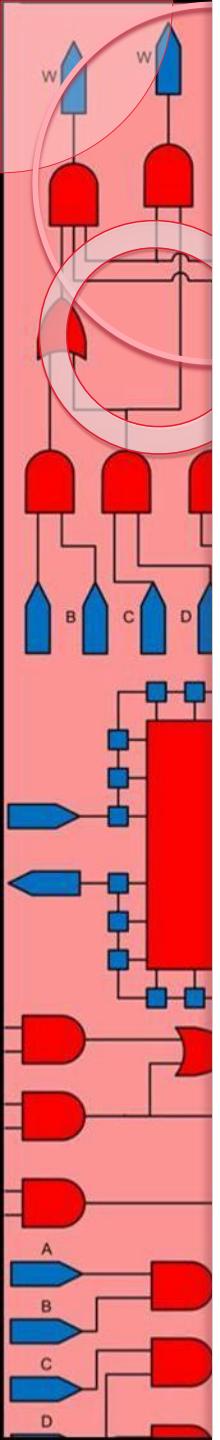
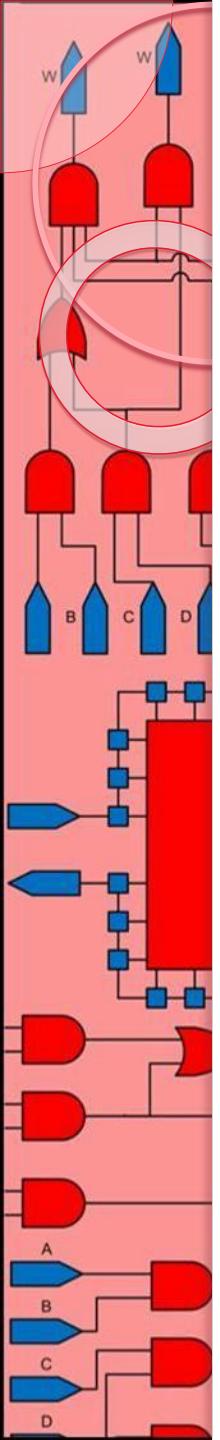
# Summary

- State Machine Coding
  - Moore Detector
  - A Mealy Machine Example
  - Huffman Coding Style
  - More Complex Outputs




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog
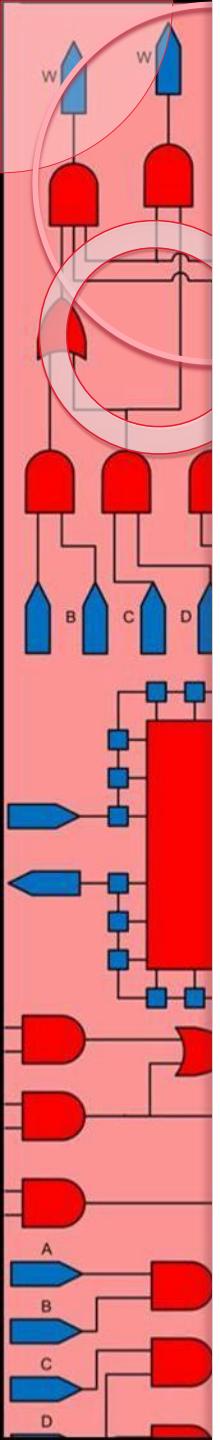
## Lecture 14: Memories (Used in RTL Datapath)


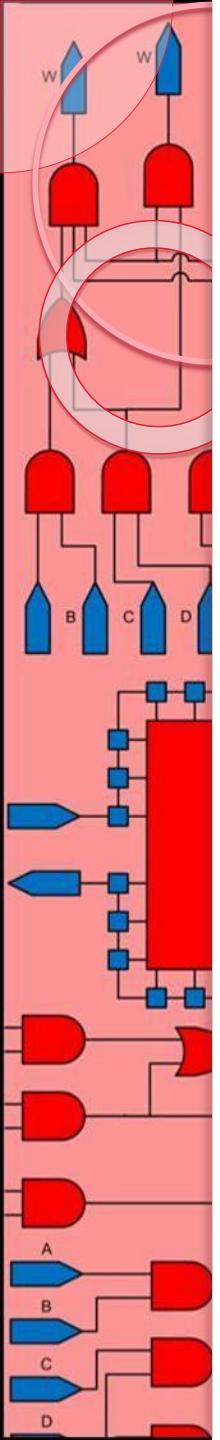
# Memories

- Memory declaration
- Memory part selection
- Memory module
- Summary




# Memories

- Memory declaration

```
reg [7:0] a_array [0:1023][0:511];
```

```
reg [7:0] Areg;                      // An 8-bit vector
reg Amem [7:0];                     // A memory of 8 1-bit elements
reg Dmem [7:0][0:3];                // 2-Dim mem, 1-bit elements
reg [7:0] Cmem [0:3];                // A memory of four 8-bit words
reg [2:0] Dmem [0:3][0:4];          // 2-Dim mem, 3-bit elements
reg [7:0] Emem [0:1023];            // A memory of 1024 8-bit words
```

## Array Declaration Examples

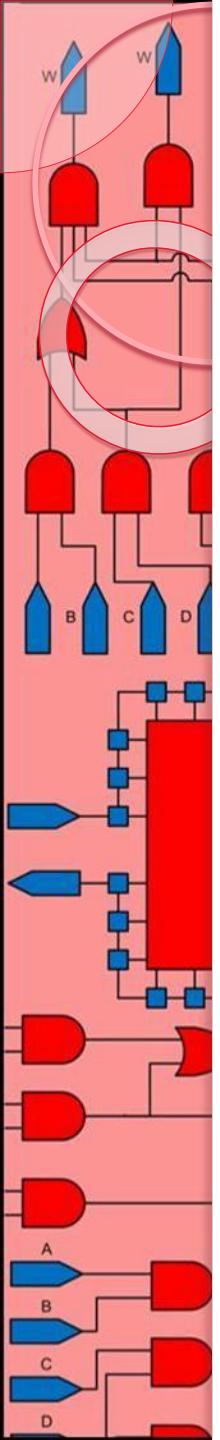

# Memories

- Memory part selection
  - Array Indexing


```
Areg [5:3] selects bits 5, 4, and 3
```

```
Areg [5:-4] selects bits 5, 4, 3, and 2
```

```
Areg [2+:4] selects bits 5, 4, 3, and 2
```

```
Cmem [Areg[7:6]] // extracts Cmem word  
// addressed by Areg[7:6]
```
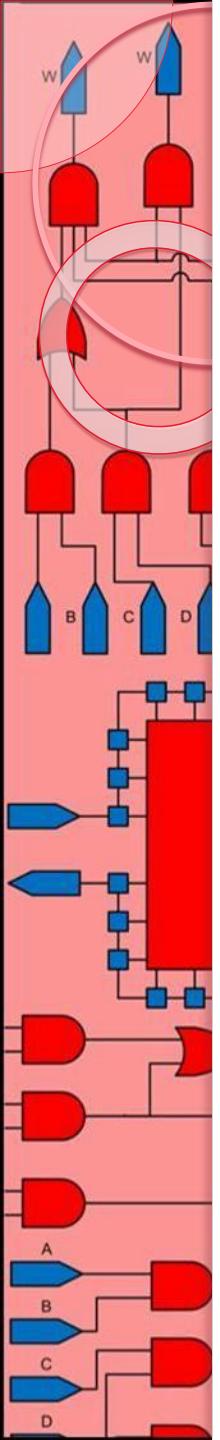
```
Emem [Emem[0]] // extracts Emem word  
// addressed by Emem[0]
```



# Memories


- Memory part selection
  - Array Indexing

```
Emem [355] [3:0] // 4 LSB of location 355
```

```
Emem [355] [3:-4] // 4 bits starting from 3, down
```

```
Emem [355:358] // Illegal.  
// This is not a 4-word block
```
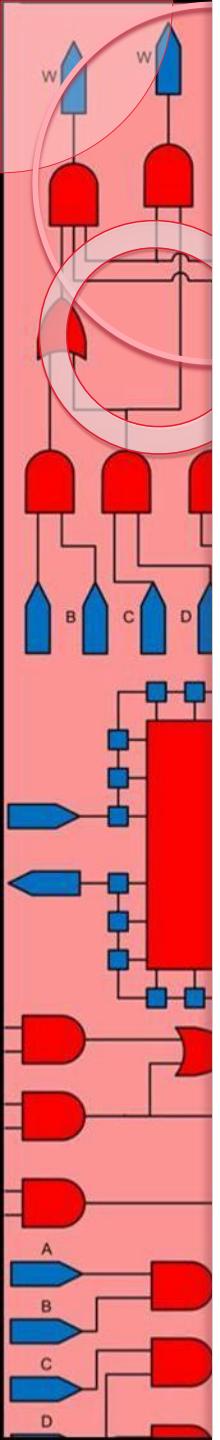
```
Dmem [0] [2] 58] // Illegal.  
// This is not a 4-word block
```




# Memories

- Memory module
  - Standard clocked register file


```
module memory (input [7:0] inbus,
                output [7:0] outbus,
                input [9:0] addr, input clk, rw);
    reg [7:0] mem [0:1023];
    assign outbus = rw ? mem [addr] : 8'bz;
    always @ (posedge clk)
        if (rw == 0) mem [addr] = inbus;
endmodule
```

## Memory Description

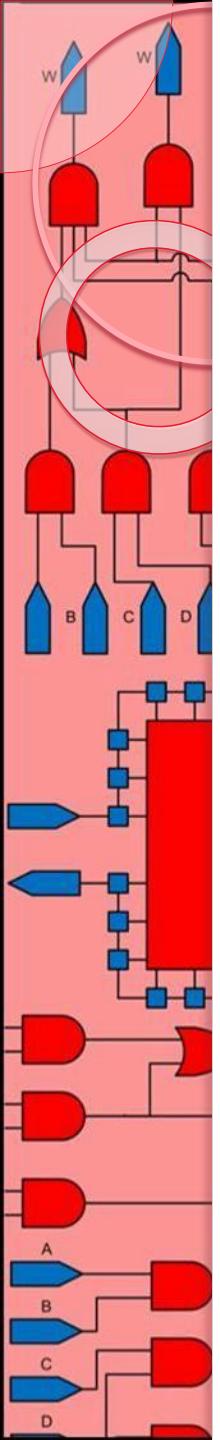
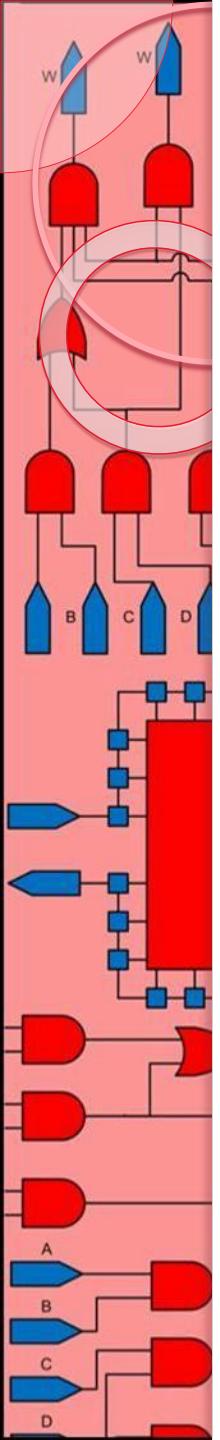
# Summary

- Memory declaration
- Memory part selection
- Memory module
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 15: Writing Testbenches

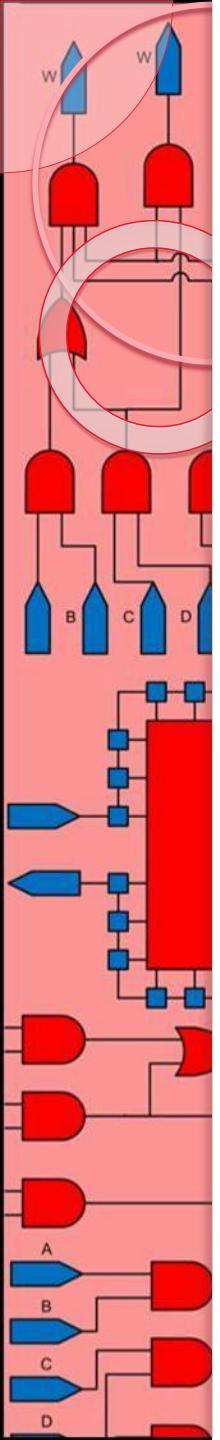
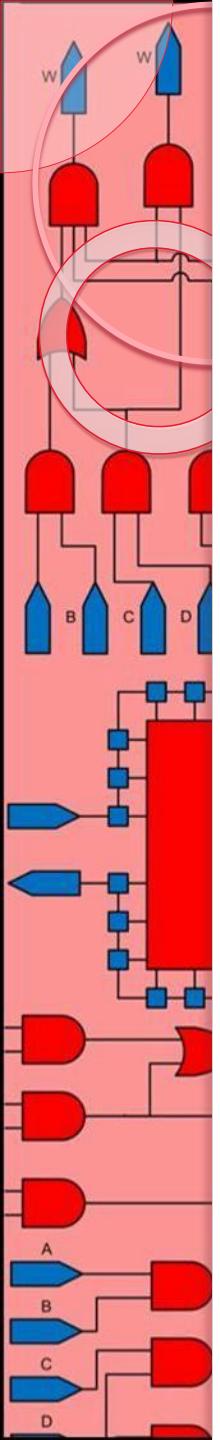
# Writing Testbenches

- Periodic data
- Random data
- Timed data
- Summary




# Writing Testbenches

- Generating Periodic Data
- Random Input Data
- Timed Data

```
module moore_detector ( input x, rst, clk, output z );
    parameter [1:0] a=0, b=1, c=2, d=3;
    reg [1:0] current;
    always @(posedge clk)
        if (rst)      current = a;
        else case (current)
            a : current <= x ? b : a ;
            b : current <= x ? b : c ;
            c : current <= x ? d : a ;
            d : current <= x ? b : c ;
            default : current <= a;
        endcase
        assign z = (current==d) ? 1'b1 : 1'b0;
endmodule
```

Circuit Under Test

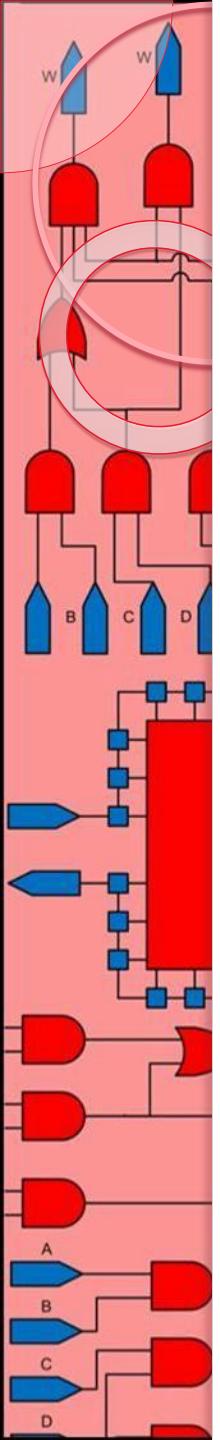


# Writing Testbenches

- Generating Periodic Data

```
`timescale 1 ns / 100 ps
module test_moore_detector;
    reg x, reset, clock;
    wire z;

    moore_detector uut ( x, reset, clock, z );
    initial begin
        clock=1'b0; x=1'b0; reset=1'b1;
    end
    initial #24 reset=1'b0;
    always #5 clock=~clock;
    always #7 x=~x;
endmodule
```

## Generating Periodic Data

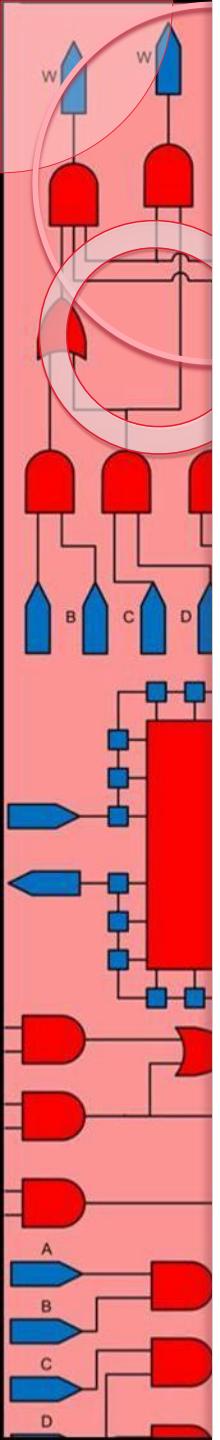


# Writing Testbenches

- Random Input Data

```
`timescale 1 ns / 100 ps

module TESTER_test_moore_detector;
    reg x, reset, clock;
    wire z;
    moore_detector uut( x, reset, clock, z );
    initial begin
        clock=1'b0; x=1'b0; reset=1'b1;
        #24 reset=1'b0;
    end
    initial #165 $finish;
    always #5 clock=~clock;
    always #7 x=$random;
endmodule
```

## Random Data Generation

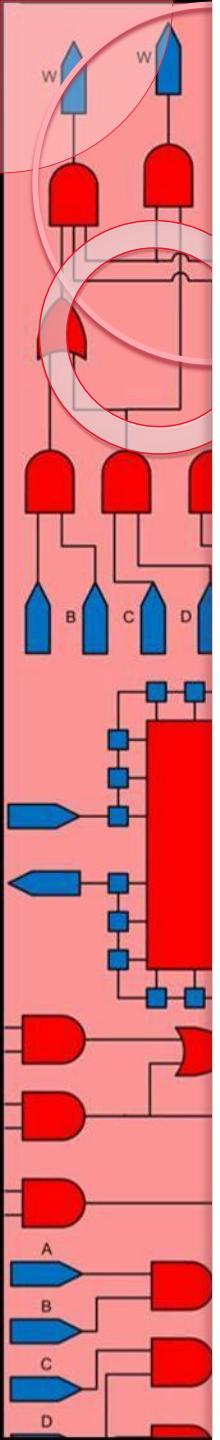


# Writing Testbenches

- Timed Data


```
`timescale 1ns/100ps
module test_moore_detector;
    reg x, reset, clock;
    wire z;
    moore_detector uut( x, reset, clock, z );
    initial begin
        clock=1'b0; x=1'b0; reset=1'b1;
        #24 reset=1'b0;
    end
    always #5 clock=~clock;
    initial begin
        #7 x=1;           #5 x=0;           #18 x=1;
        #21 x=0;          #11 x=1;          #13 x=0;
        #33 $stop;
    end
endmodule
```

## Timed Test Data Generation

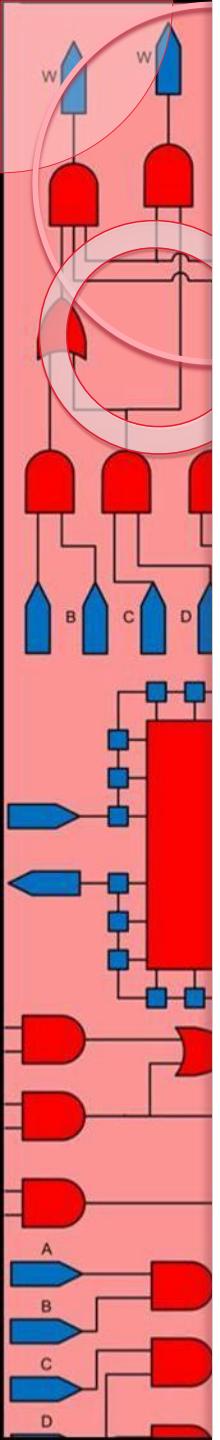
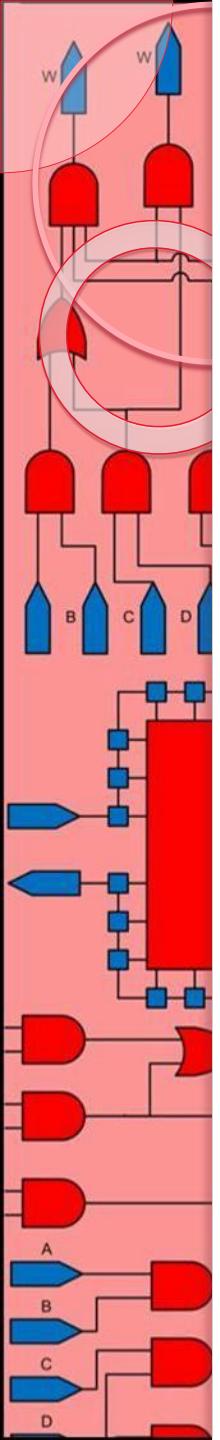
# Summary

- Periodic data
- Random data
- Timed data
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog


## Lecture 16 : RTL Methodology

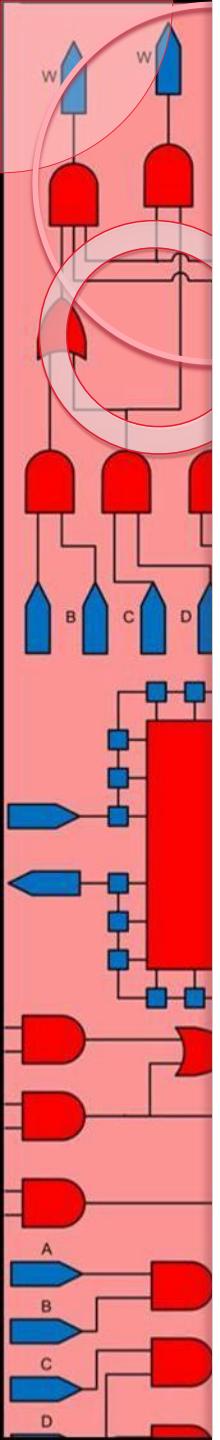


# RTL Methodology

- Transistors to processing elements
- RTL design partitioning
- Example: serial adder
- Summary


# Transistors Level Design

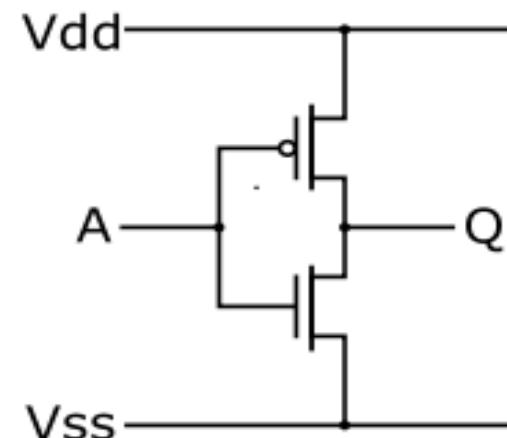


System Level

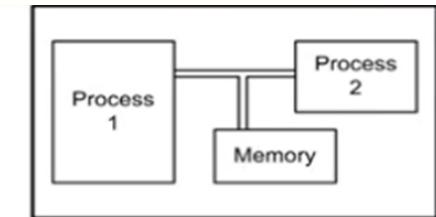

RT Level

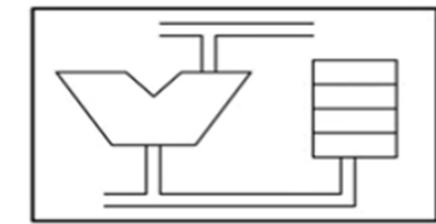



Gate Level

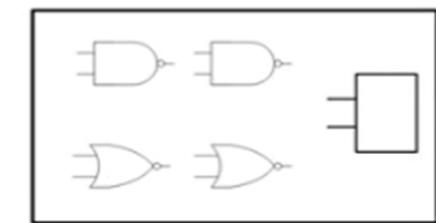


Transistor Level




# Gate Level Design

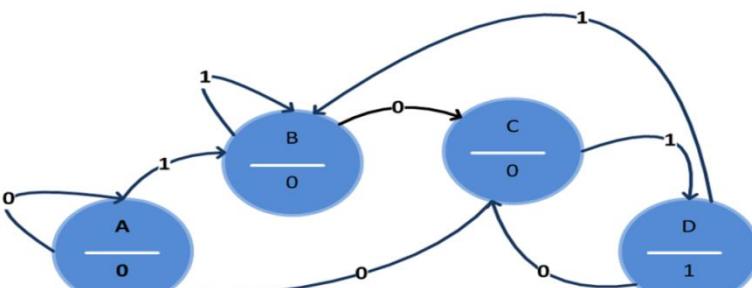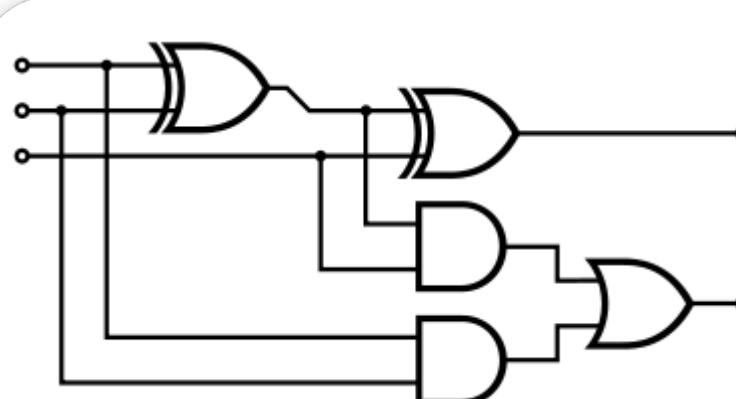


System Level

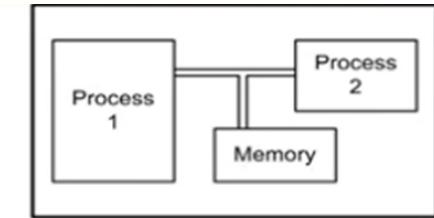


RT Level

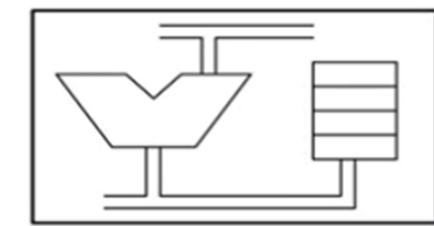



Gate Level

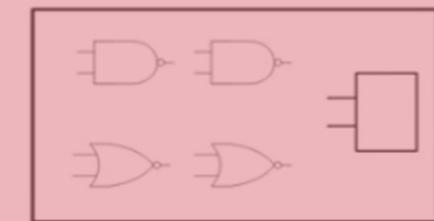

Transistor Level


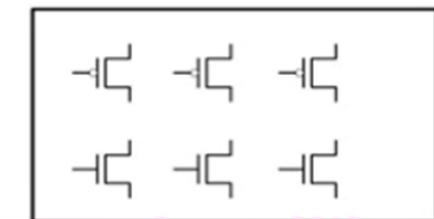


# RT Level Design

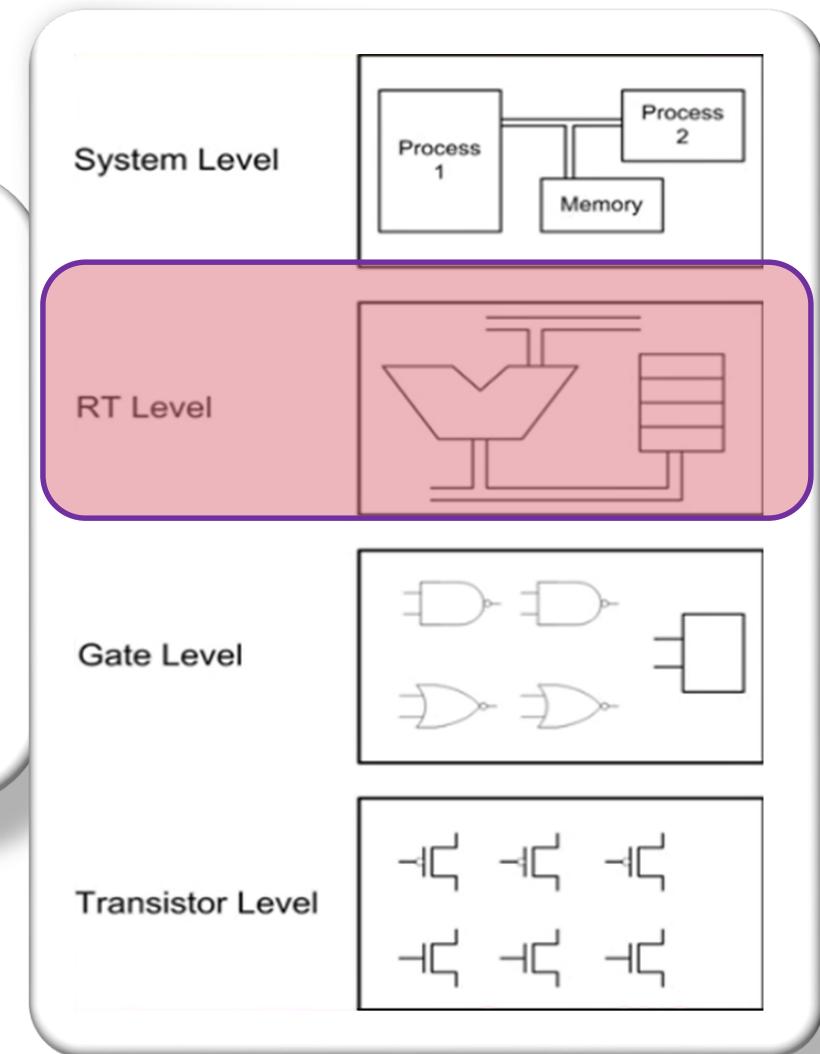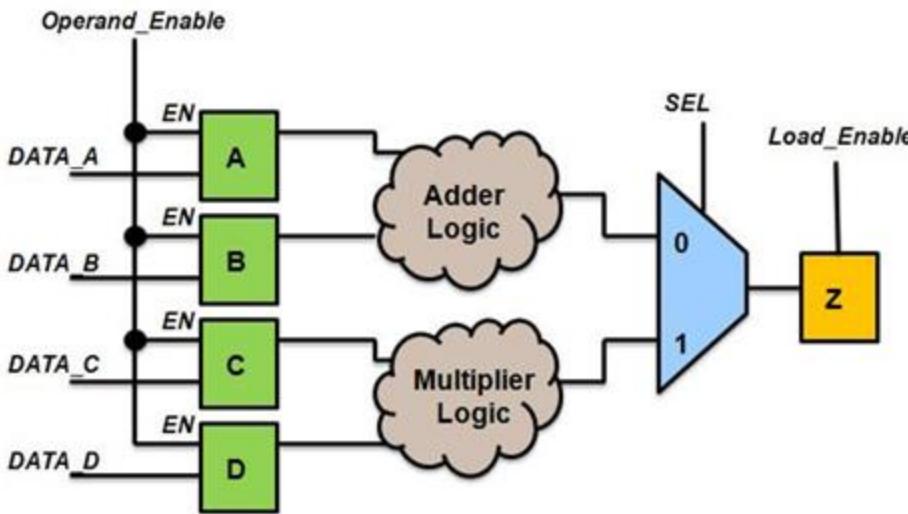

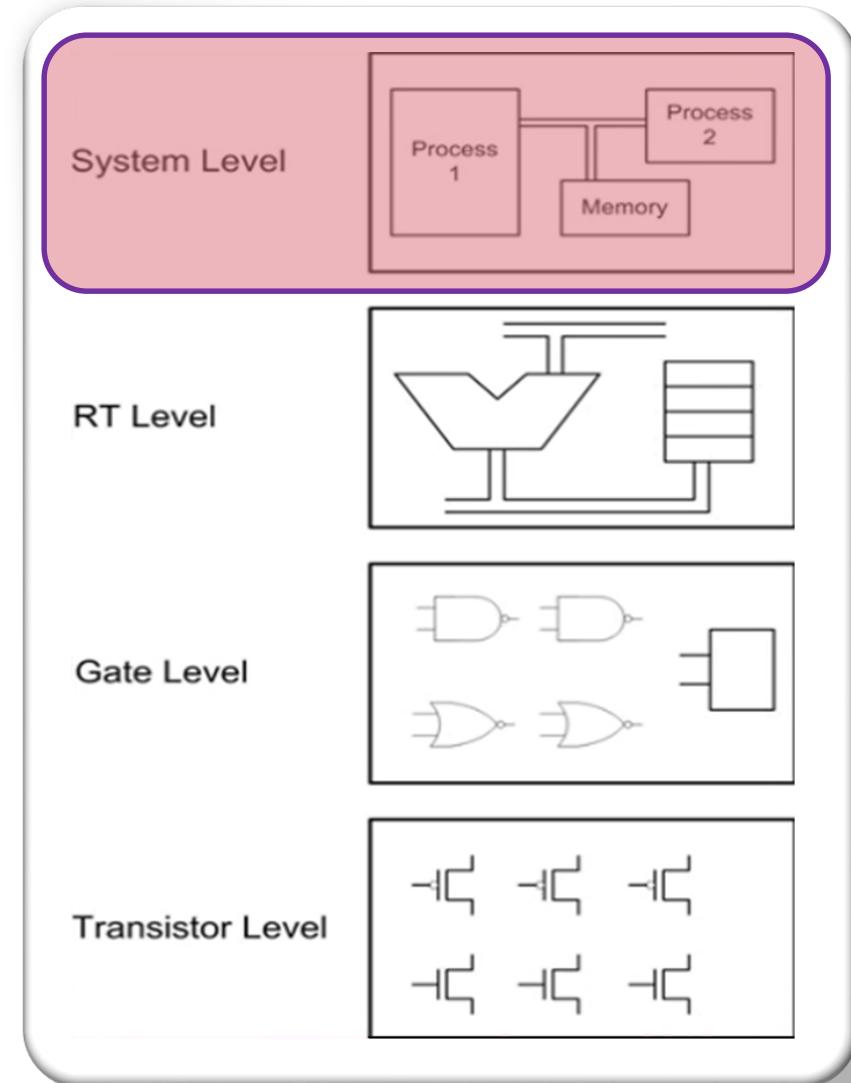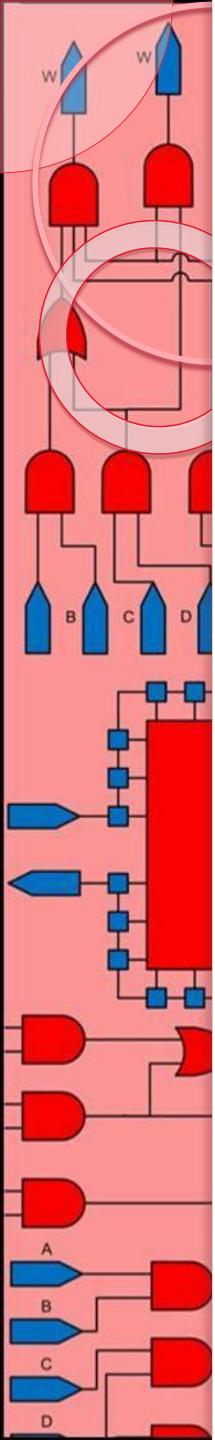
# System Level Design

Connecting CPU's, memories,  
etc. together via channel  
interconnections




# Datapath And Controller

## RTL Design

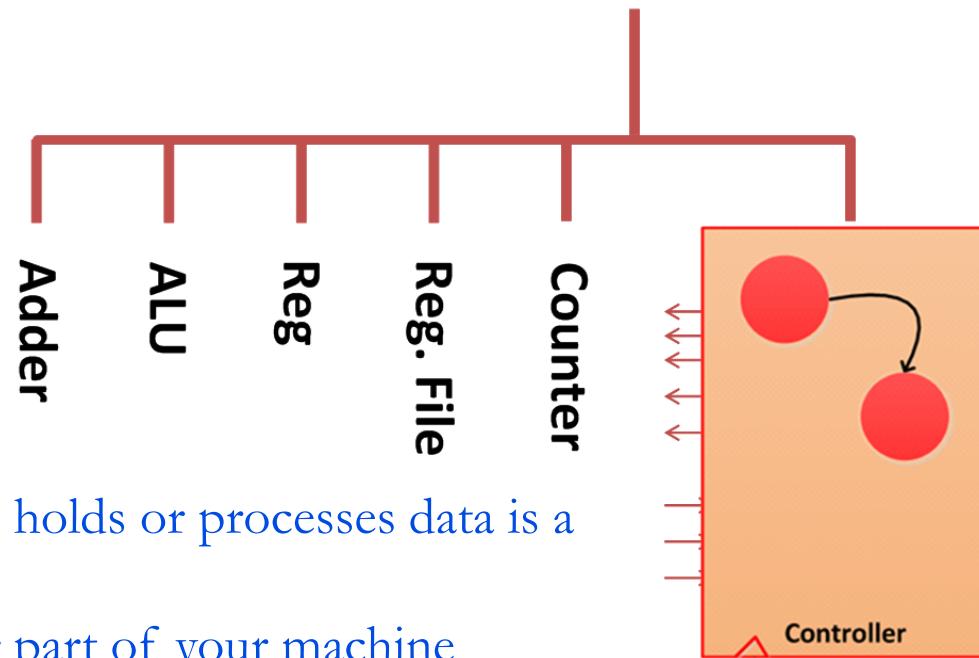


- Any element that passes, holds or processes data is a datapath element
- Controller is the thinking part of your machine
- You should decide how to wire datapath elements
- When designing datapath, don't be concern about how control signals are Issued

# RTL Datapath Example

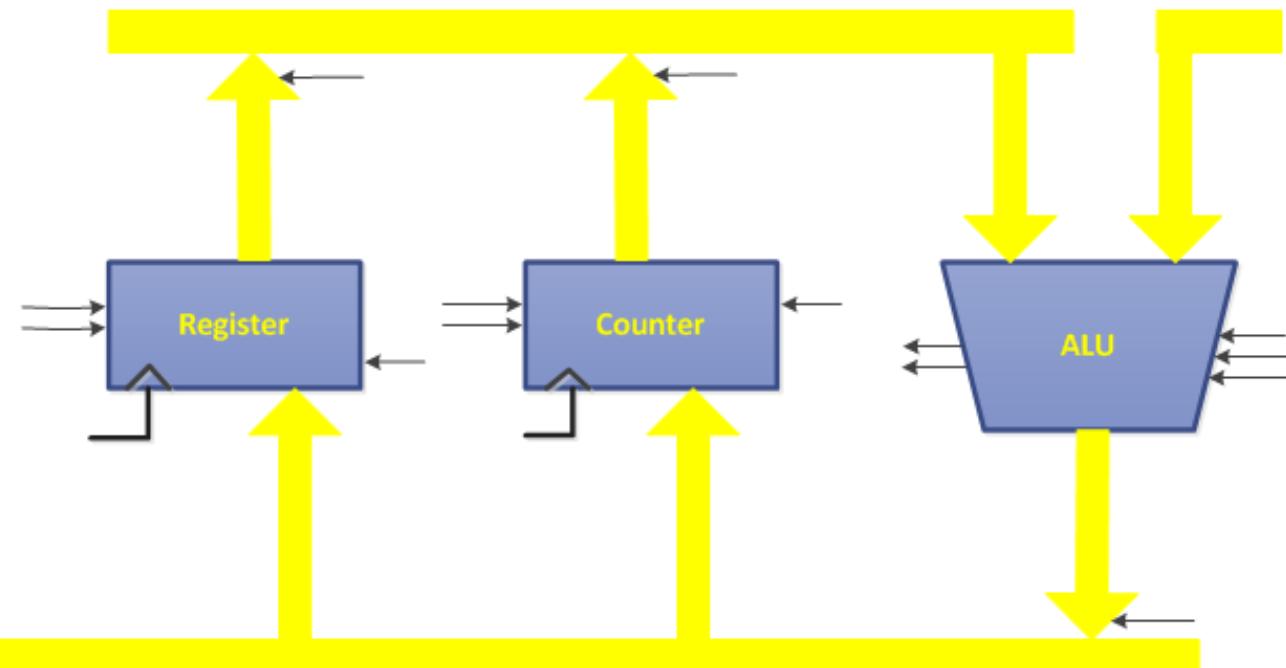

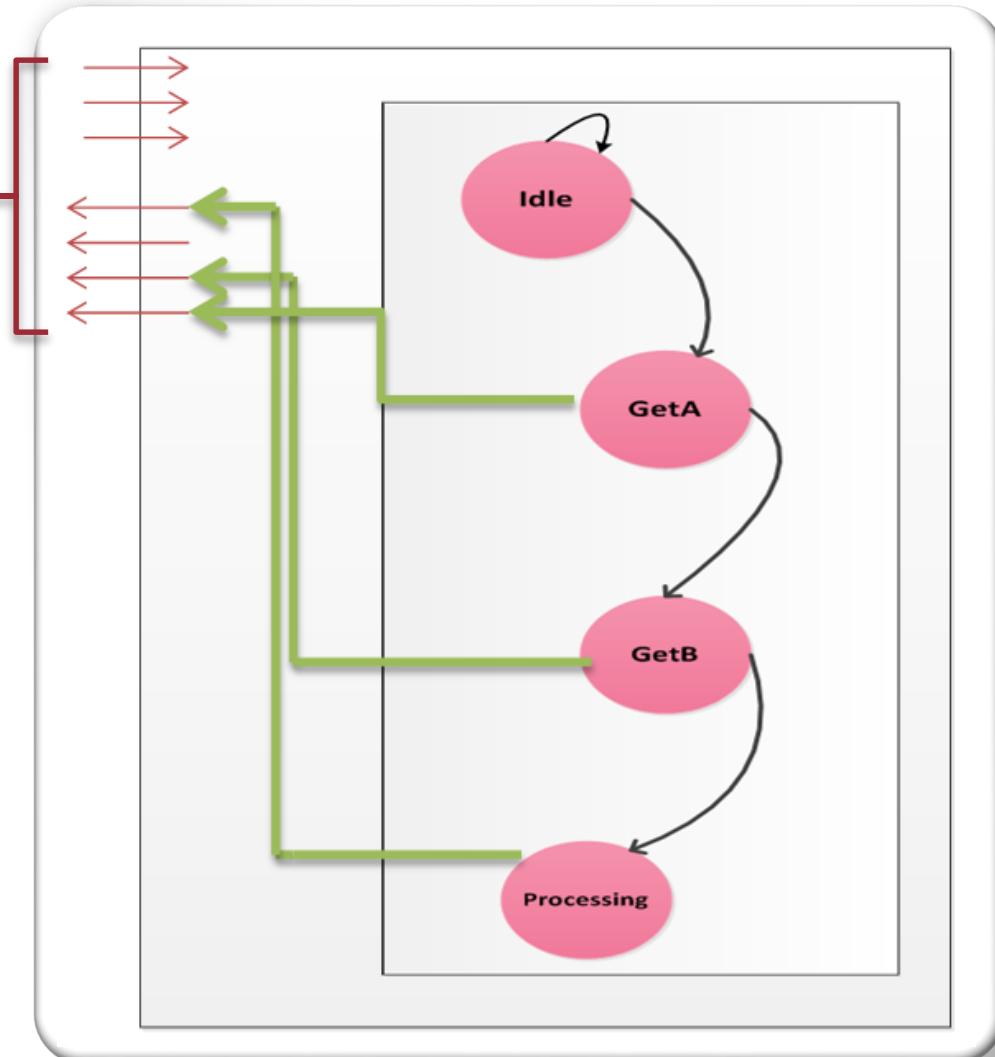
# RTL Controller Example

Signals that go to or  
Come from datapath



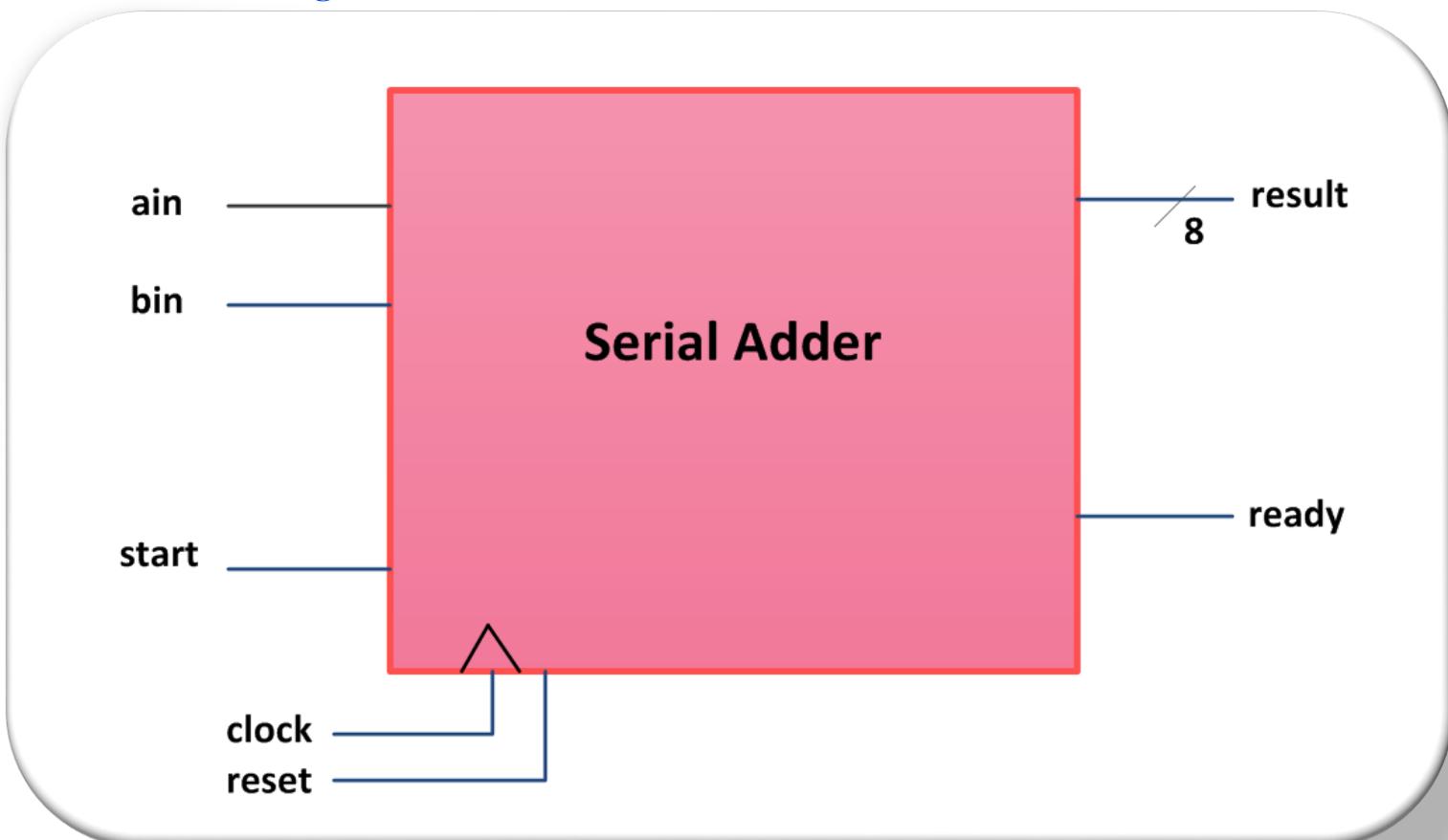
# Example: Serial Adder


After “start” signal is issued, 8 pairs of serial bits on ain and bin are added and an 8-bit result is generated.




# Design Partitioning

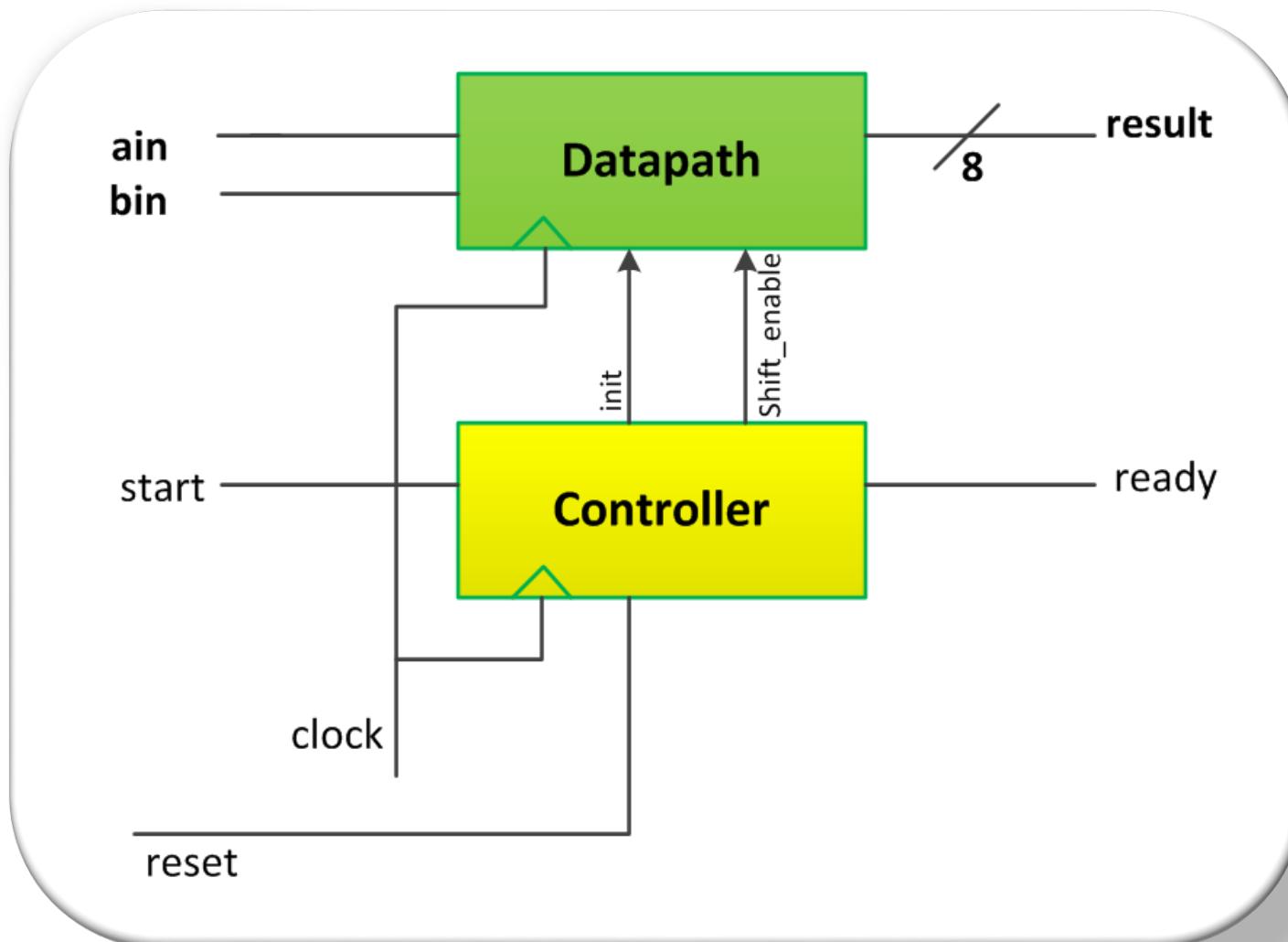


# Datapath Design

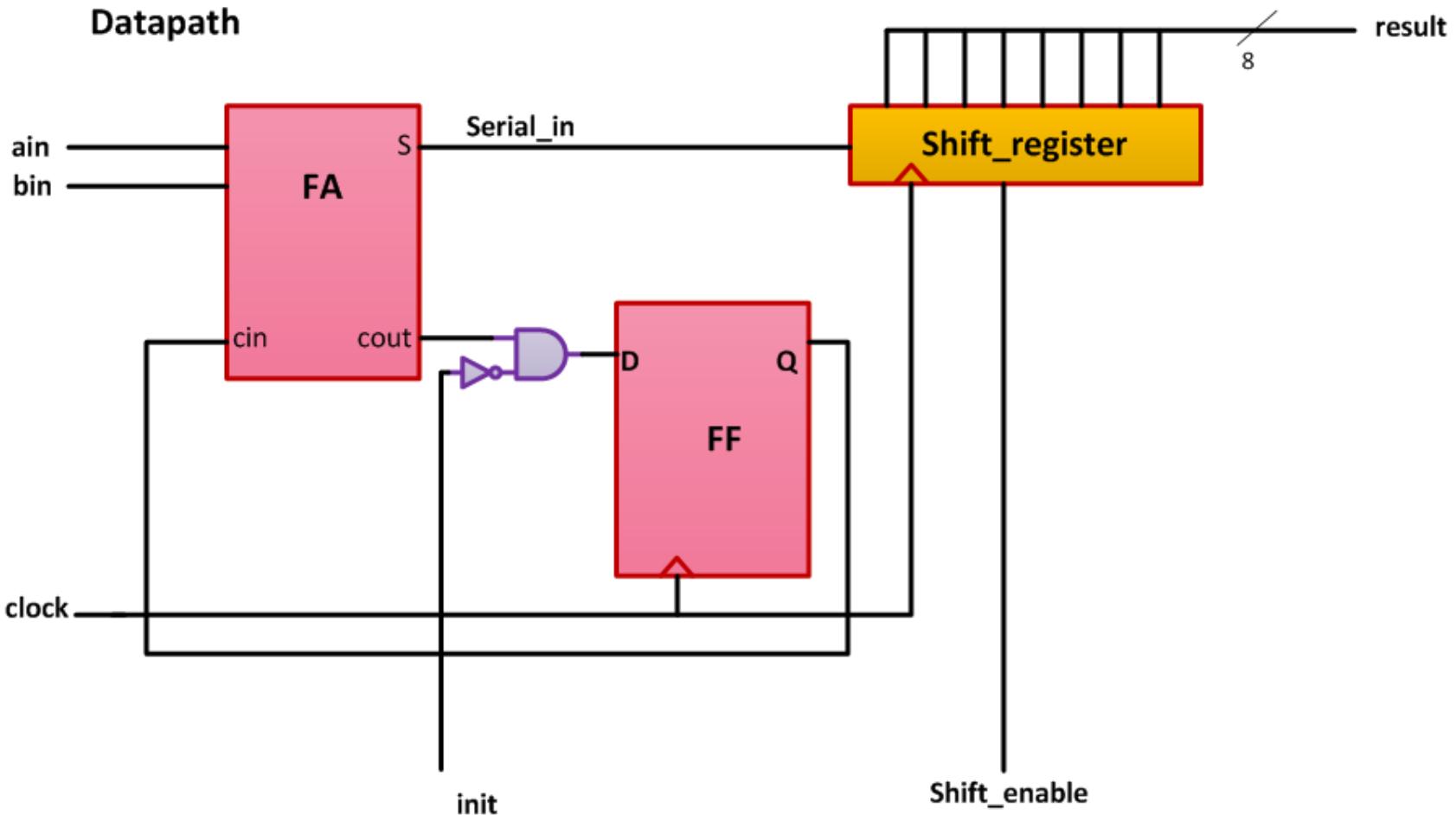


# Controller Design

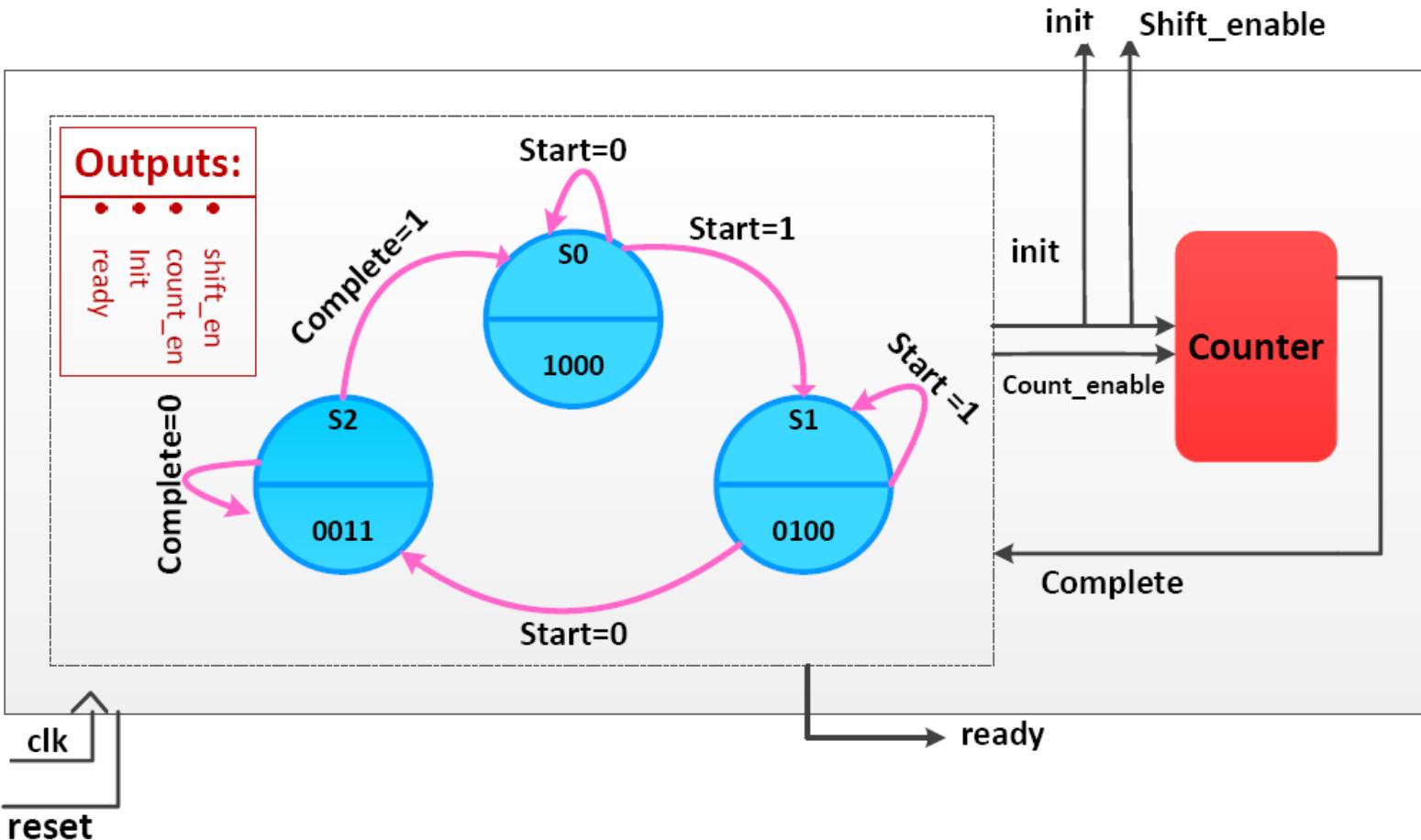


# Wiring Of Datapath And Controller

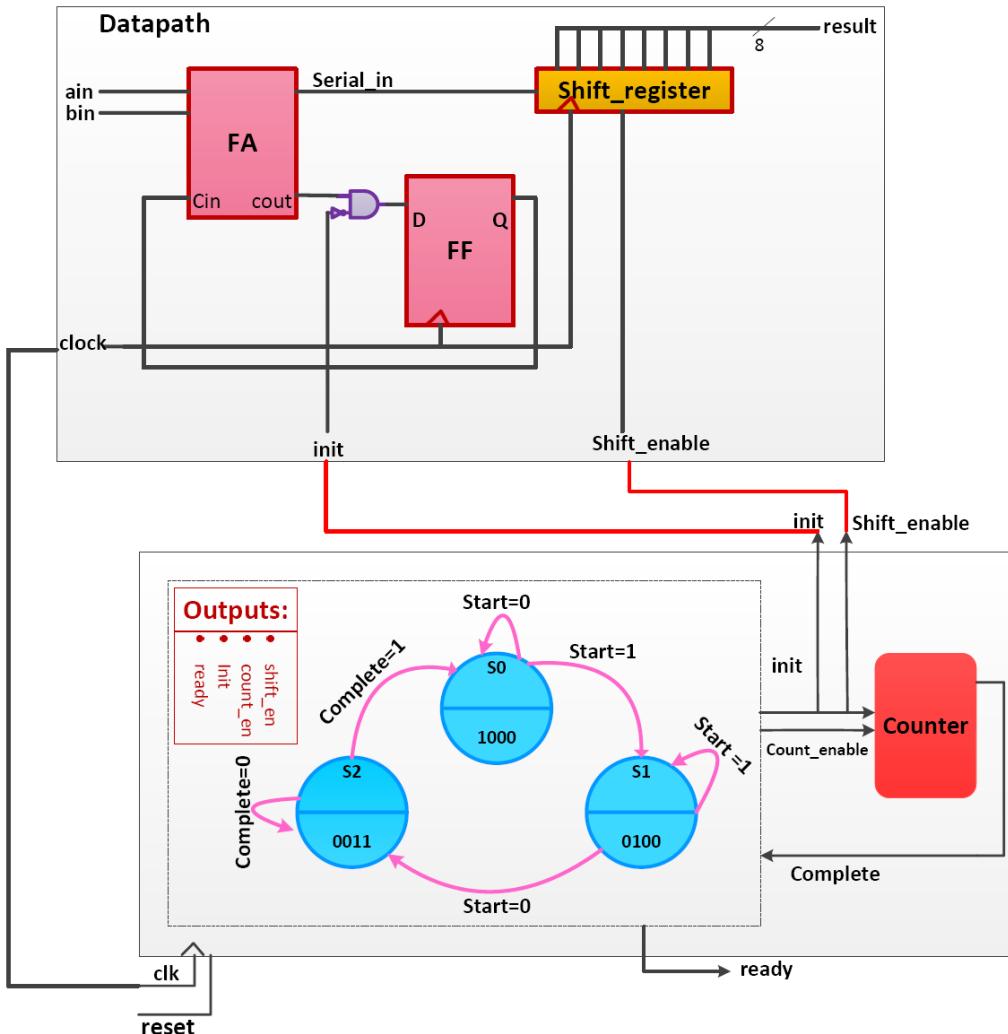

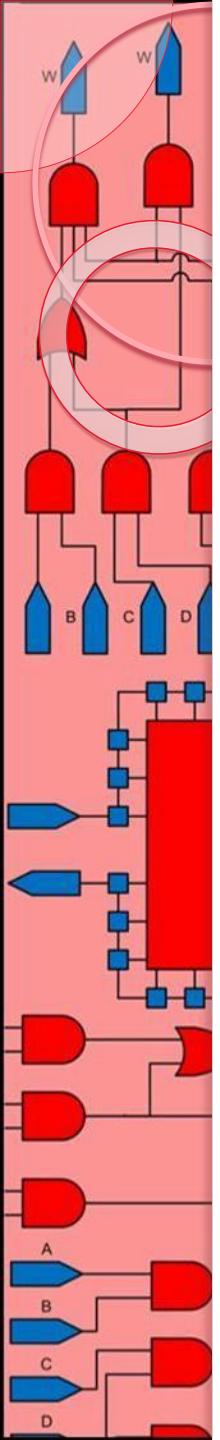
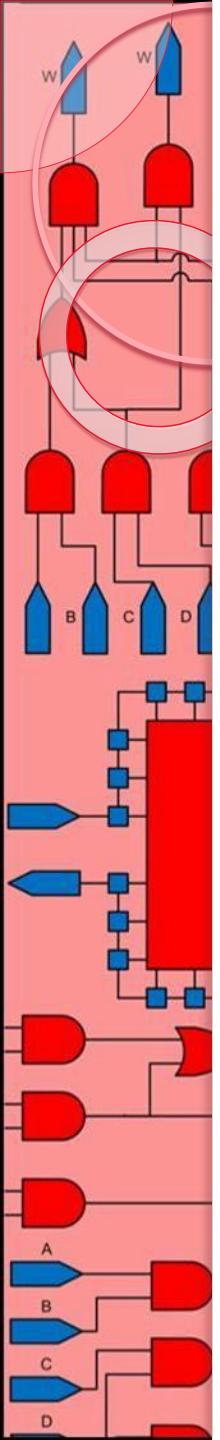
# Summary

- Transistors to processing elements
- Design abstraction levels
- Datapath/controller partitioning
- Example: serial adder
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog

## Lecture 17: RTL Timing

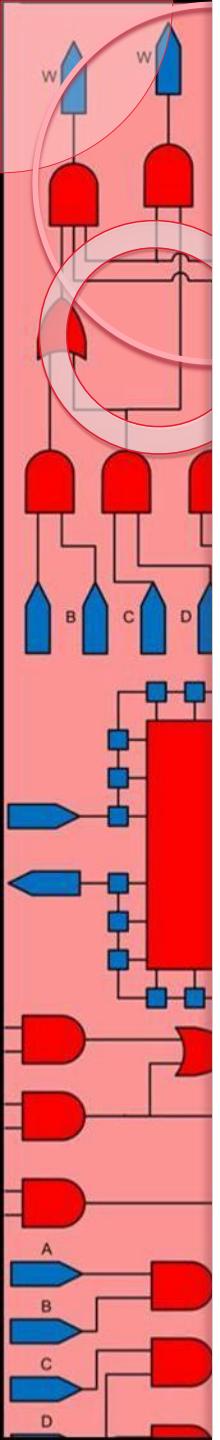

# RTL Timing

- State machine timing
- Datapath/controller timing
- Datapath timing
- Summary

# State Machine Timing

W

W

W


W

# Huffman Model of a Sequential Circuit

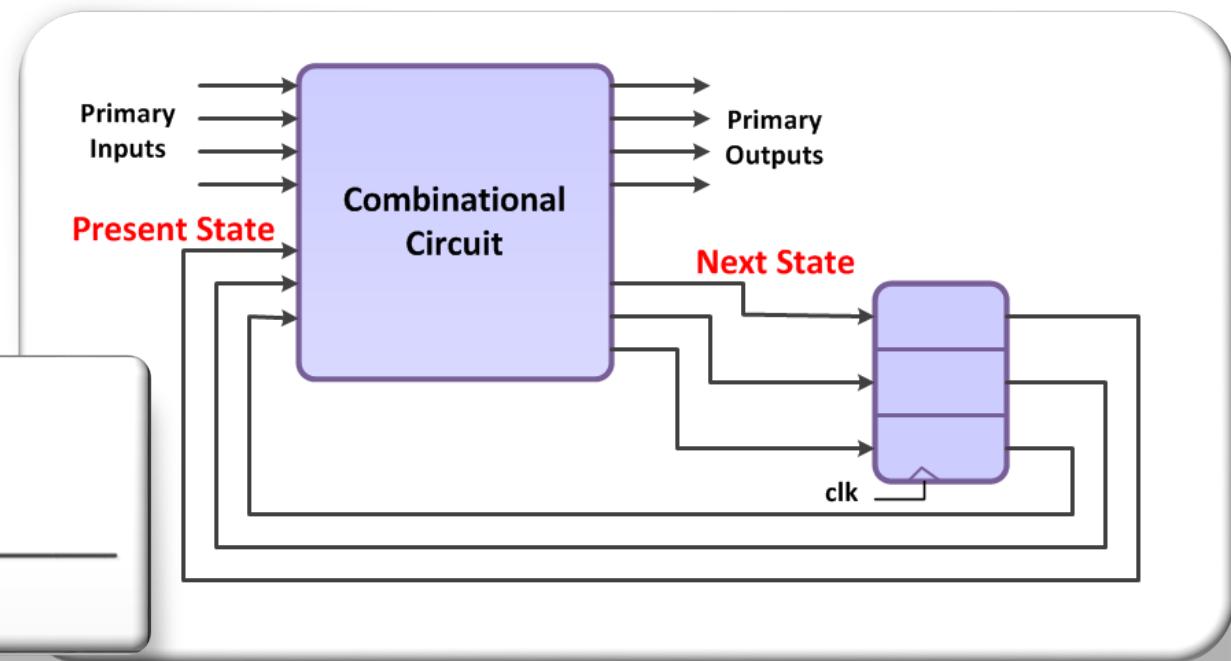


- This much of time allows the combination of PS and PI to propagate and reach to NS and PO output.
- Primary outputs producing their values right after the clock ticks and remain in that way for some time after the next clock tick.

# Datapath/Controller Timing

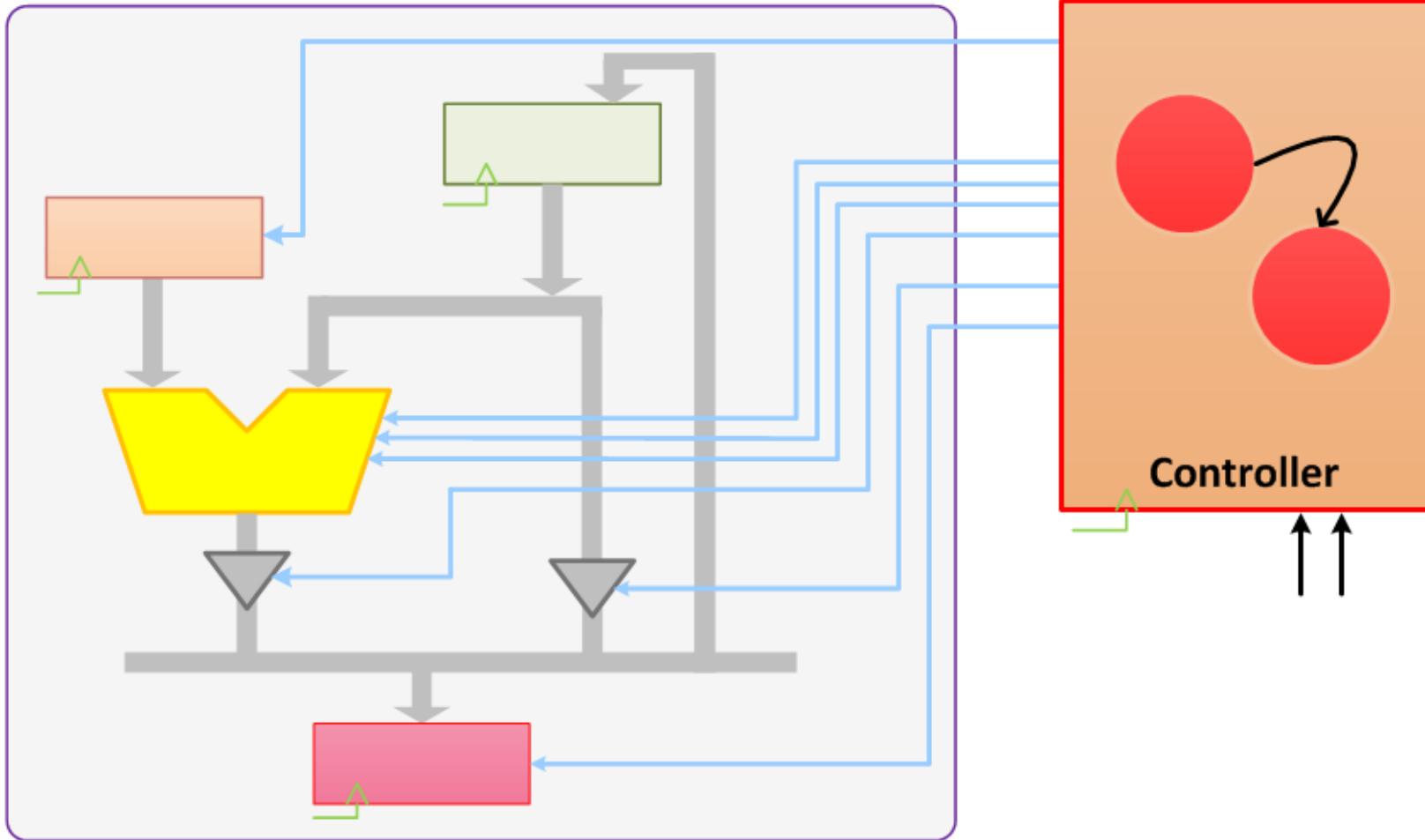


# Datapath/Controller Timing

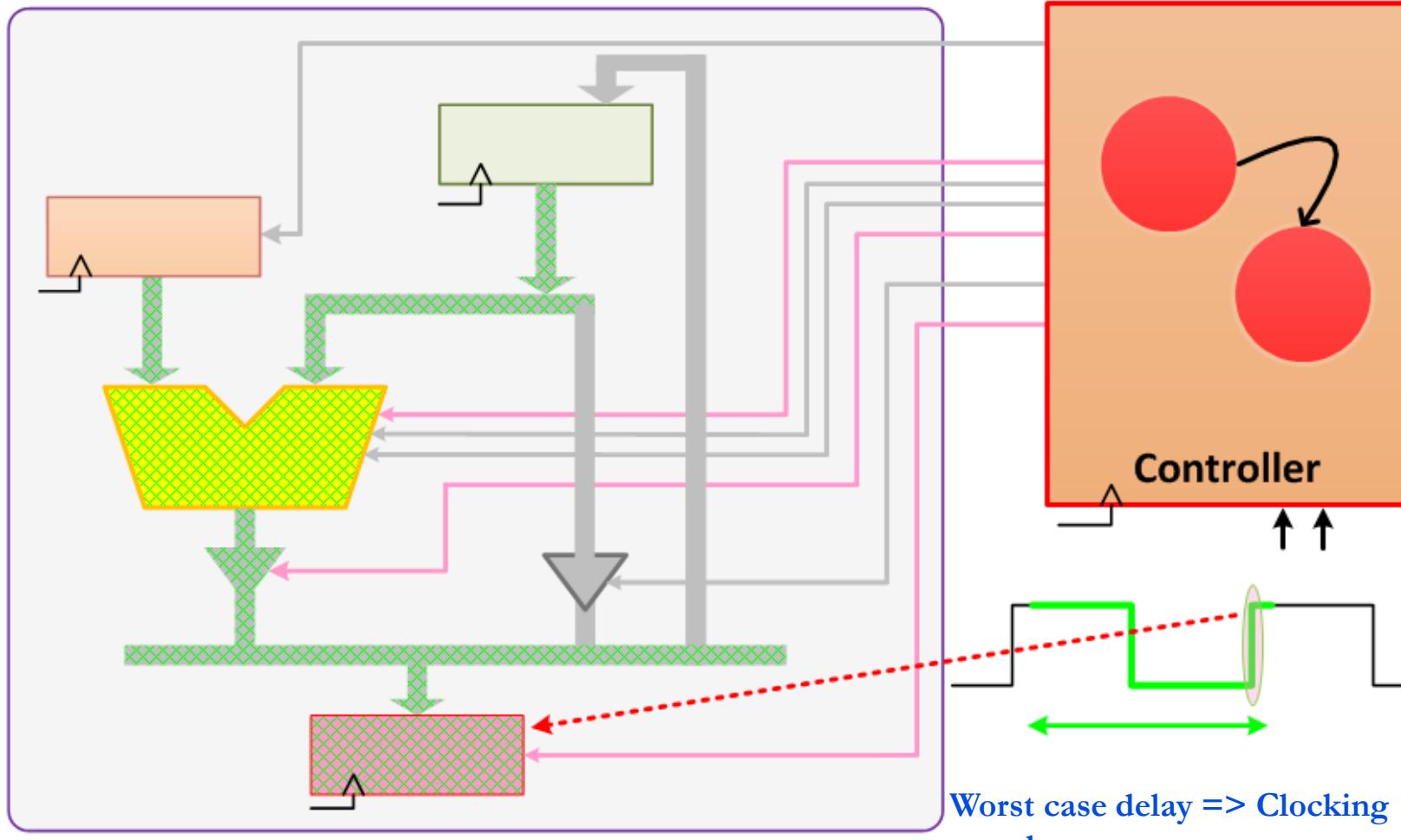

July 2014

© 2013-2014 Zain Navabi, ICEEP, University of Tehran

213

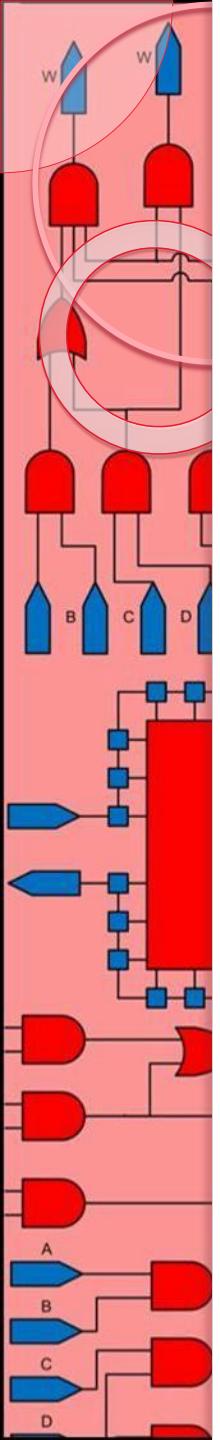



# Datapath Timing

- For finding the clock frequency we should consider the worst case delay(bottleneck) of the datapath
- If we have ALU in datapath, we should take the delay of ALU operation with the most delay, as ALU delay
- Selection of each bus has also its own delay
- Each register has setup time delay
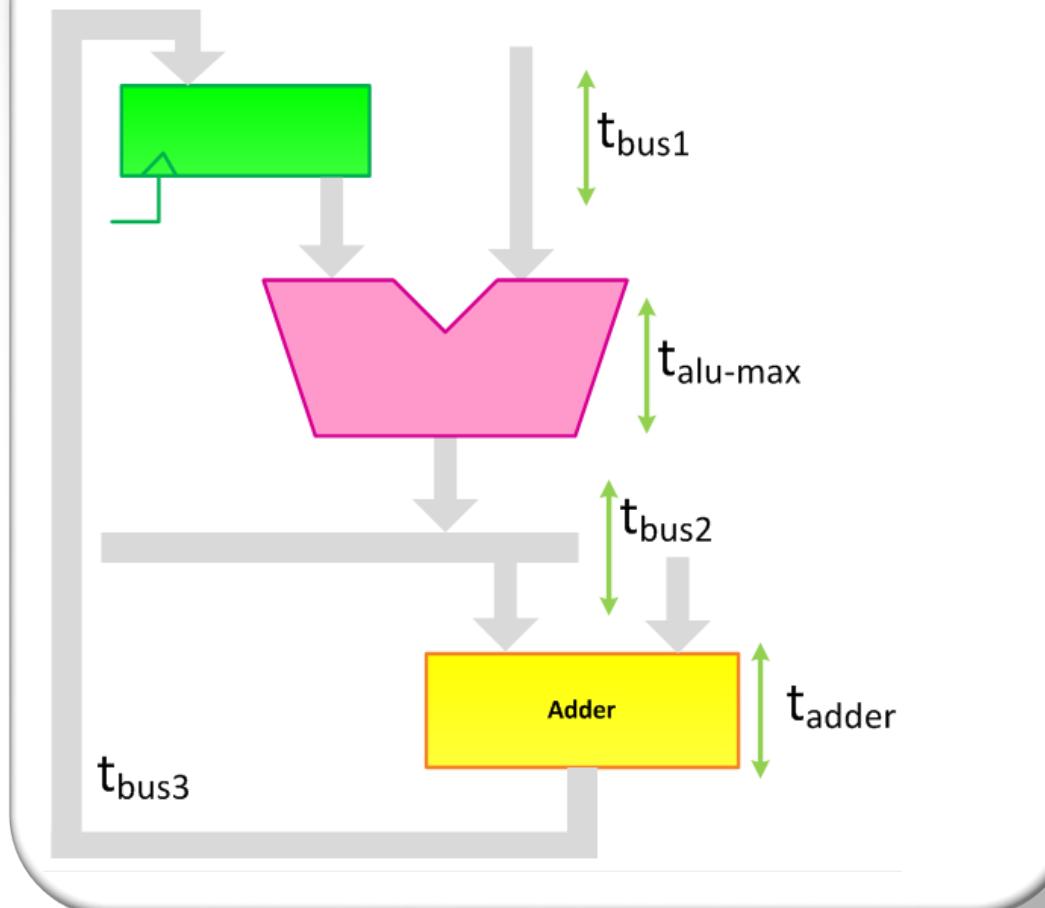
# Datapath Timing


$$t_{\text{total}} = t_{\text{bus1}} + t_{\text{alu-max}} + t_{\text{bus2}} + t_{\text{adder}} + t_{\text{bus3}} + t_{\text{setup}}$$



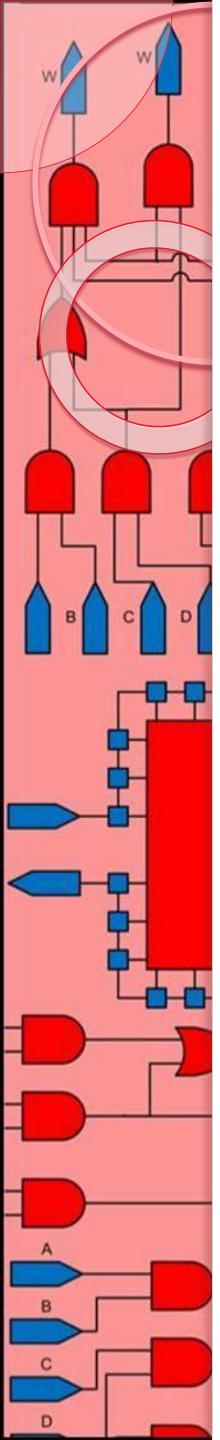
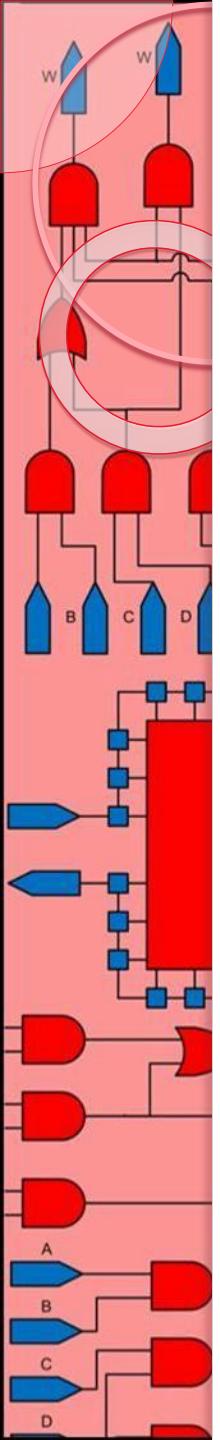
# Summary

- Signals from the controller
- Controller timing
- Datapath timing
- Datapath / Controller Synchronization
- Longest path propagation
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog

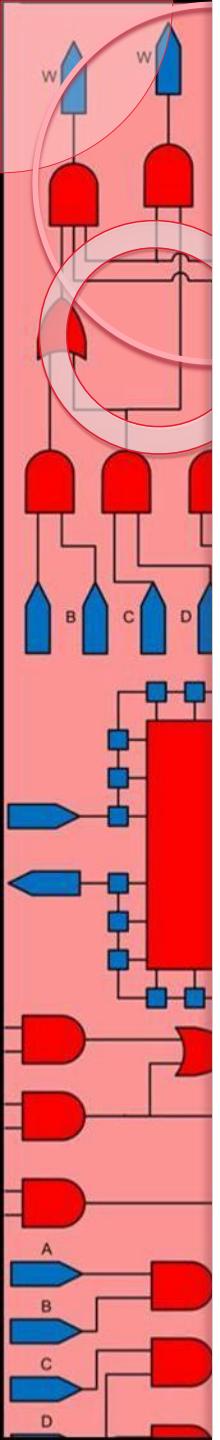
## Lecture 18: RTL Processing Element Design



# RTL Processing Element Design

- Simple unsigned integer divider
- Datapath
- Controller
- Verilog description
- Testbench
- Summary


# Unsigned Integer Divider

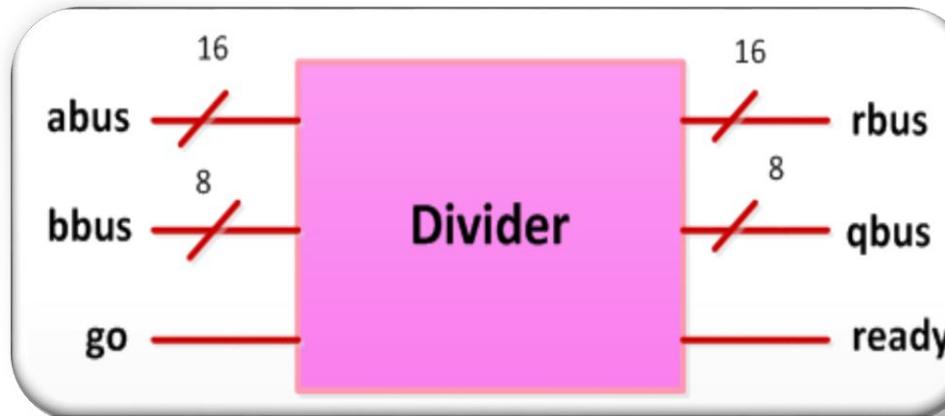

Emphasis is on a simple algorithm, and not very efficient.


- Dividing A by B by subtracting B from A until the remainder is less than B
- The number of times that subtraction successfully happens is the quotient
- The value that is left behind is the remainder

# Unsigned Integer Divider

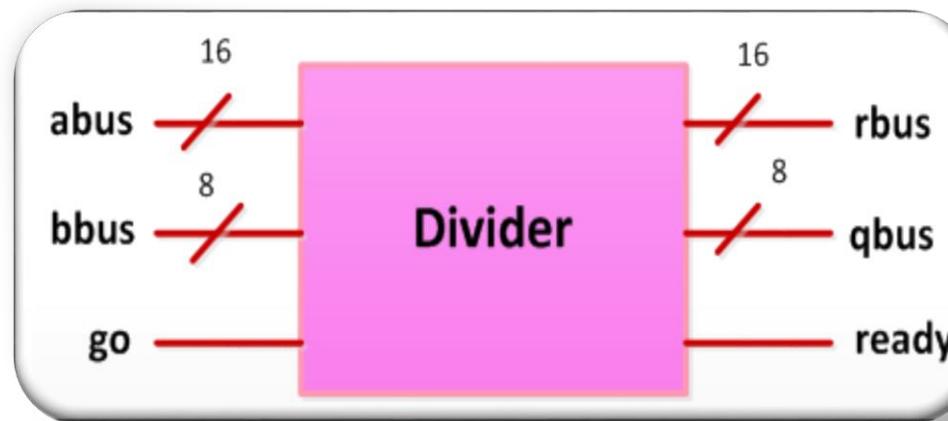



- The circuit has a 16-bit input bus for A, an 8-bit input bus for B and two 8-bit buses for remainder and quotient
- After a complete pulse happens on go, the circuit reads the A and B operands and division begins
- After division is completed, circuit places R and Q on the corresponding buses and issues a one-clock duration pulse on ready

# Unsigned Integer Divider Datapath

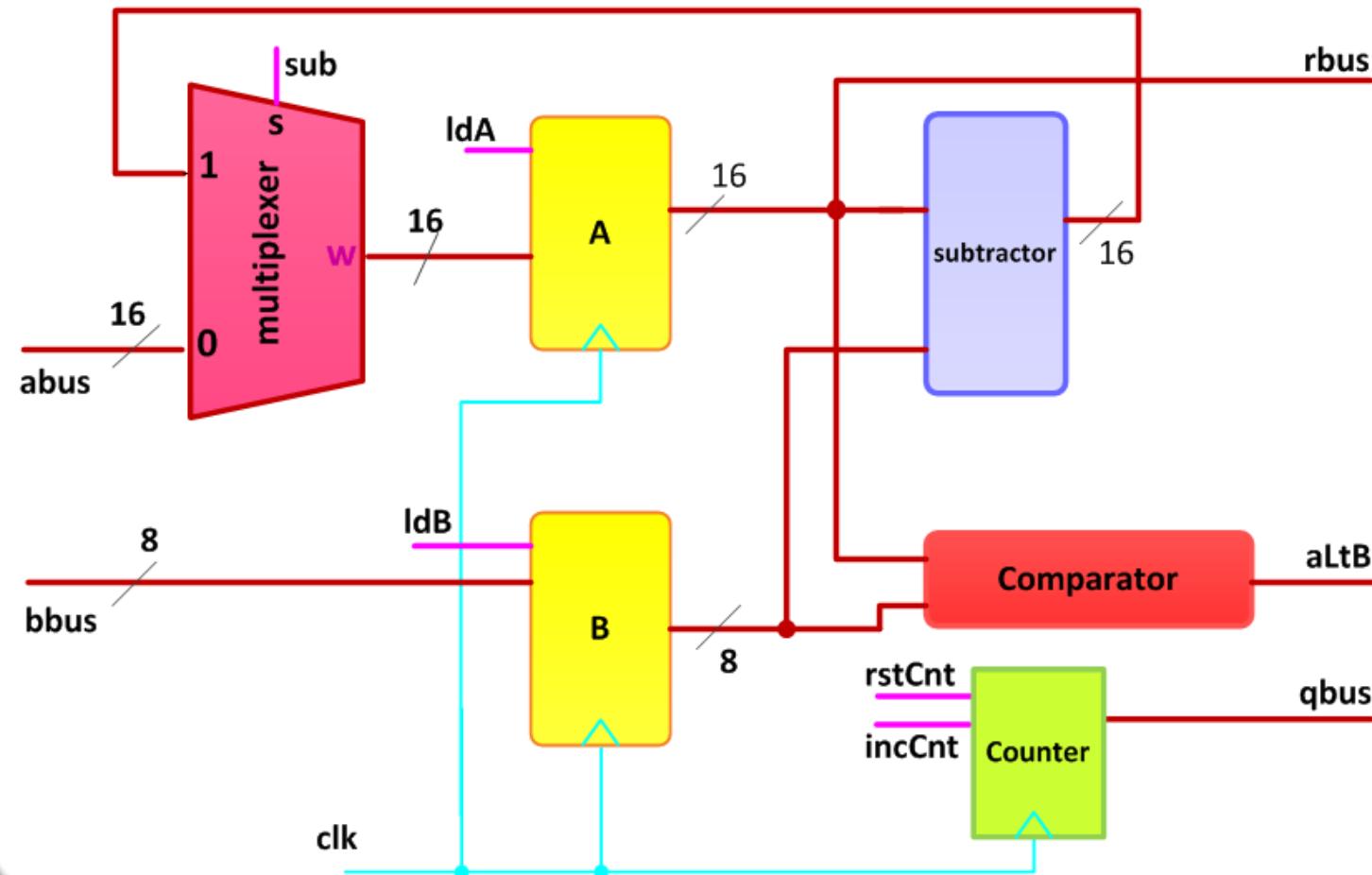

# Unsigned Integer Divider Controller

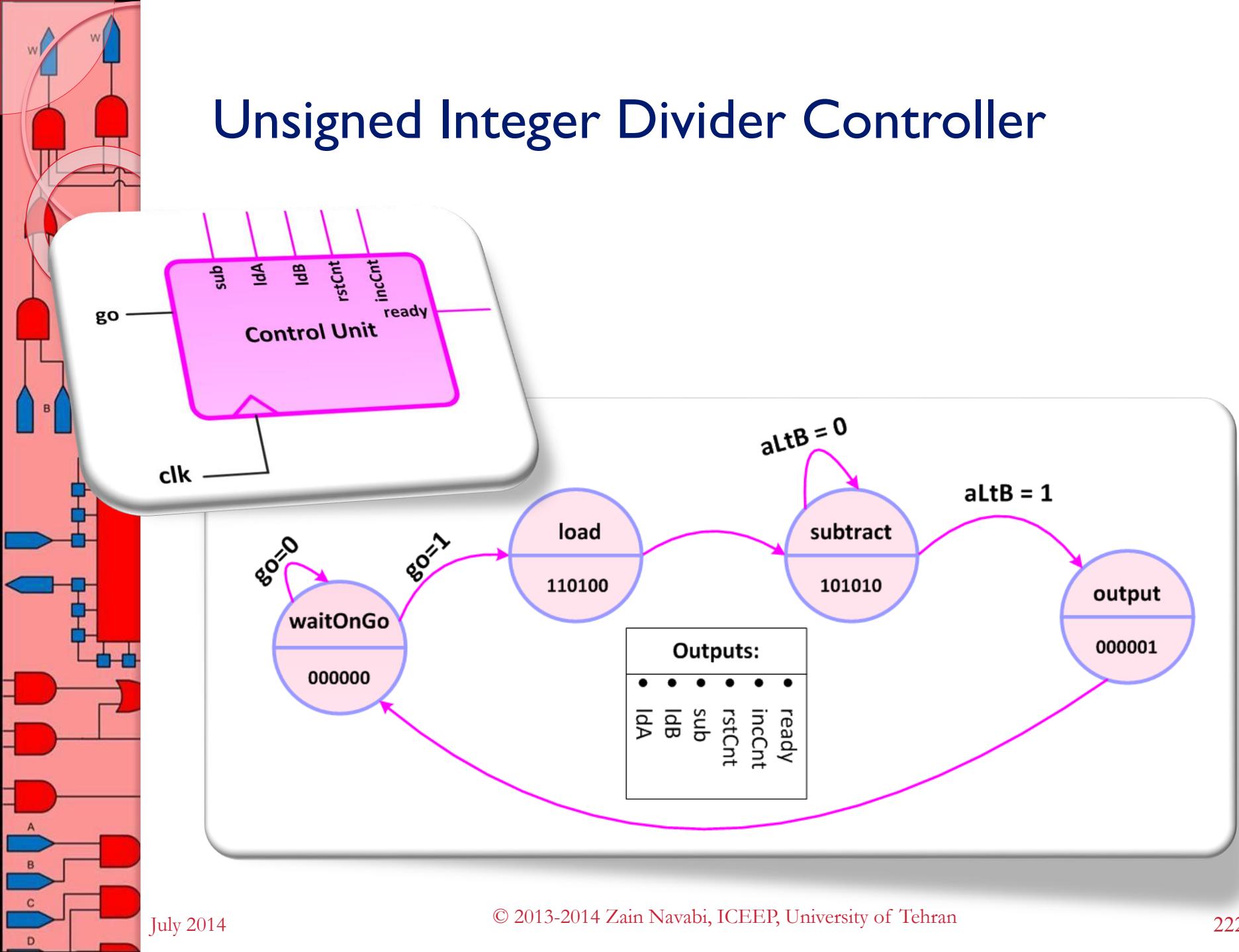

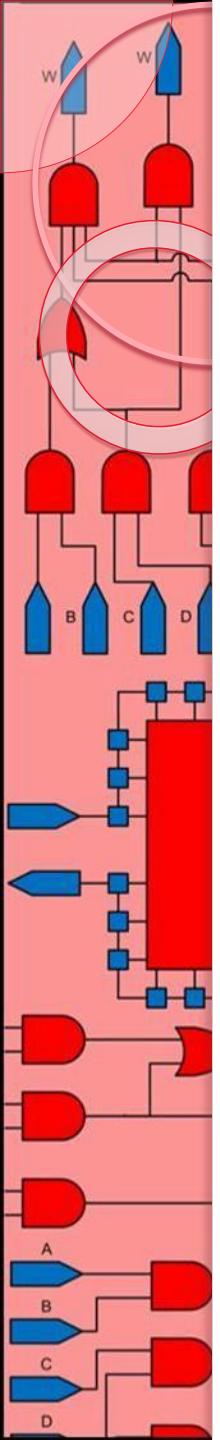


# Unsigned Integer Divider
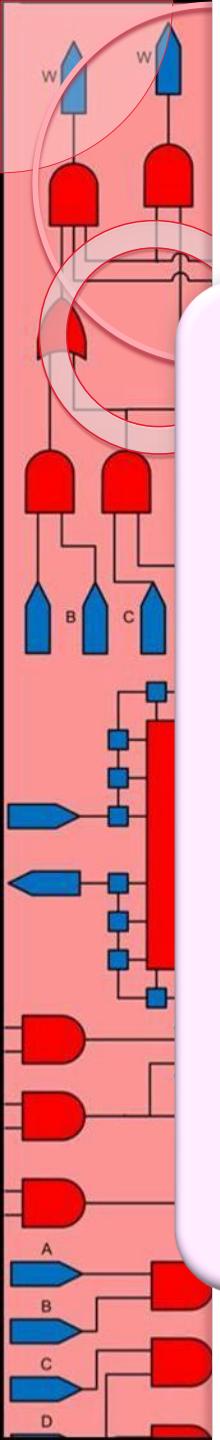
## Verilog Code of Controller

```
'timescale 1ns/1ns
module controller( input clk, rst, go, aLtB, output reg sub ,ldA ,ldB ,rstCnt ,incCnt ,ready);
    parameter waitOnGo = 2'b00, load = 2'b01, subtract = 2'b10, getout = 2'b11;
    reg[1:0] ps, ns;

    always @( ps, go, aLtB )
        begin
            ns = waitOnGo; ldA = 1'b0; ldB = 1'b0; sub = 1'b0;
            rstCnt = 1'b0; incCnt = 1'b0; ready = 1'b0;
            case (ps)
                waitOnGo: begin
                    if(go == 1'b1) ns = load; else ns = waitOnGo;
                end
                load: begin
                    ldA = 1'b1; ldB = 1'b1; rstCnt = 1'b1; ns = subtract;
                end
                subtract: begin
                    if(aLtB == 1'b1) ns = getout;
                    else begin
                        ns = subtract; ldA = 1'b1; sub = 1'b1; incCnt = 1'b1;
                    end
                end
            end
        end
endmodule
```




# Unsigned Integer Divider
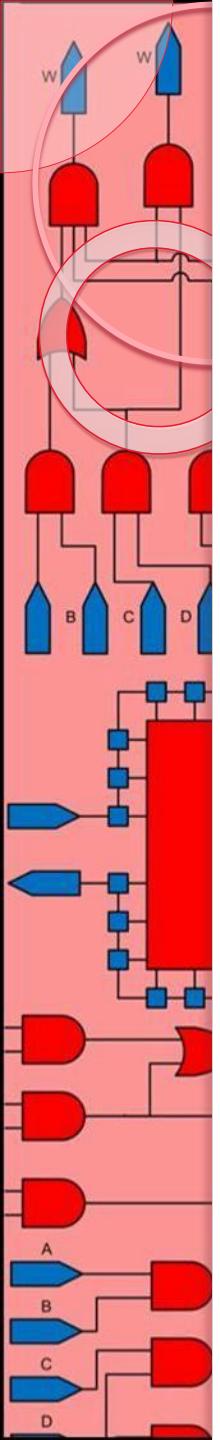
## Verilog Code of Controller

```
getout: begin
    ready = 1'b1; ns = waitOnGo;
end
endcase
end

always @(posedge clk)
begin
    if (rst == 1'b1) ps = waitOnGo;
    else ps = ns;
end
```



# Unsigned Integer Divider

## Verilog Code of Datapath

```
module datapath ( aBus, bBus, clk, rstCnt, incCnt, ldA, ldB, sub, rBus, qBus, aLtB);


    input [15:0] aBus, bBus;
    input clk, rstCnt, incCnt, ldA, ldB, sub;
    output [15:0] rBus, qBus;
    output aLtB;

    wire [15:0] subOut, muxOut, aRegOut, bRegOut;

    mux16_2to1 g0(aBus, subOut, sub, muxOut);
    reg16 g1(clk, ldA, muxOut, aRegOut);
    reg16 g2(clk, ldB, bBus, bRegOut);
    subtractor g3(aRegOut, bRegOut, subOut);
    comparator g4 (aRegOut, bRegOut, aLtB);
    counter16 g5(clk, rstCnt, incCnt, qBus);

    assign rBus = aRegOut;

endmodule
```

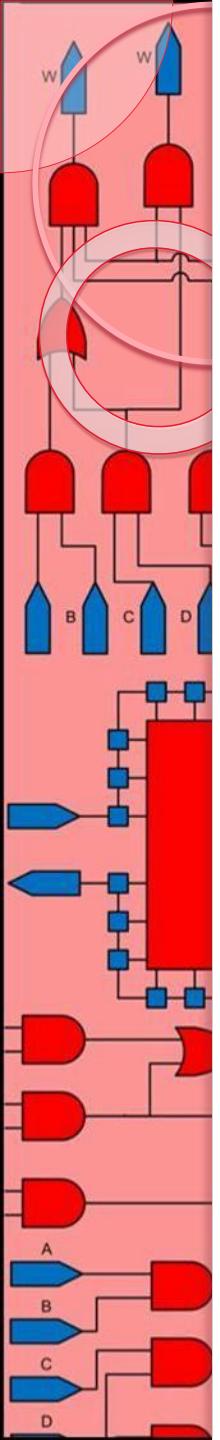

# Complete Design

```
'timescale 1ns/1ns


module divider (clk, go, aBus, bBus, qBus, rBus, ready);
    input clk, go;
    input [15:0] aBus, bBus;
    output [15:0] qBus, rBus;
    output ready;

    wire rstCnt, incCnt, lda, ldb, sub, aLtb;

    datapath DP(aBus, bBus, clk, rstCnt, incCnt, lda, ldb, sub, rBus, qBus, aLtb);
    controller CTRL(clk, rst, go, aLtb, sub, lda, ldb, rstCnt, incCnt, ready);

endmodule
```

1

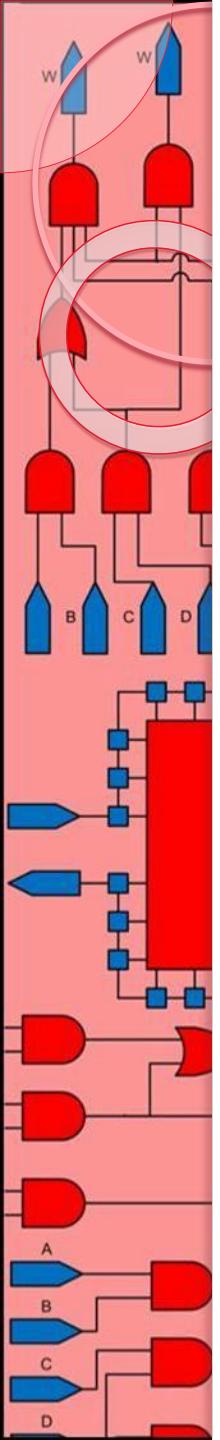


# Testbench

```
module divider_TB ();
    reg clk, go;
    reg [15:0] aBus, bBus;
    wire ready;
    wire [15:0] qBus, rBus;

    divider DIV(clk, go, aBus, bBus, qBus, rBus, ready);
initial begin
    clk = 1'b0;
    aBus = 16'b00001000011100100;
    bBus = 16'b00000000101100101;
    go = 1'b1;
    #15;
    go = 1'b0;


    #50;
    aBus = 16'b01101010000001101;
    bBus = 16'b00001001011001100;
    go = 1'b1;
    #15;
    go = 1'b0;

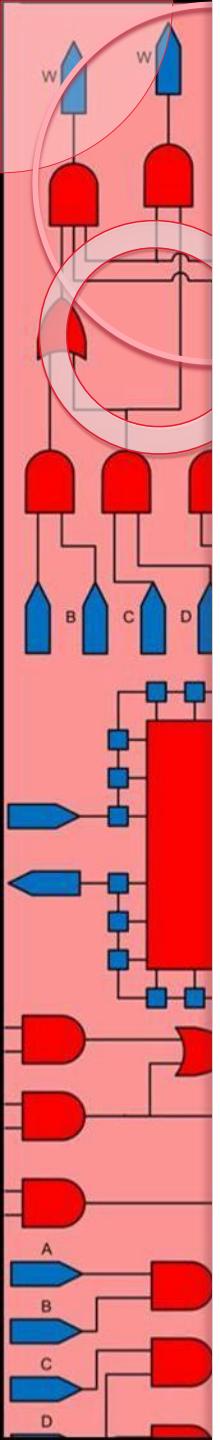    #50;
    aBus = 16'b00001010011101111;
    bBus = 16'b000000010010111101;
    go = 1'b1;
    #15;
    go = 1'b0;
end
```


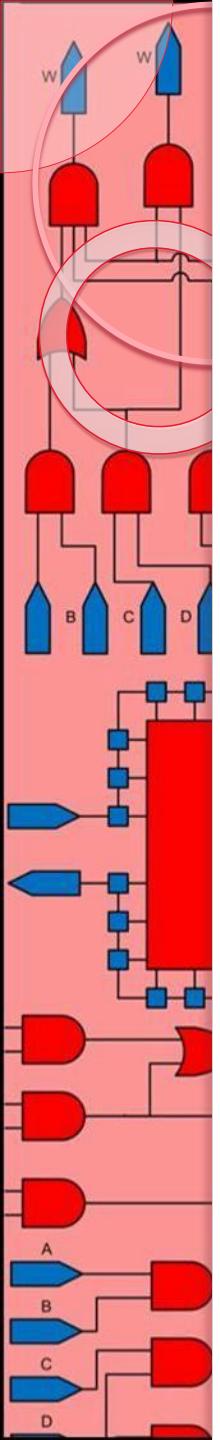
# Summary

- Simple unsigned integer divider
- Datapath
- Controller
- Verilog description
- Testbench
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog

## Lecture 19: Handshaking

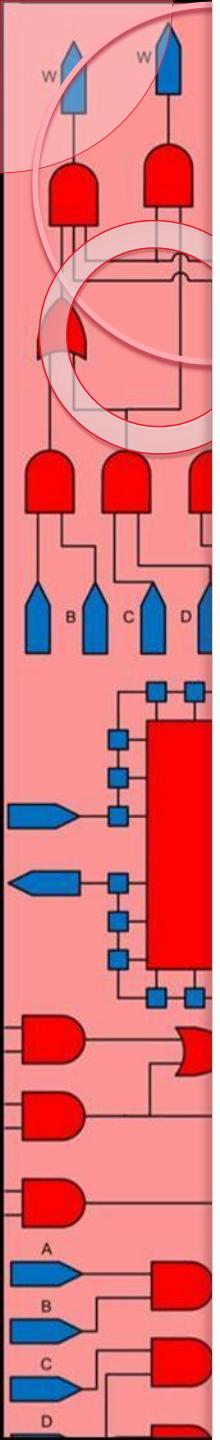
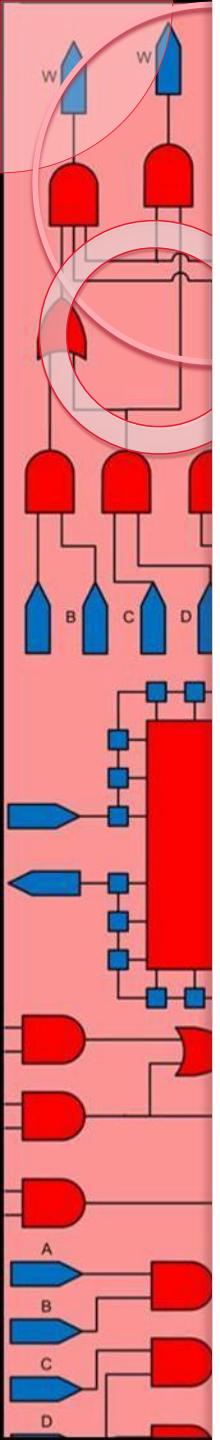
# Handshaking

- Handshaking definition
- Types of handshaking
  - Handshaking between two systems
  - Handshaking for accessing a shared bus
  - Memory handshaking
  - DMA mode or burst mode
- Handshaking with timing details




# Why Handshaking?

- Two systems wants to communicate data and they don't necessarily have the same timing
- The systems have to send some signals before the actual data is transmitted
- Handshaking implementation is a part of the control of the system
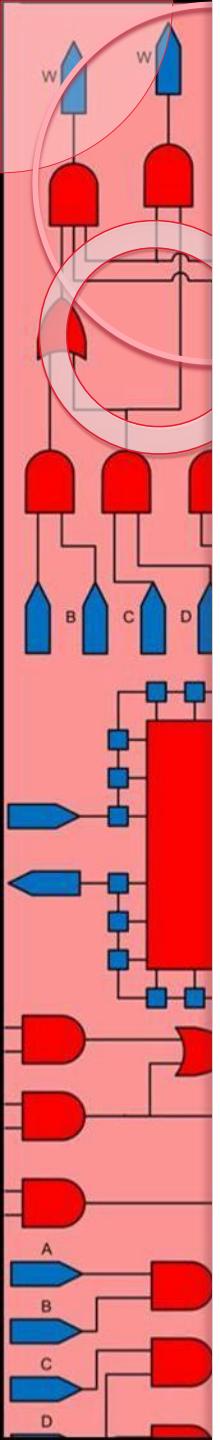
# Between two RTLs Handshaking


- Two systems wants to communicate data and they don't necessarily have the same timing
- The systems have to send some signals before the actual data is transmitted
- Handshaking implementation is a part of the control of the system




# Types of Handshaking

- Handshaking between two systems
- Handshaking for accessing a shared bus
- Memory handshaking
- DMA mode or burst mode
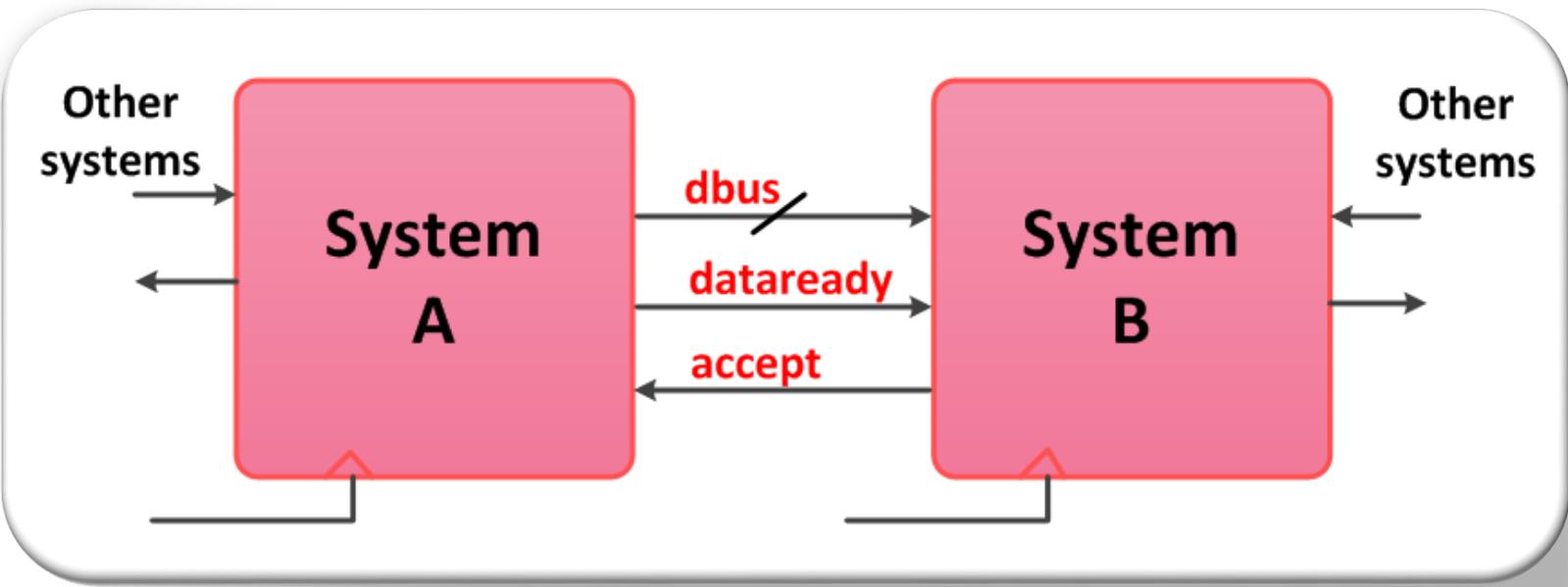
# Handshaking Type One: Handshaking Between Two Systems




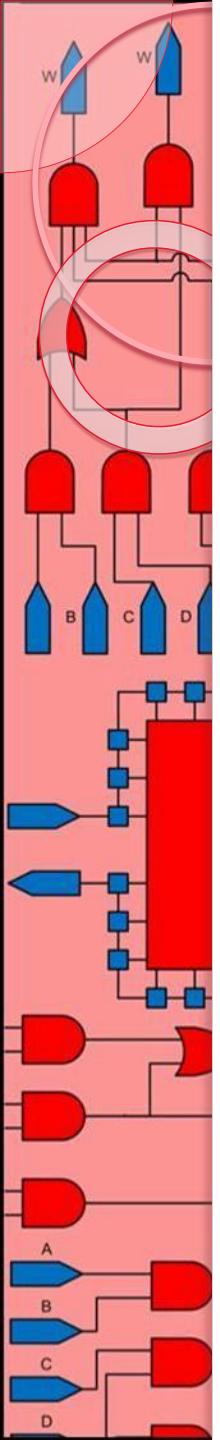- Each system has its own clocking
- They have to have certain signals to talk




# Handshaking Type One: Handshaking Between Two Systems



- Fully responsive handshaking

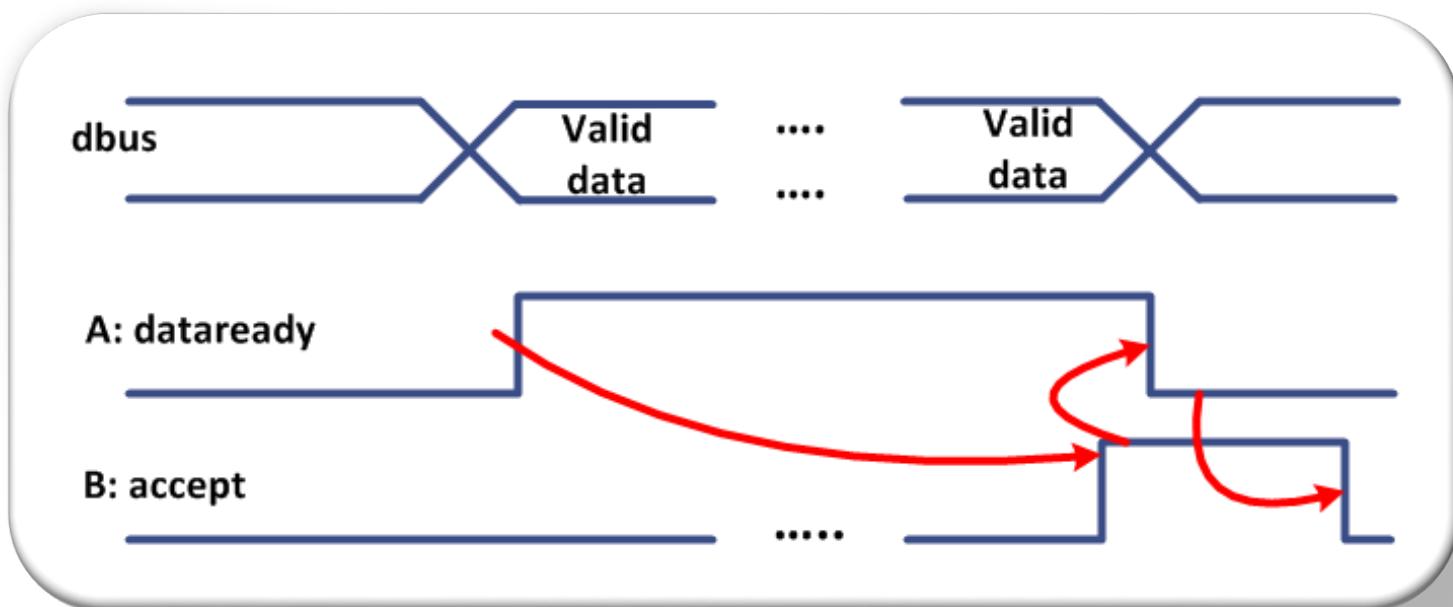

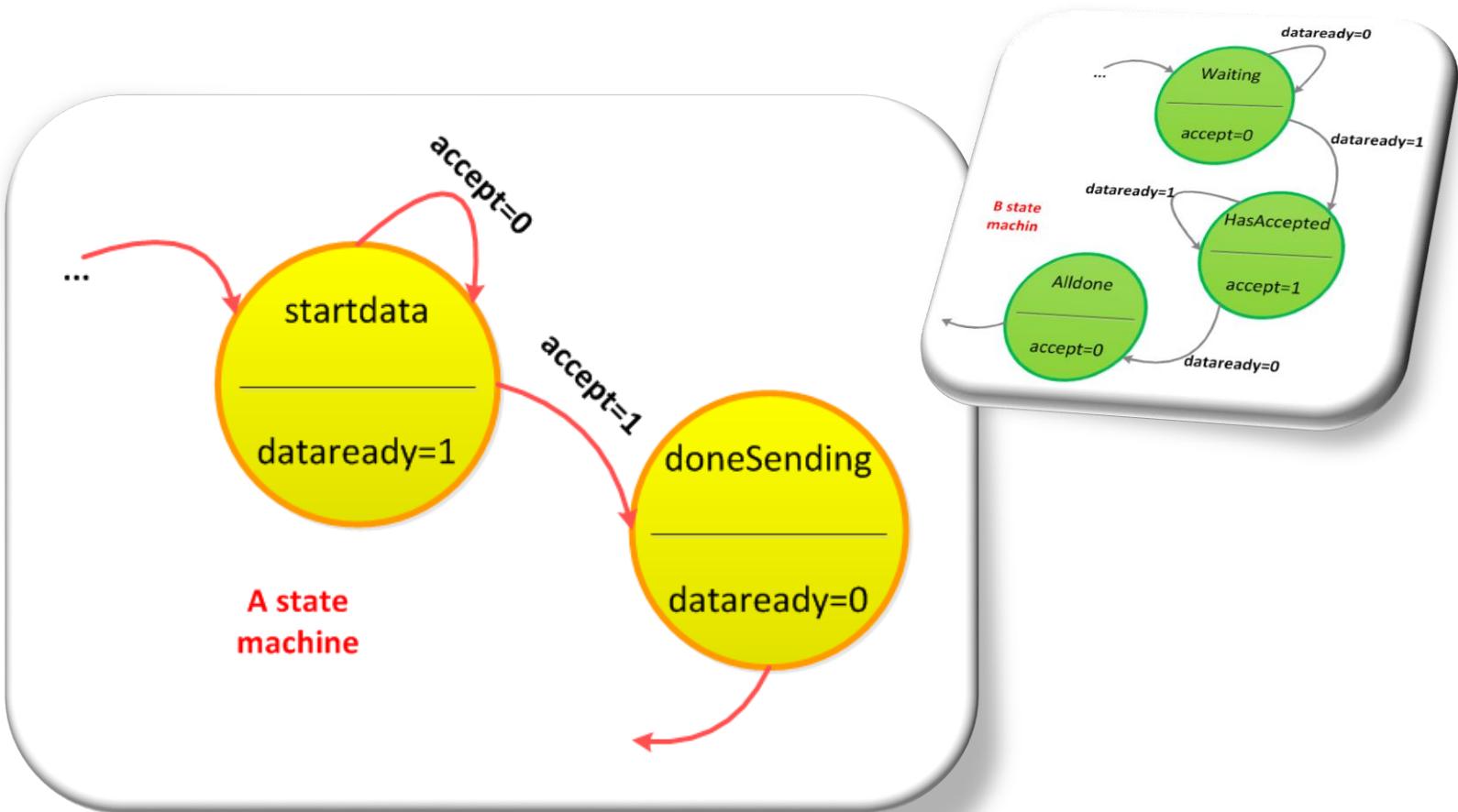
# Handshaking Type One: Handshaking Between Two Systems


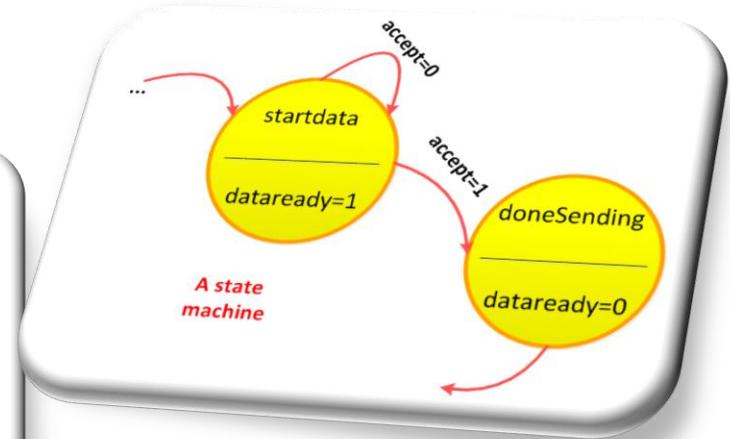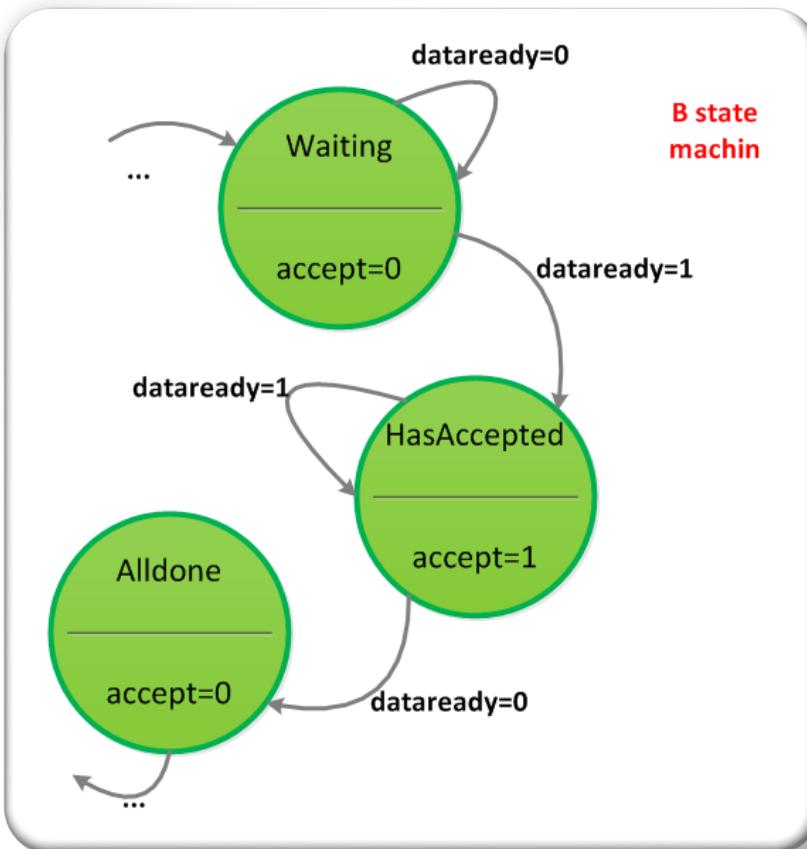
# Handshaking Type One: Handshaking Between Two Systems




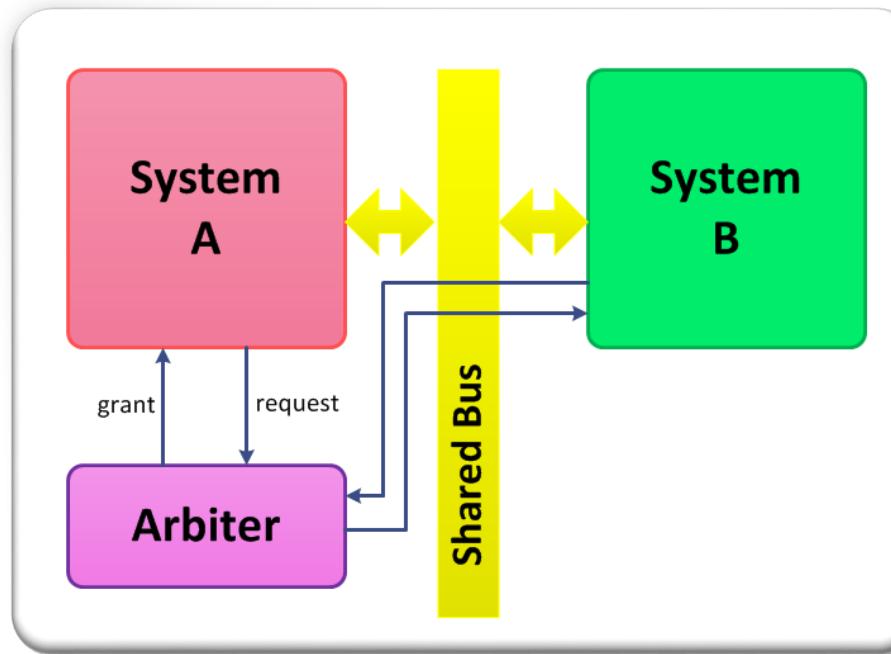
# Handshaking Type Two: Handshaking for accessing a shared bus



- Using an arbiter to assure that none of the systems will simultaneously access the shared bus
- Each system has to have its own request and grant signals
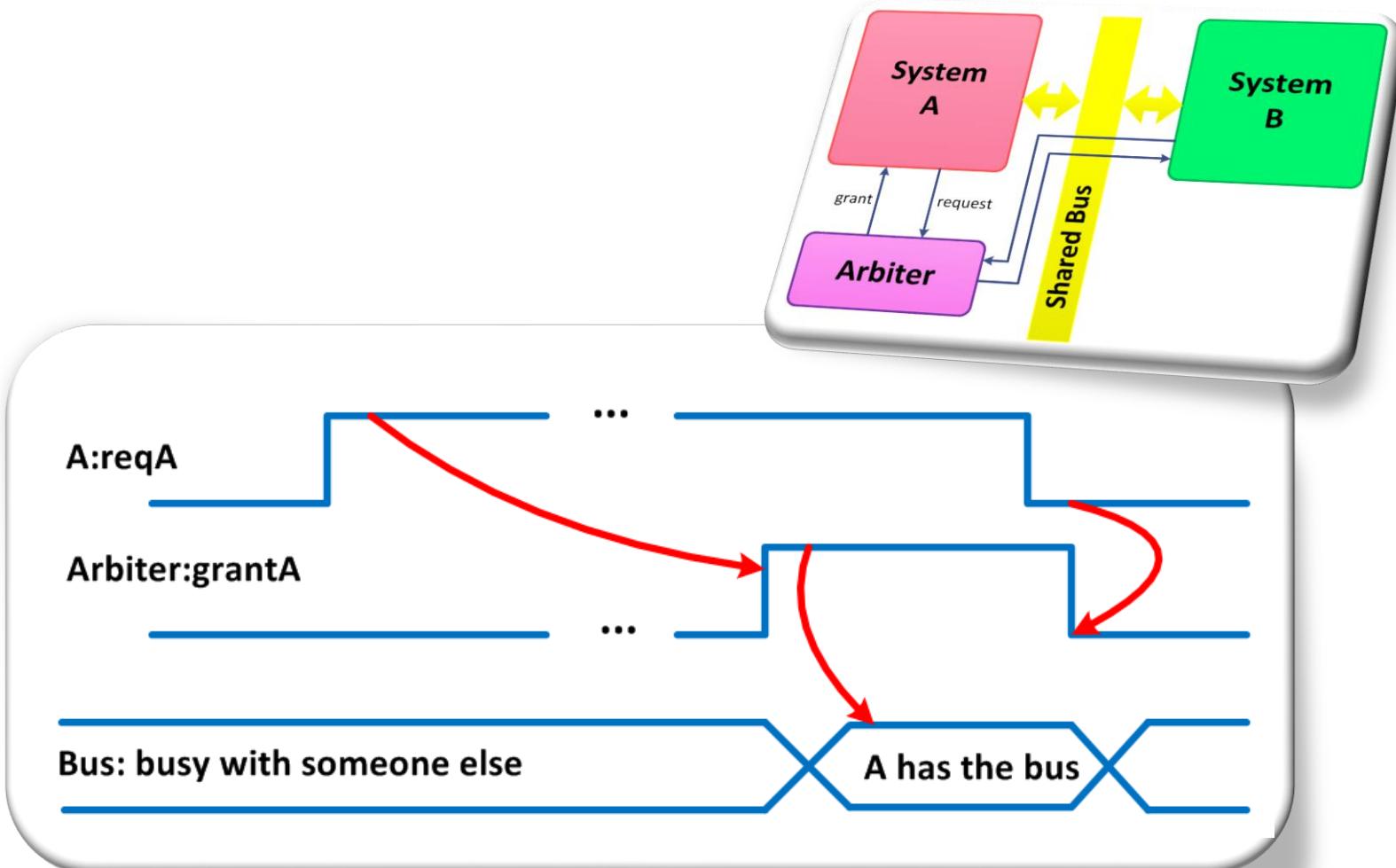
# Handshaking Type Two: Handshaking for accessing a shared bus






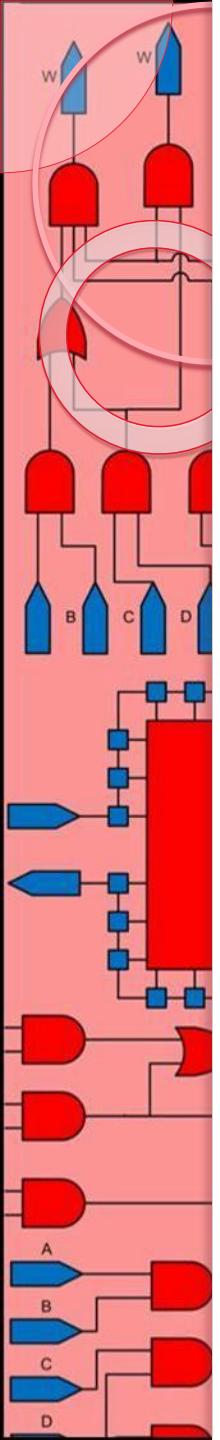


## Two level handshaking

- Assume that system A wants to send some data to B through a shared bus
- At first A should talk to the arbiter and catches the bus by issuing a request .
- Once it puts the data on bus it informs system B by issuing ready
- After data is picked up by B,A removes its request.

# Two level handshaking

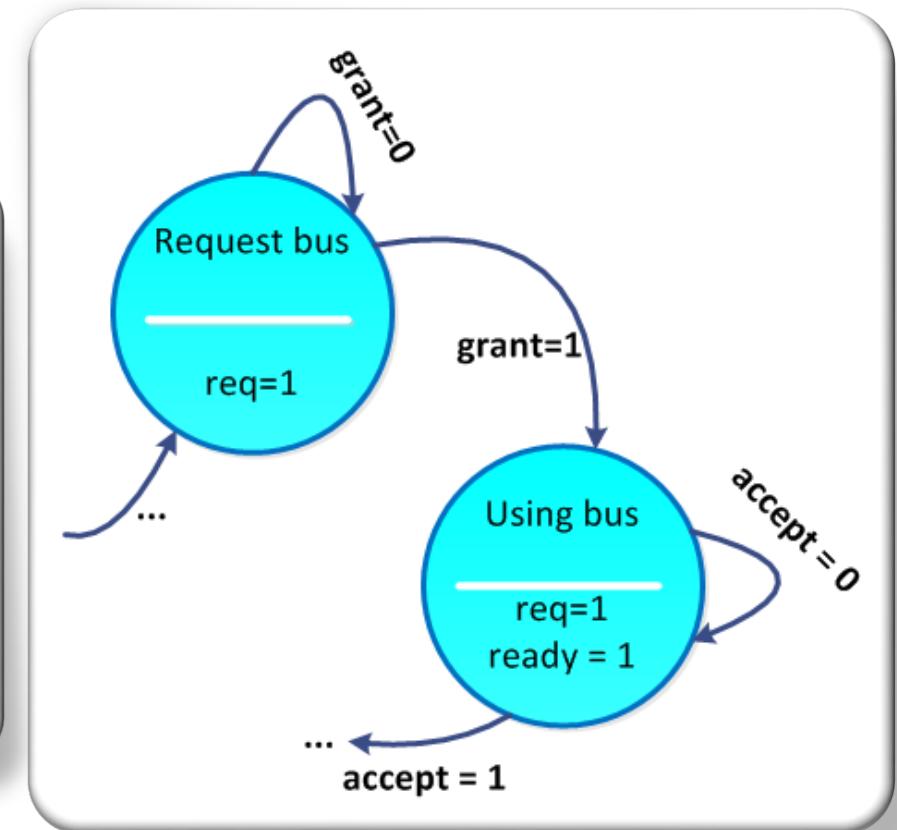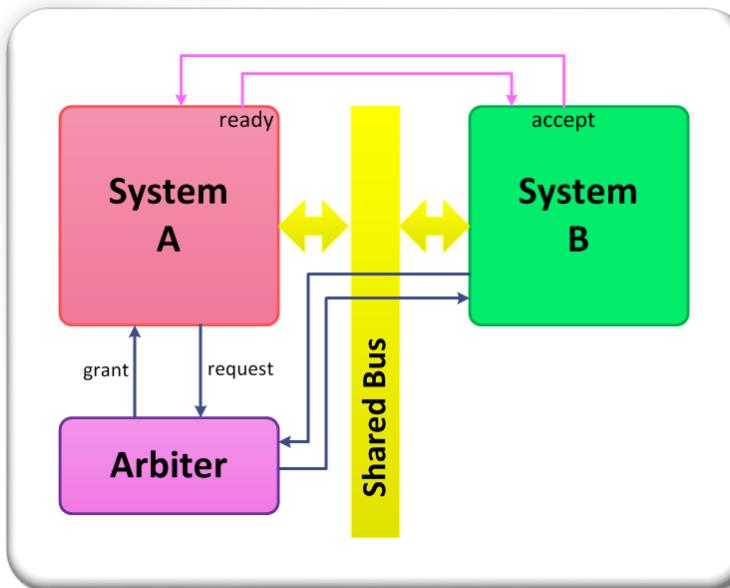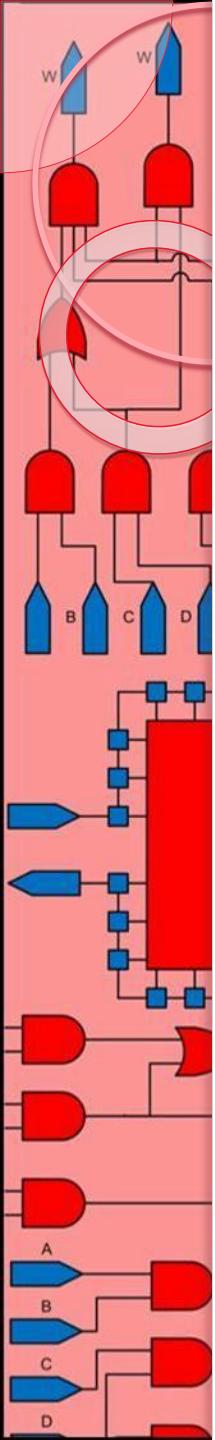

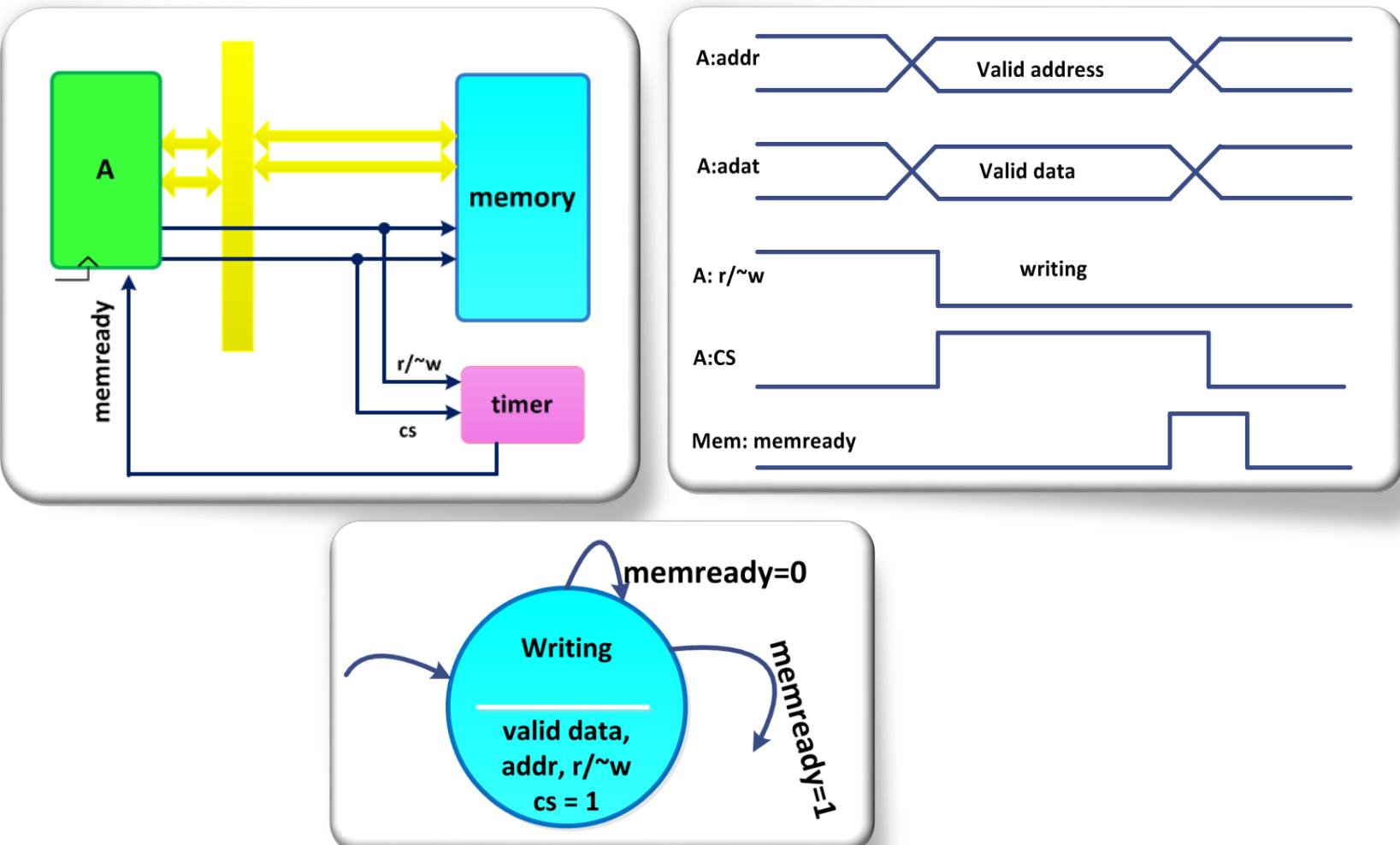
# Handshaking Type Three: memory handshaking




# Combining Type Two and Three of Handshaking

- We can combine type two and three of handshaking
- At first A should deal with arbiter and gets the permission of using the bus
- Then it should send signals to the memory and waits for memready

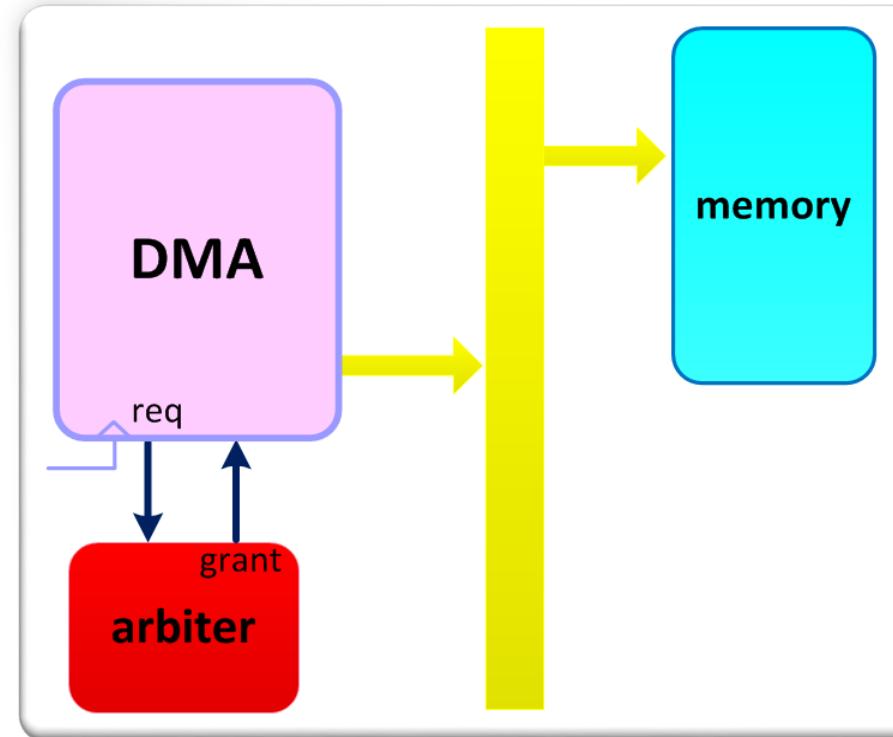
# Handshaking Type Four: DMA Mode Or Burst Mode



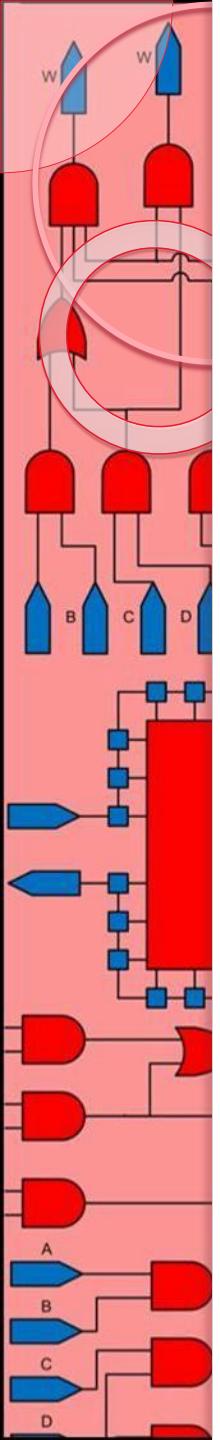
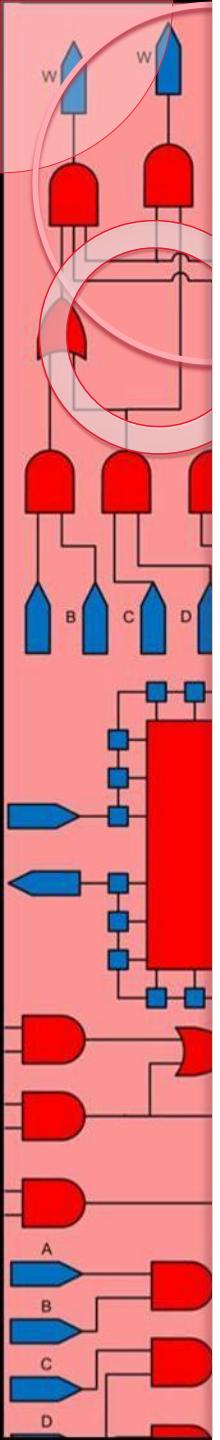
# Summary

- Handshaking definition
- Types of handshaking
  - Handshaking between two systems
  - Handshaking for accessing a shared bus
  - Memory handshaking
  - DMA mode or burst mode
- Handshaking with timing details
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran

# Basics of Digital Design at RT Level with Verilog


## Lecture 20: Inter RTL Communications

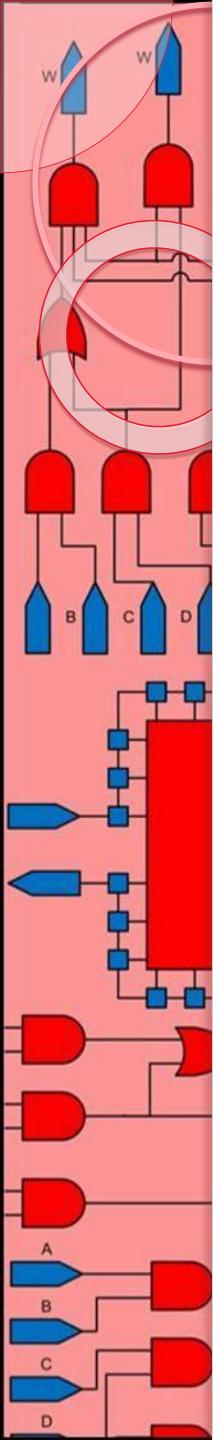


# Inter RTL Communications

- RTL Handshaking
- Arbitration
- Inter-RTL device communications
- Interfacing
- Signals from the controller
- Datapath and Controller design
- Verilog descriptions
- Summary



# Memory Interface: Design Example

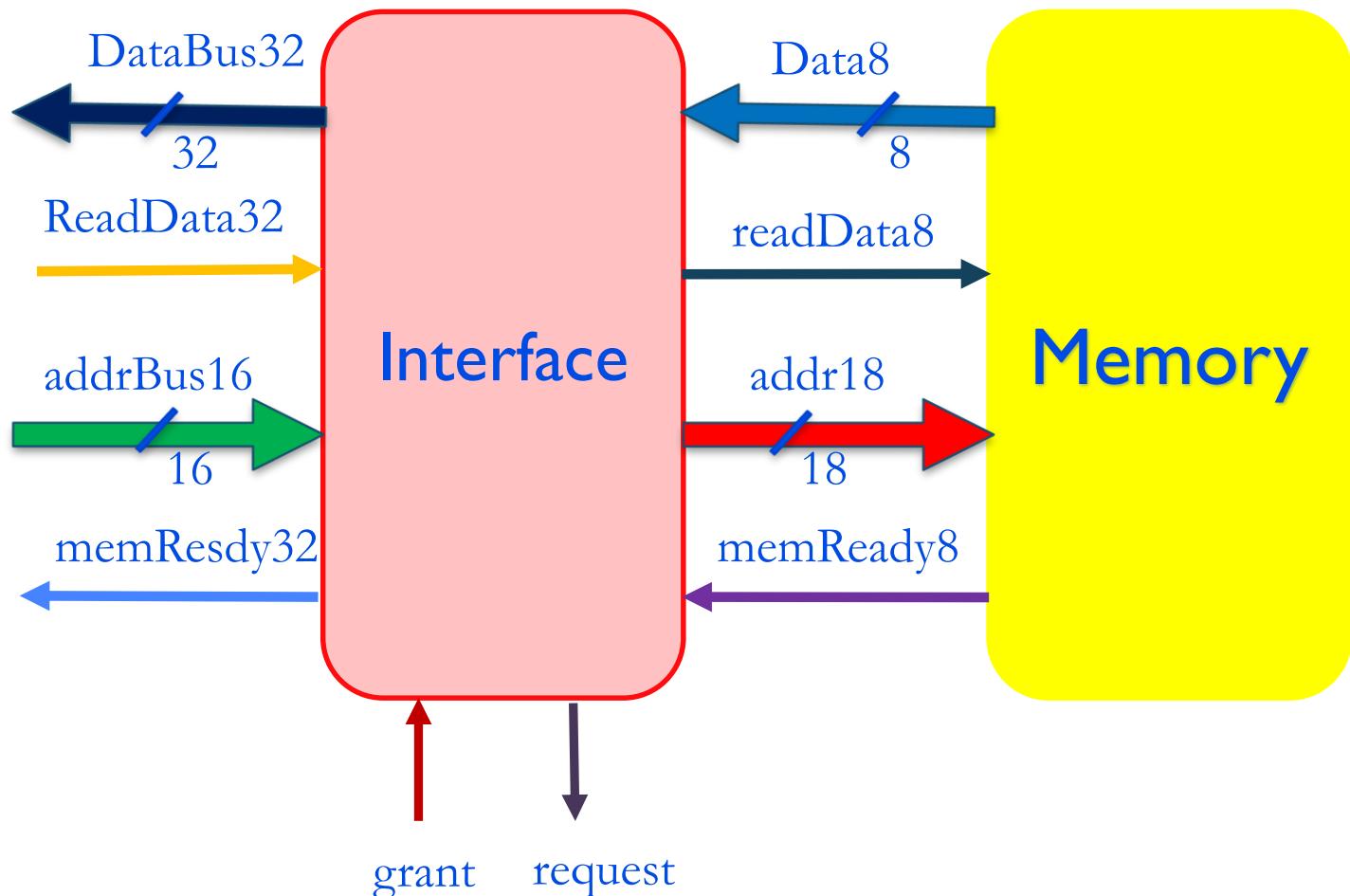

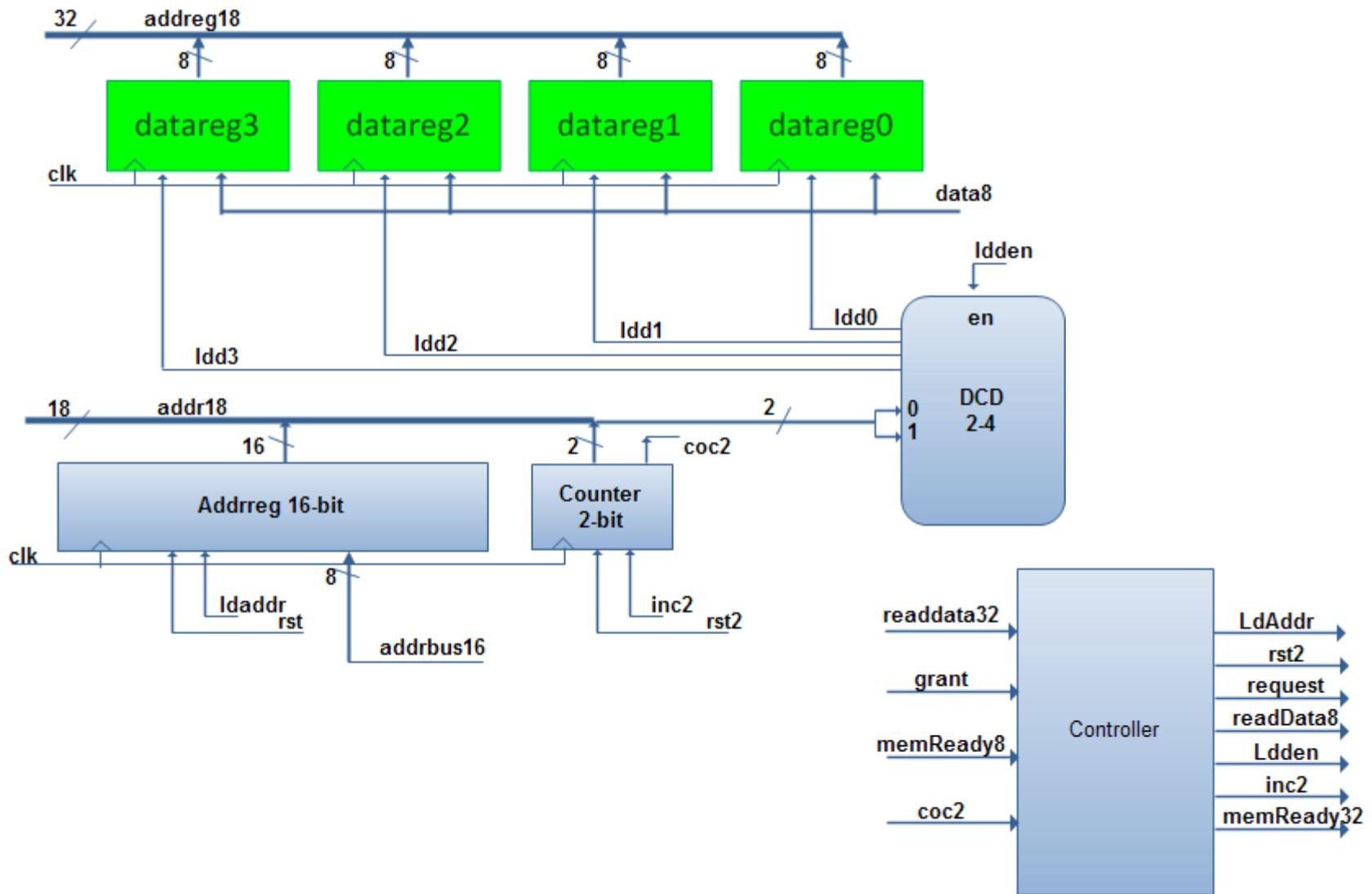
# Memory Interface: Datapath&Controller Partitioning



# Memory Interface: State Machine

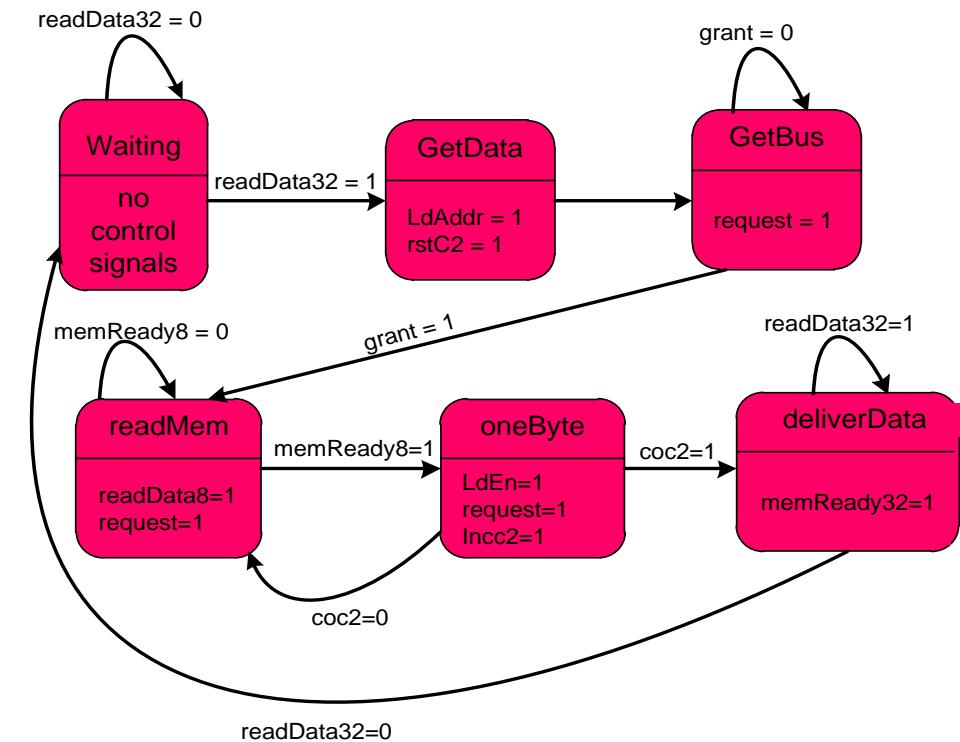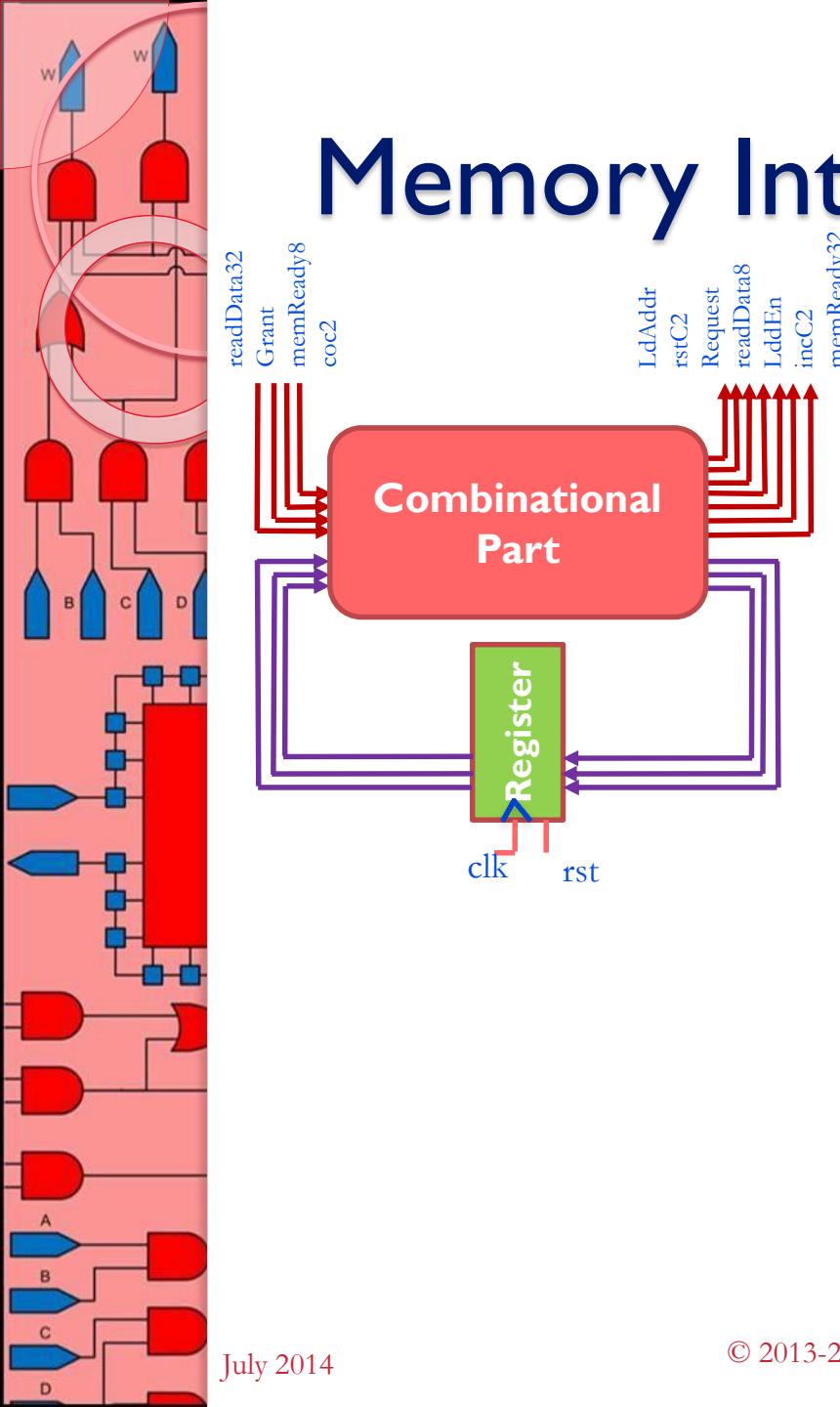

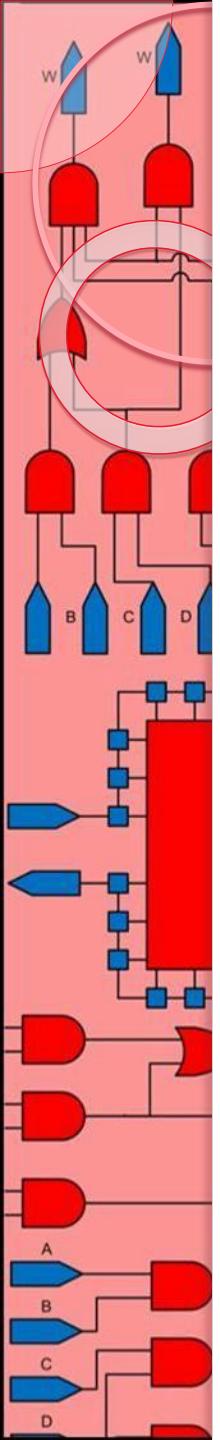


# Memory Interface: Datapath Verilog Code

```
module MI_datapath( input [15:0]addrbus16,input [7:0]data8, input clk, rst,
                     input ldaddr,incc2,rst2 ,ldden,
                     output [17:0]addr18,output [31:0]databus32,output reg coc2);

    wire [17:0] addreg18;
    reg [15:0] addreg16;
    reg [1:0] counter2;
    reg [3:0] ldd =0;
    reg [7:0]datareg0,datareg1,datareg2,datareg3;


    always @ (posedge clk, posedge rst)begin // 16-bit address register
        if (rst)
            addreg16 <=16'b0;
        if (ldaddr)
            addreg16 <= addrbus16;
    end

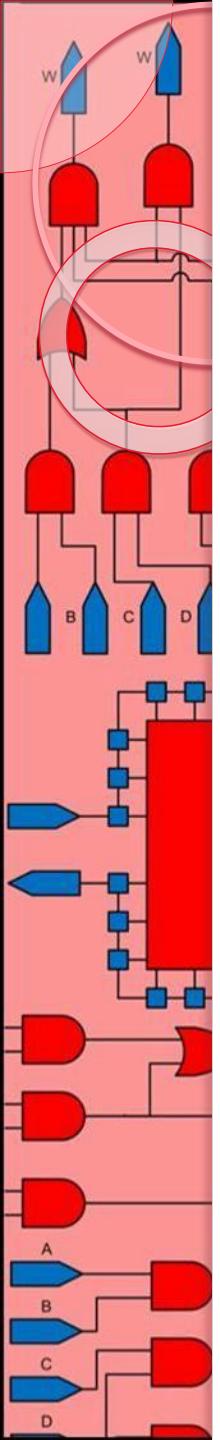    always @ (posedge clk, posedge rst2)begin // 2-bit counter
        if (rst2)
            counter2 <=2'b0;
        else if(incc2)
            {coc2, counter2} <=counter2 +1;
    end
endmodule
```



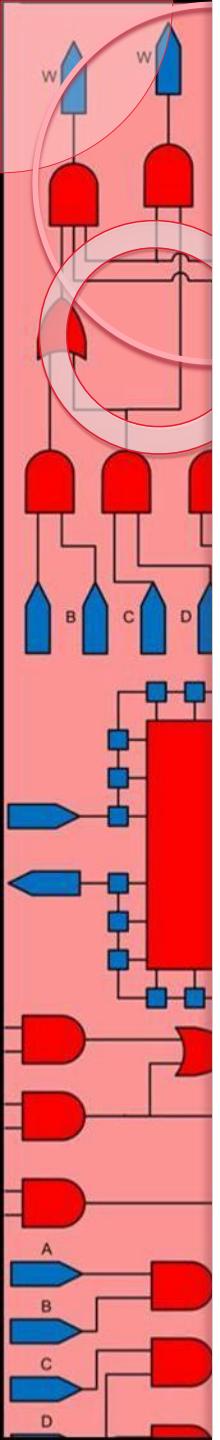
# Memory Interface: Datapath Verilog Code

```
//assign coc2=&{counter2,incc2};  
assign addreg18={addreg16,counter2}; // 18-bit address to memory  
assign addr18=addreg18;  
  
always @ (ldden)begin      // decoder  
    ldd = 4'b0000;  
    if(counter2==2'b00)  
        ldd[0] = 1;  
    else if(counter2==2'b01)  
        ldd[1] = 1;  
    else if(counter2==2'b10)  
        ldd[2] = 1;  
    else if(counter2==2'b11)  
        ldd[3] = 1;  
end
```


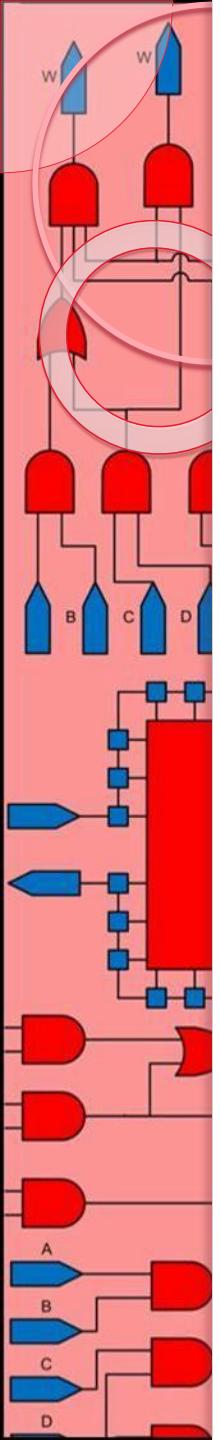
# Memory Interface: Datapath Verilog Code

```
always @ (posedge clk, posedge rst) begin
    if (rst)begin
        datareg0 <=8'b0;
        datareg1 <=8'b0;
        datareg2 <=8'b0;
        datareg3 <=8'b0;
    end
    else if(ldd[0])
        datareg0 <= data8;
    else if(ldd[1])
        datareg1 <= data8;
    else if(ldd[2])
        datareg2 <= data8;
    else if(ldd[3])
        datareg3 <= data8;
    end
    assign databus32={datareg3,datareg2,datareg1,datareg0};
endmodule
```




# Memory Interface: Controller Verilog Code

```
module MI_cu(input clk,rst,readdata32,grant,memready8,coc2,
              output reg ldaddr, rst2, request, readdata8,ldden,
              incc2,memready32);


    reg [2:0] ns,ps;

    always @ (ps,readdata32,grant,memready8,coc2)begin:comb
        ldaddr=1'b0;rst2=1'b0;request=1'b0;readdata8=1'b0;
        ldden=1'b0;incc2=1'b0;memready32=1'b0;
        case(ps)
            3'b000:
                if(readdata32)
                    ns=1;
                else
                    ns=0;
            3'b001:begin
                ns=2;ldaddr=1'b1;rst2=1'b1;
                end
            3'b010:begin
                if(grant)
                    ns=3;
                else
                    ns=2;request=1'b1;
                end
        endcase
    end
endmodule
```

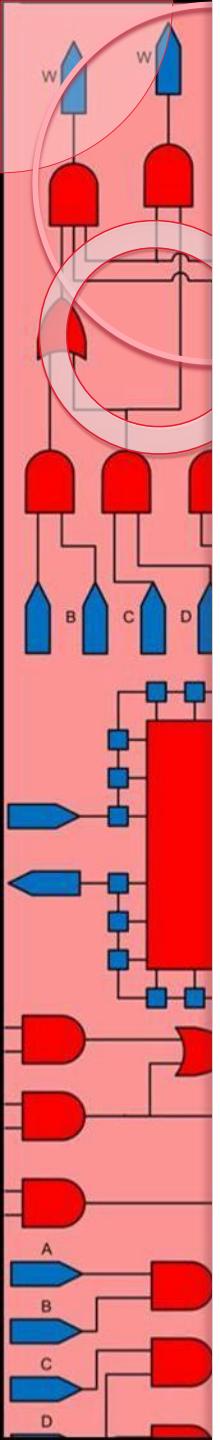

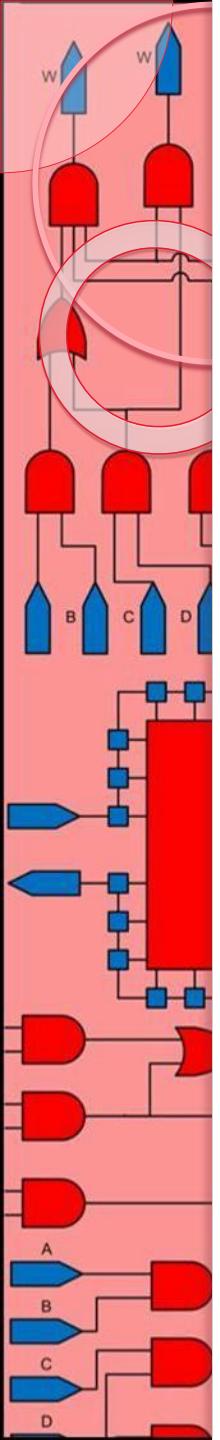
# Memory Interface: Controller Verilog Code

```
3'b011:begin
    if(memready8)
        ns=4;
    else ns=3;
        request=1'b1;
    end
3'b100:begin
    if(coc2)
        ns=5;
    else
        ns=3;ldden=1'b1;request=1'b1;incc2=1'b1;
    end
3'b101:begin
    if(readdata32)
        ns=5;
    else
        ns=0;memready32=1'b1;
    end
default:begin
    ns=0;ldaddr=1'b0;rst2=1'b0;
    request=1'b0;readdata8=1'b0;
    ldden=1'b0;incc2=1'b0;memready32=1'b0;
end
endcase
end
```


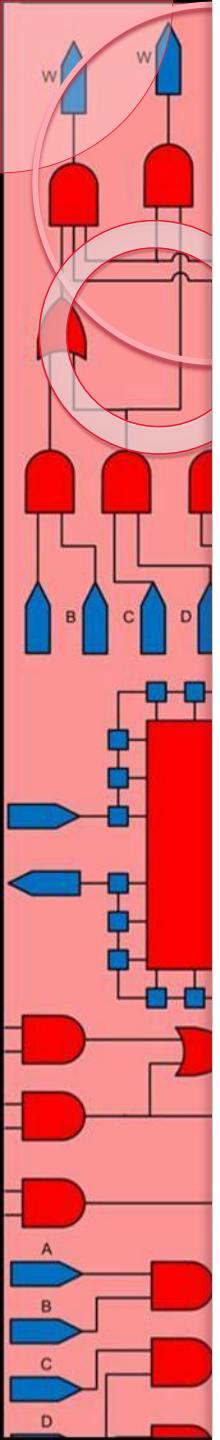
# Memory Interface: Controller Verilog Code

```
always@ (posedge clk,posedge rst)begin:seq
    if(rst)
        ps<=3'b0;
    else
        ps<=ns;
end
endmodule
```




# Memory Interface: Complete System Verilog Code

```
module MI_system(    input readdata32,grant,memready8,clk,rst,
                     input [15:0] addrbus16,
                     input [7:0]data8,output [31:0] databus32,
                     output [17:0]addr18 ,
                     output memready32, request, readdata8);
  wire coc2;
  wire incc2,ldaddr,ldden,rst2;

  MI_cu  U1 ( clk,rst,readdata32,grant,memready8, coc2, ldaddr,
               rst2, request, readdata8,ldden,incc2,memready32);


  MI_datapath U2 (addrbus16, data8, clk, rst, ldaddr,incc2,rst2,
                  ldden, addr18, databus32,coc2);

endmodule
```

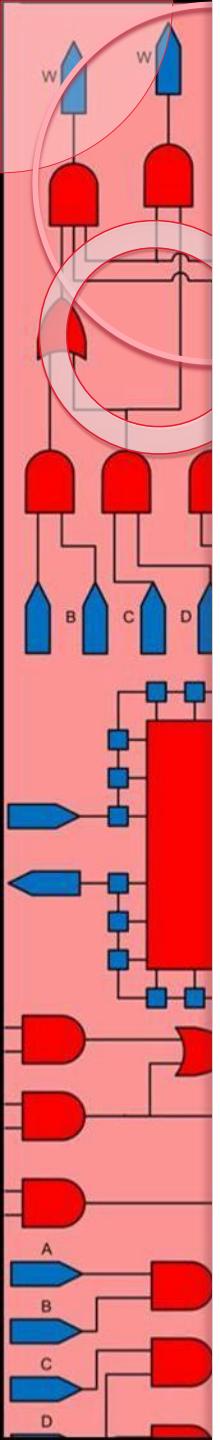
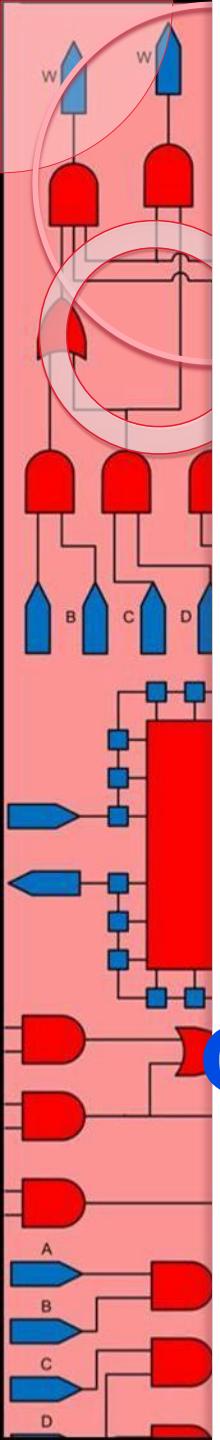
# Inter RTL Communications

- RTL Handshaking
- Arbitration
- Inter-RTL device communications
- Interfacing
- Signals from the controller
- Datapath and Controller design
- Verilog descriptions
- Summary




Lecture Series:  
Basics of Digital Design at RT Level with Verilog

Z. Navabi, University of Tehran


# Basics of Digital Design at RT Level with Verilog
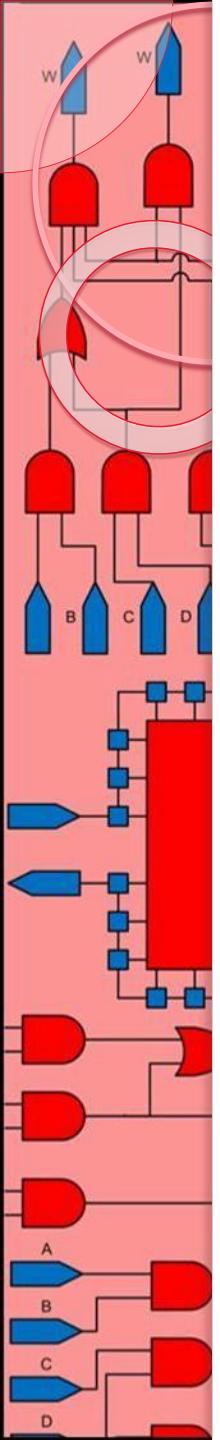
## Lecture 21: Complete RTL: Processing Elements and Communications





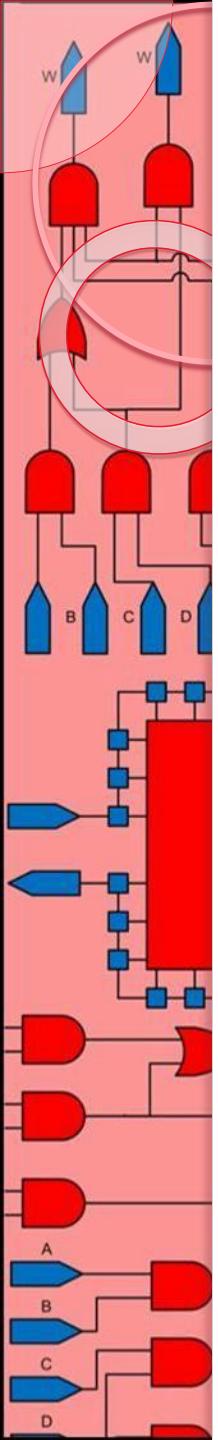
# RTL Processing Elements and Communications


- Overview
- PE and IO wrappers
- A PE example (includes Verilog)
  - Datapath controller partitioning
  - Datapath design
  - Controller design
- IO wrappers
  - Datapath controller partitioning
  - Datapath design
  - Controller design
- Summary




# Bus Based Design

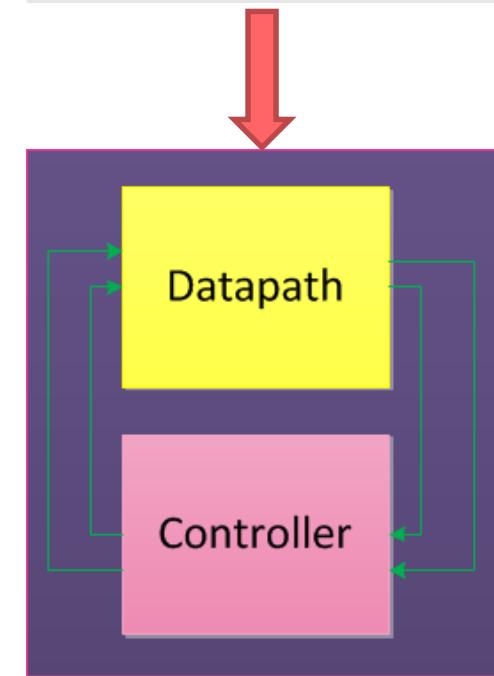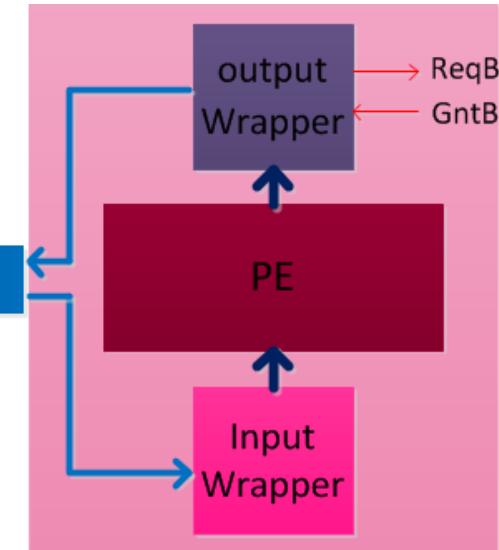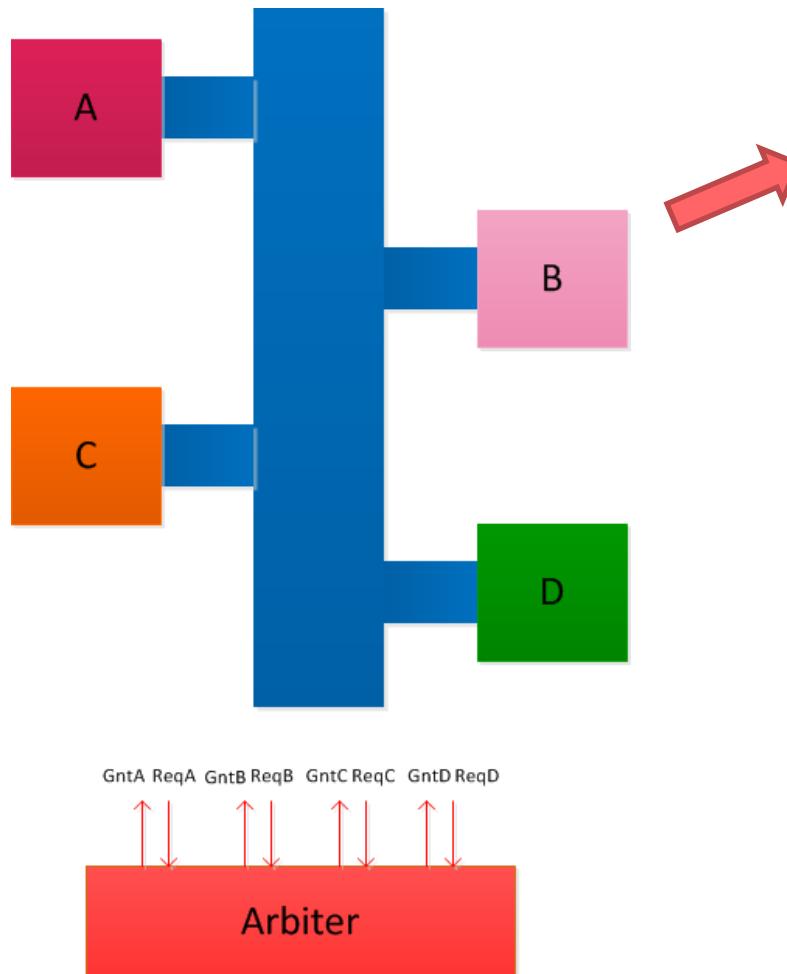


# Exponentiation Module: Design Example

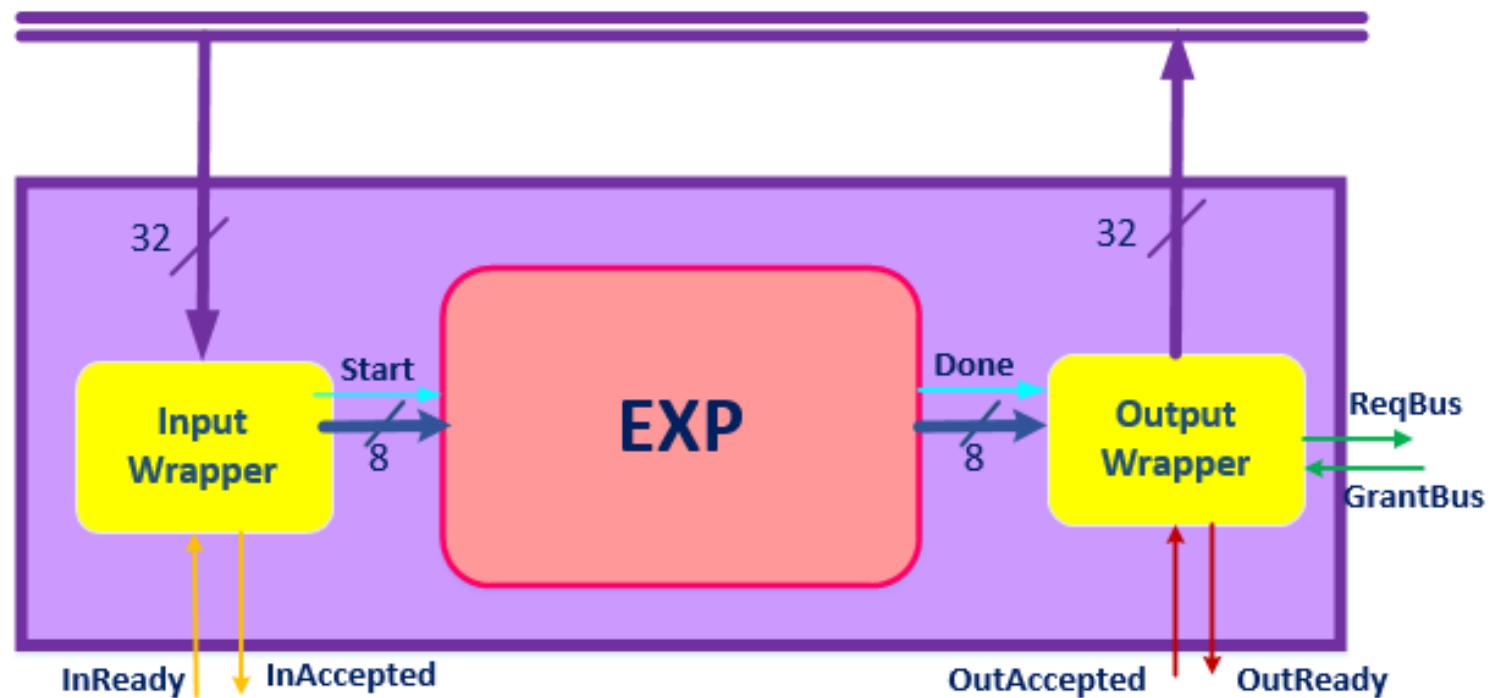

# Exponentiation Module

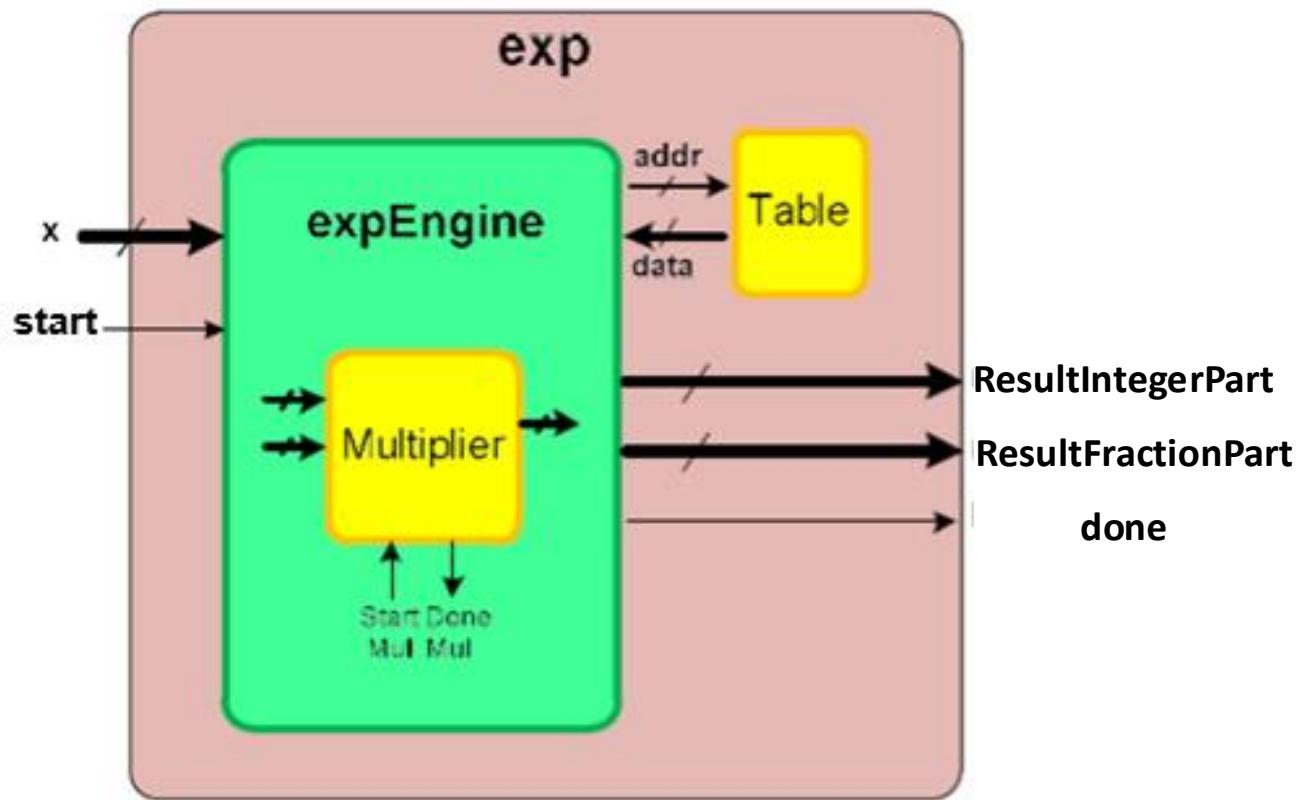

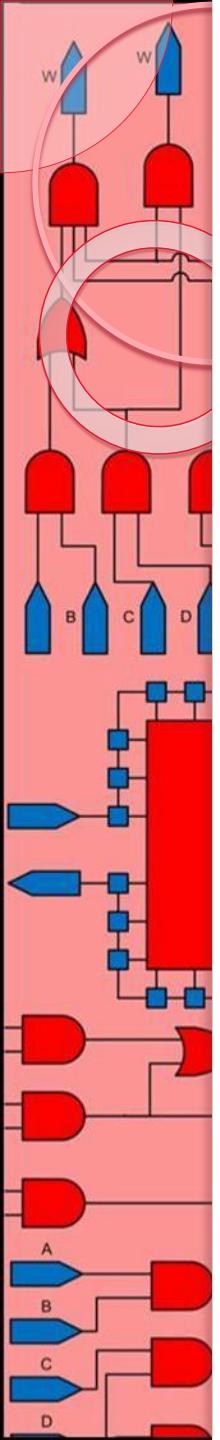


# Exponential Function Algorithm


$$e^x = \sum_{k=0}^{\infty} \frac{x^k}{k!}$$

```
e = 1;  
a = 1;  
for( i = 1; i < n; i++ ) {  
    a = a * x * ( 1 / i );  
    e = e + a;  
}
```


# Datapath / Controller

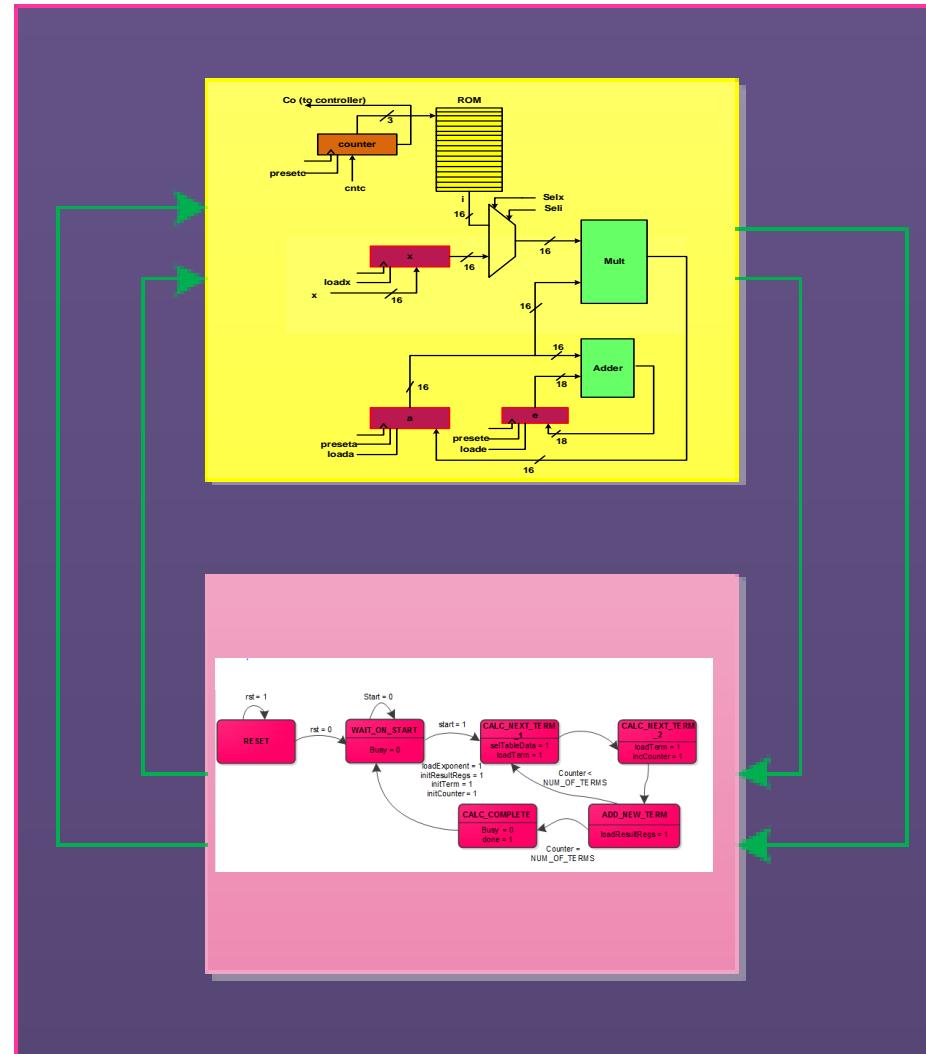


# Datapath

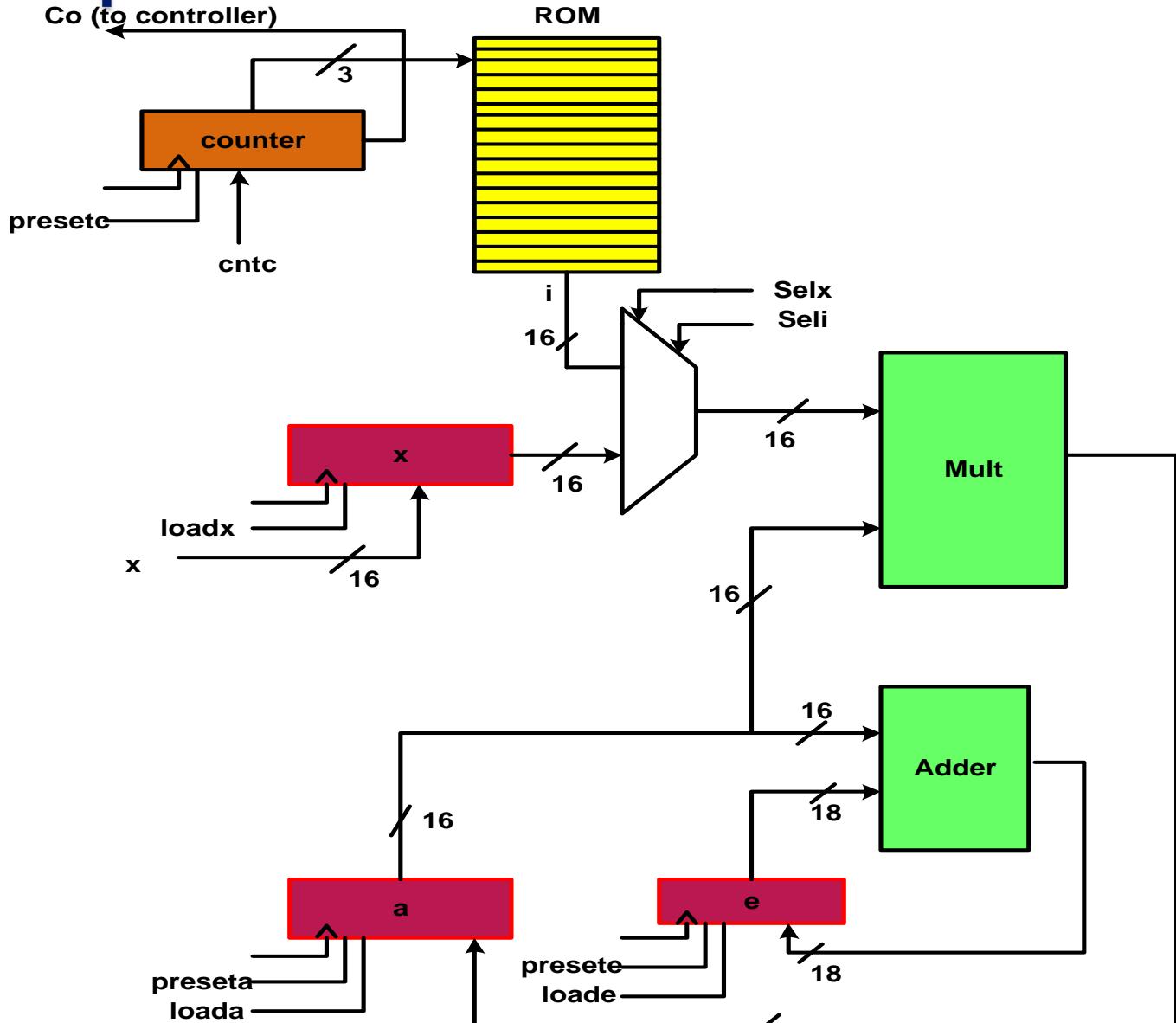

# Controller

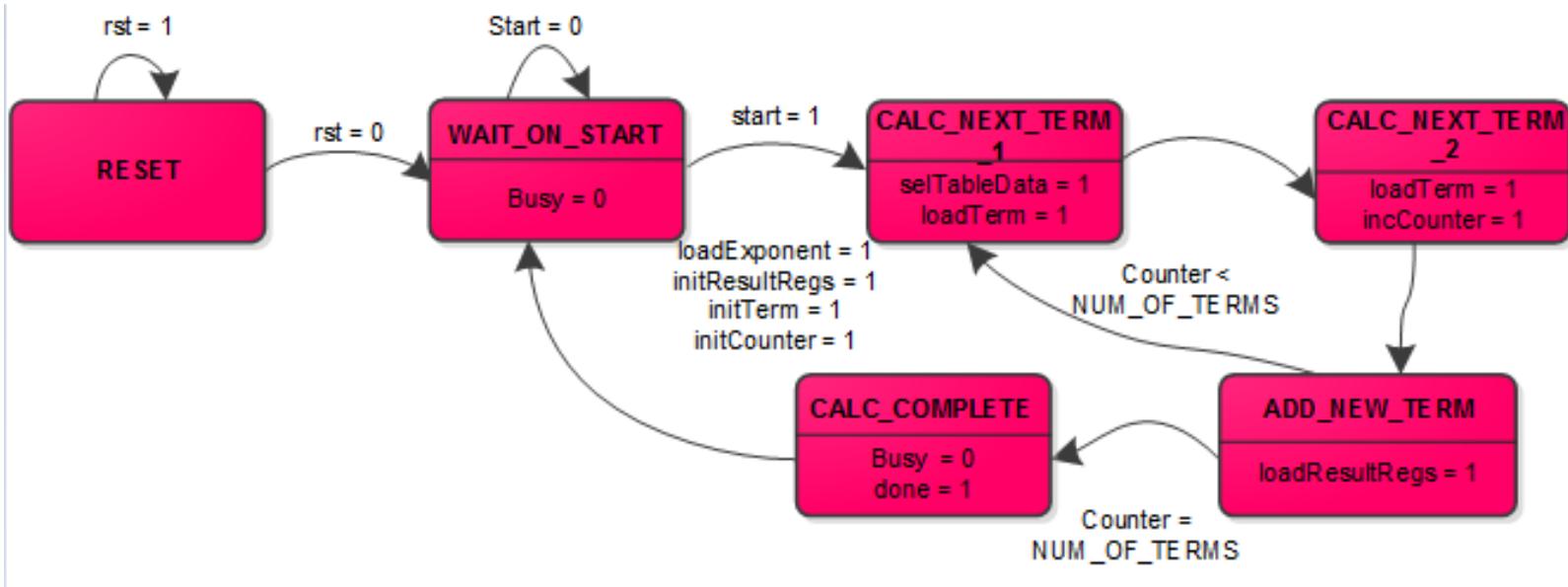

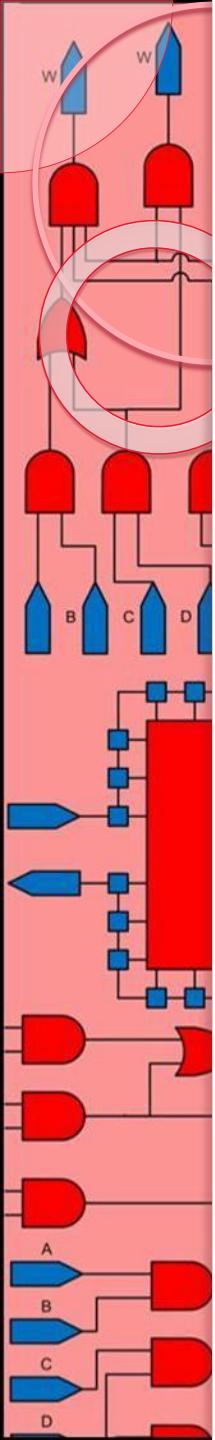


# Exponentiation Module :

Datapath Verilog Code

```
'define RESET          0
`define WAIT_ON_START    1
`define CALC_NEXT_TERM_1    2
`define CALC_NEXT_TERM_2    3
`define ADD_NEW_TERM      4
`define CALC_COMPLETE      5


module expEngine  ( clk, rst, start, x, busy, done, addr,
...                                tableData, resultIPart, resultFFPart );
parameter F_WIDTH = 16;
parameter NUM_OF_TERMS = 8;
parameter CNT_WIDTH = 4;
input   clk, rst, start;
input [F_WIDTH - 1:0] x;
output  busy, done;
output [CNT_WIDTH - 1:0] addr;
input  [F_WIDTH - 1:0] tableData;
output [1:0 ] resultIPart;
output [F_WIDTH - 1:0 ]resultFFPart;
reg [F_WIDTH - 1:0] exponent;
reg [F_WIDTH - 1:0] term;
reg [1:0 ] resultIPart;
reg [F_WIDTH - 1:0 ]resultFFPart;
wire [F_WIDTH * 2 - 1:0 ] multResult;
reg [F_WIDTH - 1:0 ] multRInput;
wire [F_WIDTH + 1:0] addResult;
reg [CNT_WIDTH - 1:0] counter;
```

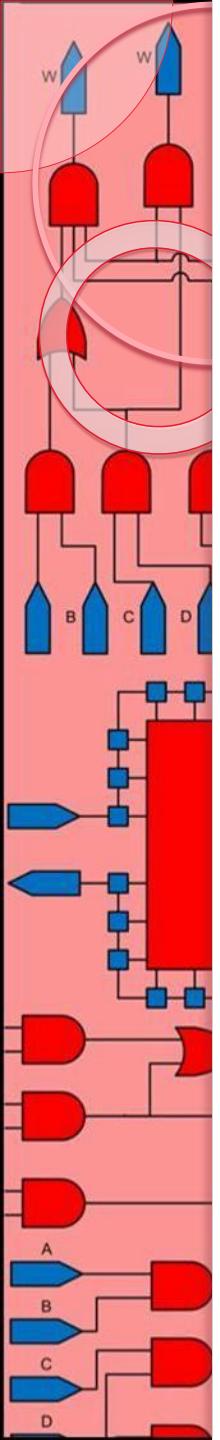

# Exponentiation Module
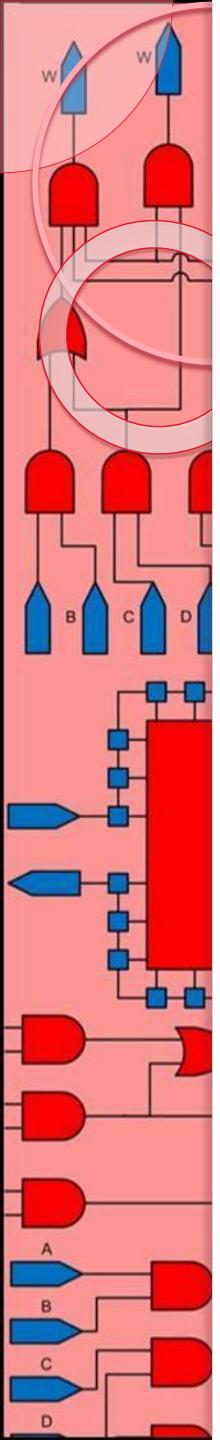
## Datapath Verilog Code

```
reg [2:0] pState, nState;  
//=====  
//Datapath  
//=====  
//Exponent register  
always @(posedge clk) begin  
    if( rstExponent )  
        exponent <= 0;  
    else if( loadExponent )  
        exponent <= x;  
end  
//Term register: register storing one of terms in Tailor series  
always @(posedge clk) begin  
    if( rstTerm )  
        term <= 0;  
    else if( initTerm )  
        term <= 32'hFFFFFFF;  
    else if( loadTerm )  
        term <= multResult [F_WIDTH * 2 - 1: F_WIDTH];  
end  
//Multiplexer on the right input of the multiplier  
always @(* selTableData or tableData or exponent) begin  
    if( selTableData )  
        multRInput <= tableData;  
    else  
        multRInput <= exponent;  
end  
//Multiplier  
assign multResult = term * multRInput ;
```




# Exponentiation Module

## Datapath Verilog Code

```
assign addResult = term + { resultIPart, resultFFPart };
//Registers storing integral part and fractional parts of the result
always @(posedge clk) begin
    if( rstResultRegs )
        { resultIPart, resultFFPart } <= 0;
    else if( initResultRegs ) begin
        resultIPart <= 1;
        resultFFPart <= 0;
    end
    else if( loadResultRegs )
        { resultIPart, resultFFPart } <= addResult;
end

//Counter
always @(posedge clk) begin
    if( rstCounter )
        counter <= 0;
    else if( initCounter )
        counter <= 1;
    else if( incCounter )
        counter <= counter + 1;
end


assign addr = counter;
```

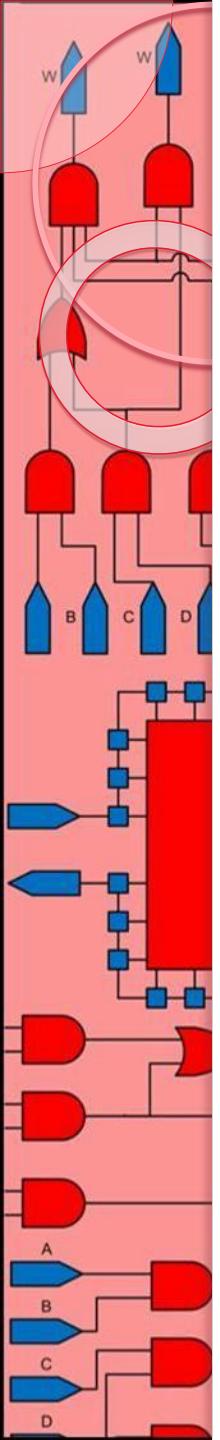

# Exponentiation Module :
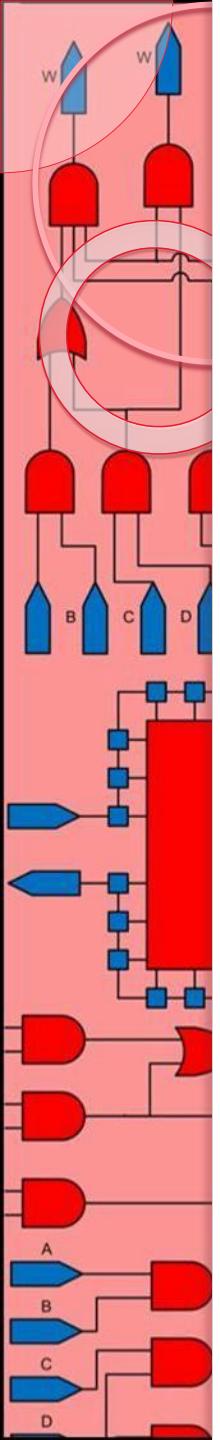
## Combinational Table Verilog Code

```
module Table ( addr, tableData );
    parameter ADDR_WIDTH = 3;
    parameter F_WIDTH = 16;
    input [ADDR_WIDTH - 1:0] addr;
    output [F_WIDTH - 1:0] tableData;
    reg [31:0]temp;
    always @ ( addr ) begin
        temp <= 0;
        case ( addr )
            0: temp <= 32'h00000000;
            1: temp <= 32'hFFFFFF; //Fixed point representation of 1
            2: temp <= 32'h80000000; //Fixed point representation of 1/2
            3: temp <= 32'h55555555; //Fixed point representation of 1/3
            4: temp <= 32'h40000000; //Fixed point representation of 1/4
            5: temp <= 32'h33333333; //Fixed point representation of 1/5
            6: temp <= 32'h2AAAAAAA; //Fixed point representation of 1/6
            7: temp <= 32'h24924924; //Fixed point representation of 1/7
            8: temp <= 32'h20000000; //Fixed point representation of 1/8
            9: temp <= 32'h1C71C71C; //Fixed point representation of 1/9
            10: temp <= 32'h19999999; //Fixed point representation of 1/10
            11: temp <= 32'h1745D174; //Fixed point representation of 1/11
            12: temp <= 32'h15555555; //Fixed point representation of 1/12
            13: temp <= 32'h13B13B13; //Fixed point representation of 1/13
            14: temp <= 32'h12492492 ; //Fixed point representation of 1/14
            15: temp <= 32'h11111111; //Fixed point representation of 1/15
        endcase
    end
    assign tableData = temp[31: 31 - F_WIDTH + 1];
endmodule
```




# Exponentiation Module :
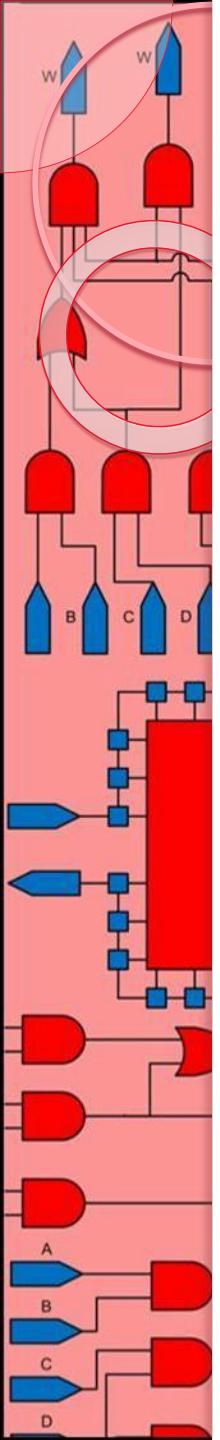
## Controller Verilog Code

```
//=====
//Controller
//=====


    always @( pState or rst or start or counter ) begin
        nState <= 'RESET;
        loadExponent <= 1'b0;
        rstExponent <= 1'b0;
        loadTerm <= 1'b0;
        rstTerm <= 1'b0;
        initTerm <= 1'b0;
        selTableData <= 1'b0;
        rstResultRegs <= 1'b0;
        initResultRegs <= 1'b0;
        loadResultRegs <= 1'b0;
        initResultRegs <= 1'b0;
        incCounter <= 1'b0;
        rstCounter <= 1'b0;
        initCounter <= 1'b0;
        busy <= 1'b1;
        done <= 1'b0;
```



# Exponentiation Module :
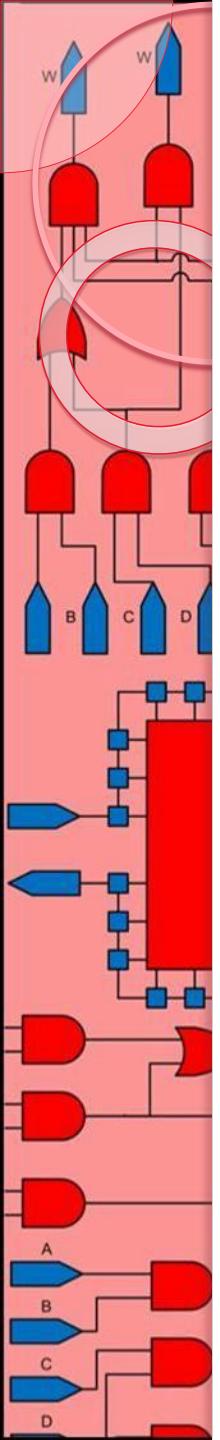
## Controller Verilog Code

```
case ( pState )
`RESET : begin
    rstExponent <= 1'b1;
    rstTerm <= 1'b1;
    rstResultRegs <= 1'b1;
    rstCounter <= 1'b1;
    busy <= 1'b0;
    done <= 1'b0;
    if( rst )
        nState <= `RESET;
    else
        nState <= `WAIT_ON_START;
end
`WAIT_ON_START: begin
    busy <= 1'b0;
    if( start ) begin
        loadExponent <= 1'b1;
        initResultRegs <= 1'b1;
        initTerm <= 1'b1;
        initCounter <= 1'b1;
        nState <= `CALC_NEXT_TERM_1;
    end
    else
        nState <= `WAIT_ON_START;
end
```



# Exponentiation Module :

## Controller Verilog Code

```
    `CALC_NEXT_TERM_1: begin
        selTableData <= 1'b1;
        loadTerm <=1'b1;
        nState <= `CALC_NEXT_TERM_2;
    end


    `CALC_NEXT_TERM_2: begin
        loadTerm <=1'b1;
        incCounter <= 1'b1;
        nState <= `ADD_NEW_TERM;
    end

    `ADD_NEW_TERM: begin
        loadResultRegs <= 1'b1;
        if( counter < NUM_OF_TERMS )
            nState <= `CALC_NEXT_TERM_1;
        else
            nState <= `CALC_COMPLETE;
    end

    `CALC_COMPLETE: begin
        busy <= 1'b0;
        done <= 1'b1;
        nState <= `WAIT_ON_START;
    end

endcase

end
```

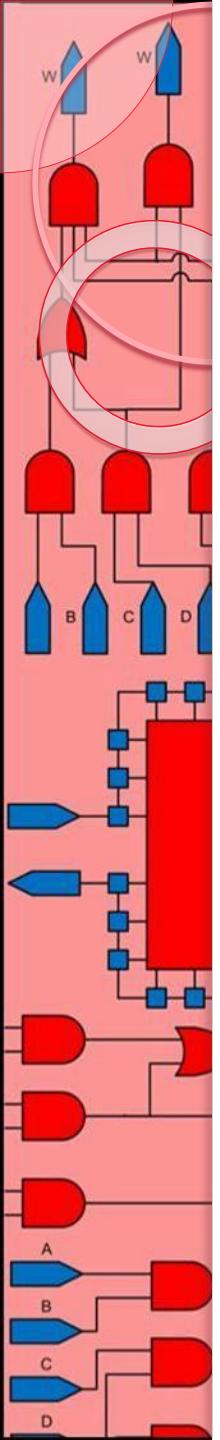

# Exponentiation Module :

## Complete System Verilog Code

```
module exp ( clk, rst, start, x, busy, done, resultIPart, resultFFPart );
    parameter F_WIDTH = 16;
    parameter NUM_OF_TERMS = 7;
    parameter CNT_WIDTH = 3;
    input    clk, rst, start;
    input    [F_WIDTH - 1:0] x;
    output   busy, done;
    output   [1:0 ] resultIPart;
    output   [F_WIDTH - 1: 0 ]resultFFPart;
    wire     [CNT_WIDTH - 1:0] addr;
    wire     [F_WIDTH - 1: 0 ] tableData;


    expEngine #( F_WIDTH, NUM_OF_TERMS, CNT_WIDTH )
        expEngine1( clk, rst, start, x, busy, done, addr,
                    tableData, resultIPart, resultFFPart );

    Table   #( CNT_WIDTH, F_WIDTH )
        Table1( addr, tableData );

endmodule;
```


# Input Wrapper:


## Datapath & Controller Partitioning

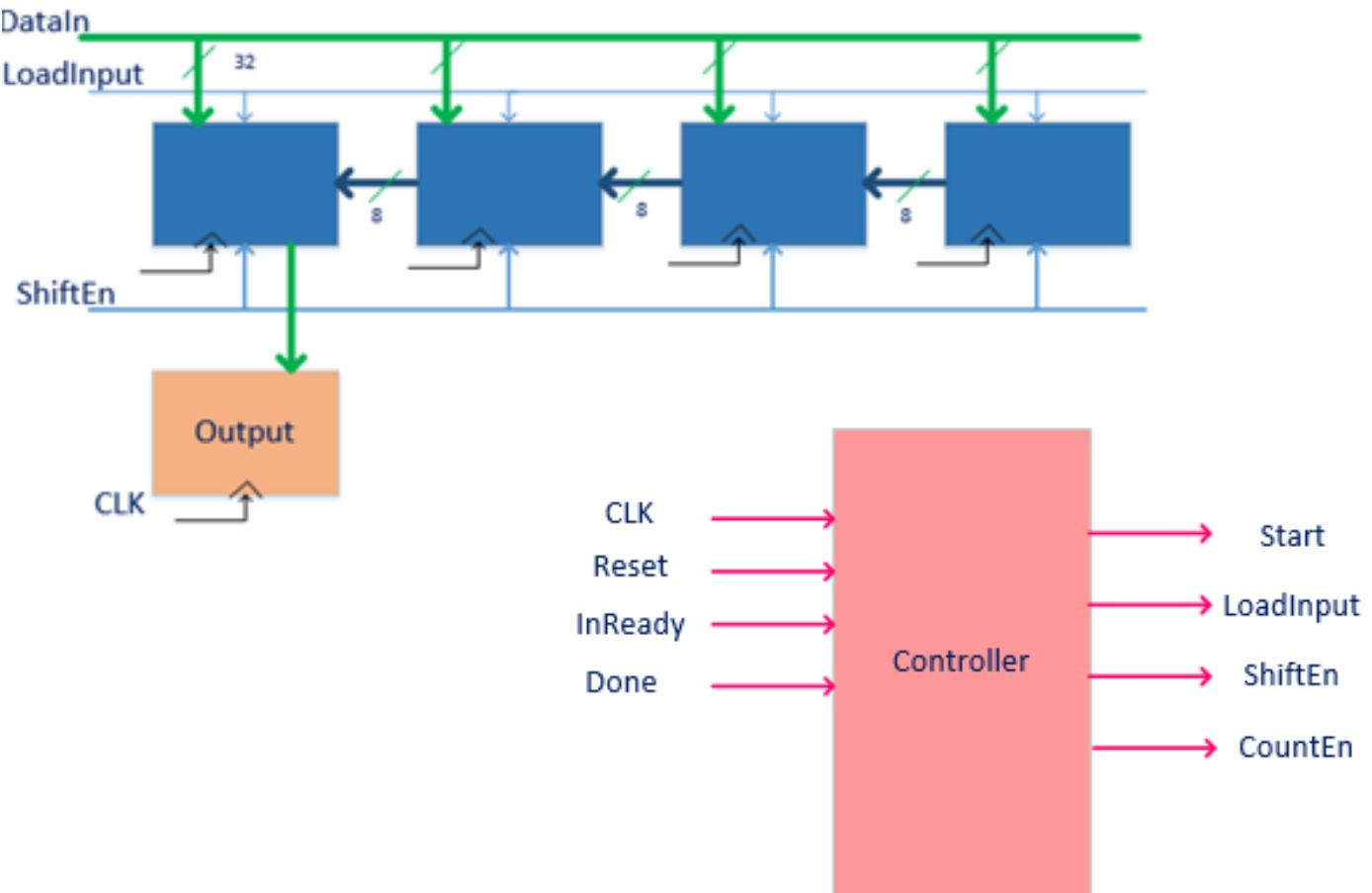

# Input Wrapper:

## State Machine

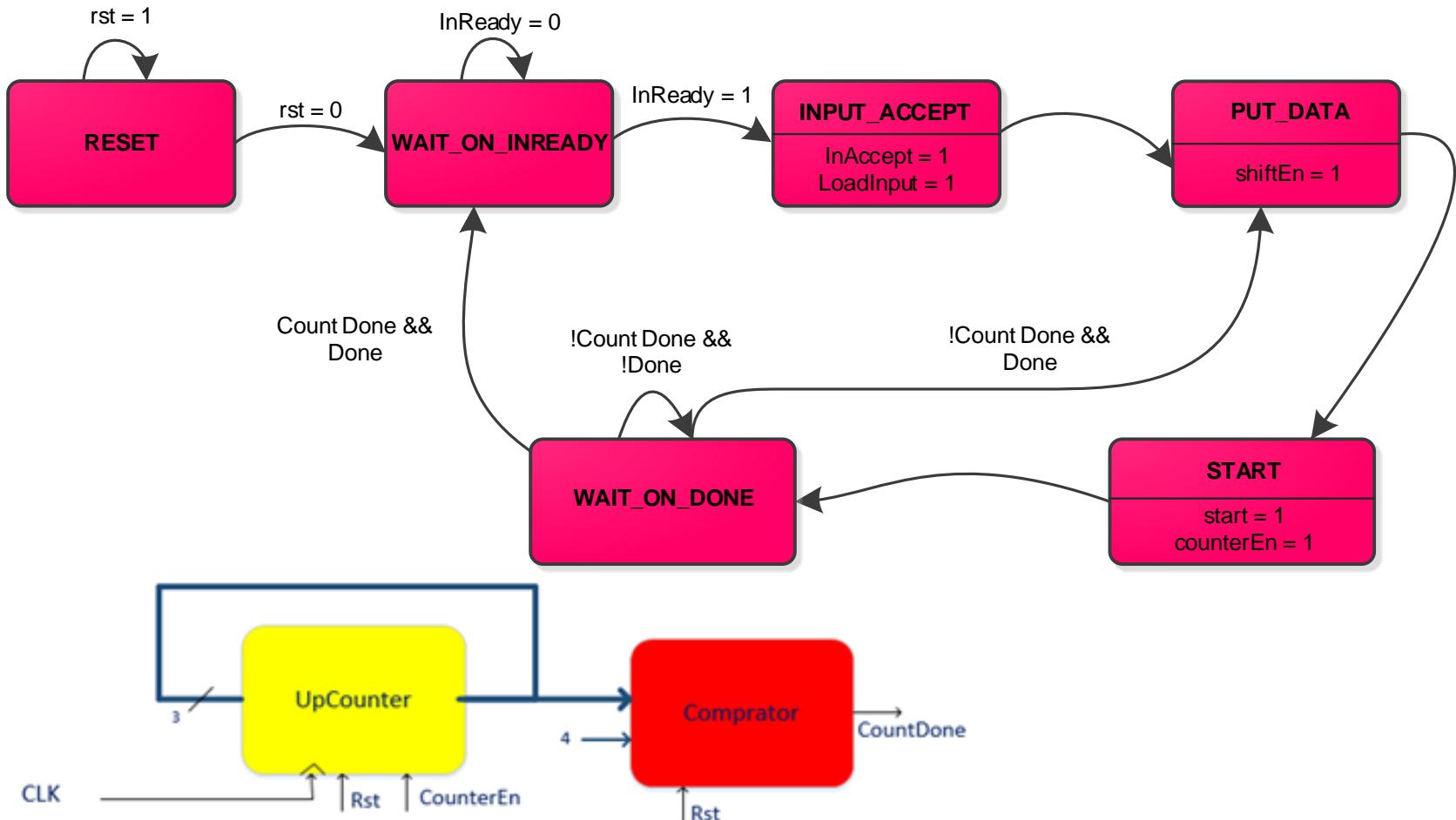


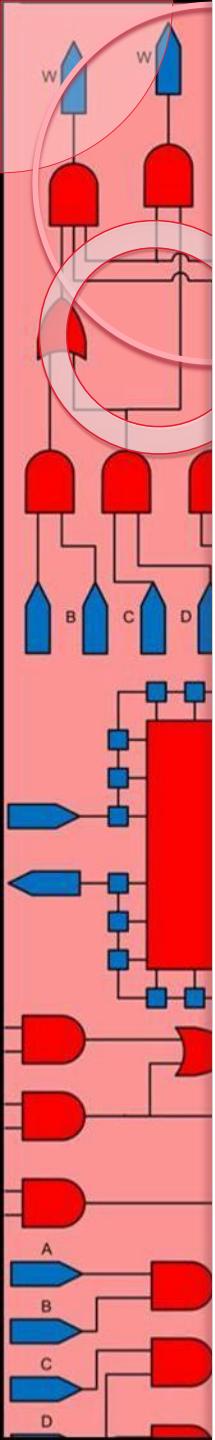

# Input Wrapper :
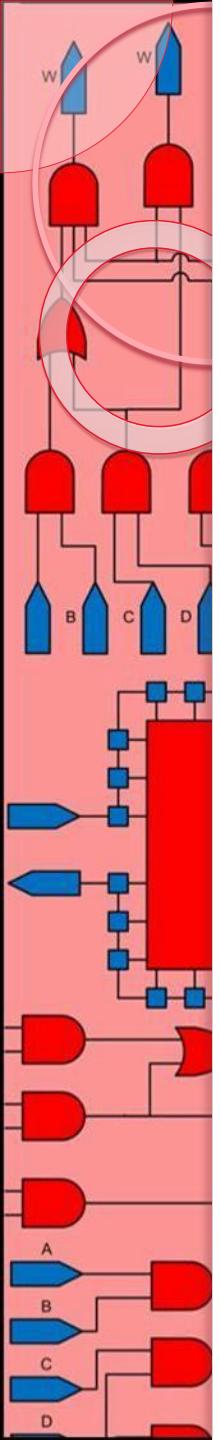
## Datapath Verilog Code

```
module inputDatapath( clk, rst, loadInput, shiftEn, countEn, dataIn,
    parameter BUS_SIZE = 32;
    parameter DATA_SIZE = 8;
    parameter NUM_REGS = 4;
    input                                clk, rst,shiftEn, loadInput, countEn;
    input      [BUS_SIZE - 1:0]   dataIn;
    output     [DATA_SIZE - 1:0]  dataOut;
    reg       [DATA_SIZE - 1:0]  buffer [NUM_REGS-1:0];
    reg
    integer                           first;
    i;
]//=====
//Datapath
//=====
//input buffer
always @ (posedge clk ) begin
    if( rst ) begin
        for ( i = 0; i < NUM_REGS ; i = i+1 )begin
            buffer[i] <= 0;
        end
    end
    else if( loadInput ) begin
        {buffer[NUM_REGS-1], buffer[NUM_REGS-2],
        buffer[NUM_REGS-3], buffer[NUM_REGS-4]} <= dataIn;
    end
    else if( shiftEn && countEn!=0 ) begin
        for ( i = NUM_REGS-1; i > 0 ; i = i-1 )begin
            buffer[i] <= buffer[i-1];
        end
    end
end
assign dataOut = buffer[NUM_REGS-1];
endmodule;
```



# Input Wrapper :


## Controller Verilog Code

```
'define RESET          0
`define WAIT_ON_INREADY 1
`define INPUT_ACCEPT   2
`define PUT_DATA        3
`define START           4
`define WAIT_ON_DONE    5

module inputController ( clk, rst, inReady, done,
                        inAccepted, start, loadInput, shiftEn, countEn );
parameter     DATA_SIZE = 8;

input          clk, rst, inReady, done;
output reg      inAccepted, start, shiftEn, loadInput;
output          countEn;
reg            [2:0] ns, ps;
reg            [2:0] count;
reg            counterEn, countDone;

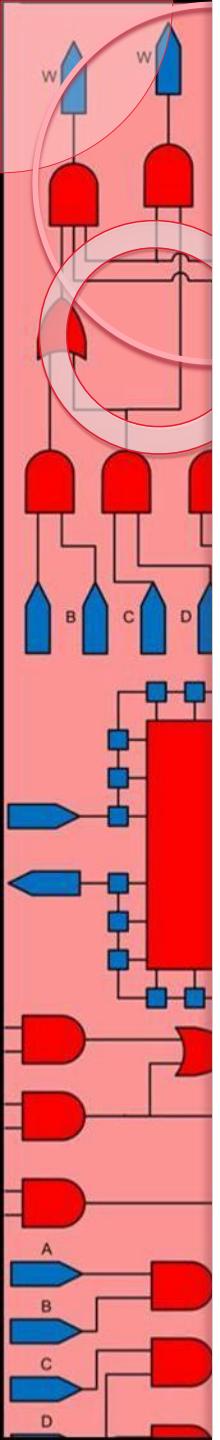//combinational part
always @ ( ps or inReady or done or rst or countDone ) begin
inAccepted = 0;
start = 0;
shiftEn = 0;
counterEn = 0;
loadInput = 0;
case ( ps )
  `RESET: begin
    if ( rst == 0 )
      ns = `WAIT_ON_INREADY;
    else
      ns = `RESET;
  end
end
```




# Input Wrapper :
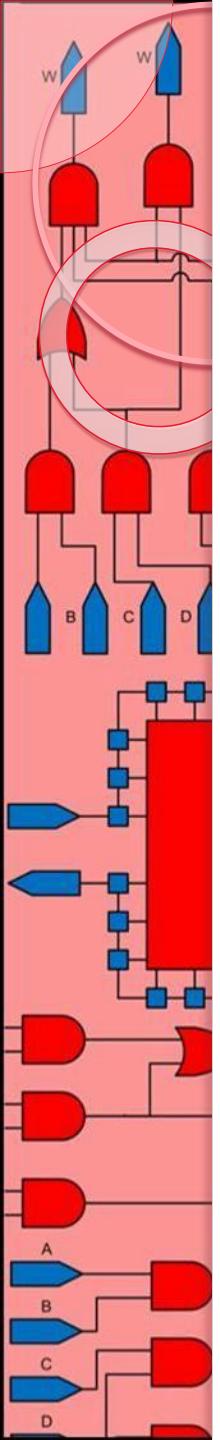
## Controller Verilog Code

```
'WAIT_ON_INREADY: begin
    if ( inReady == 1 )
        ns = `INPUT_ACCEPT;
    else
        ns = `WAIT_ON_INREADY;
end
`INPUT_ACCEPT: begin
inAccepted = 1;
loadInput = 1;
ns = `PUT_DATA;
end
`PUT_DATA:begin
shiftEn = 1;
ns = `START;
end
`START:begin
start = 1;
counterEn = 1;
ns = `WAIT_ON_DONE;
end
`WAIT_ON_DONE:begin
if (countDone && done)
    ns = `WAIT_ON_INREADY;
else if (done)
    ns = `PUT_DATA;
else if (!done)
    ns = `WAIT_ON_DONE;
end
endcase
end
```

```
'define
`define
`define
`define
`define
`define
`define
module i
...
para
input
output
output
reg
reg
reg
//cc
always
inAc
star
shif
coun
load
case
```




# Input Wrapper :
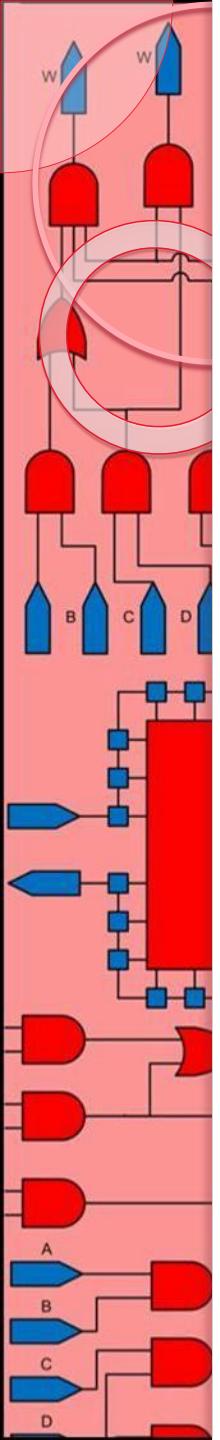
## Controller Verilog Code

```
//sequential part
always @ ( posedge clk ) begin
    if ( rst == 1 )
        ps <= `RESET;
    else
        ps <= ns;
end
//Up Counter
always @ ( posedge clk ) begin
    if( rst )
        count <= 0;
    else if( counterEn )
        count <= count + 1;
end

//Comparator
always @ ( count ) begin
    if( rst )
        countDone = 0;
    else if ( count==4 ) begin
        countDone = 1;
        count = 0;
    end
    else
        countDone = 0;
end
    assign countEn = 1 ? (count!=0) : 0;
endmodule
```



# Input Wrapper :

## Complete Verilog Code

```
module inputWrapper ( clk, rst, dataIn, inReady, busy, done, inAccepted, start, dataOut );

parameter BUS_SIZE = 32;
parameter DATA_SIZE = 8;



input          clk, rst, inReady, busy, done;
input  [BUS_SIZE-1:0] dataIn;
output [DATA_SIZE-1:0] dataOut;
output          inAccepted, start;
wire           shiftEn, loadInput, countEn;

inputDatapath #(BUS_SIZE, DATA_SIZE) datapath
( clk, rst , loadInput, shiftEn, countEn, dataIn, dataOut );

inputController #(DATA_SIZE)
controller( clk, rst, inReady, done, inAccepted,
           start, loadInput, shiftEn, countEn);
endmodule;
```


# Output Wrapper:


## Datapath & Controller Partitioning

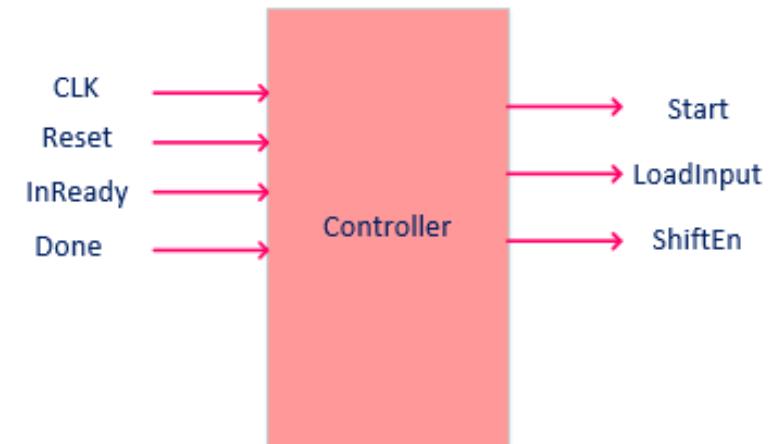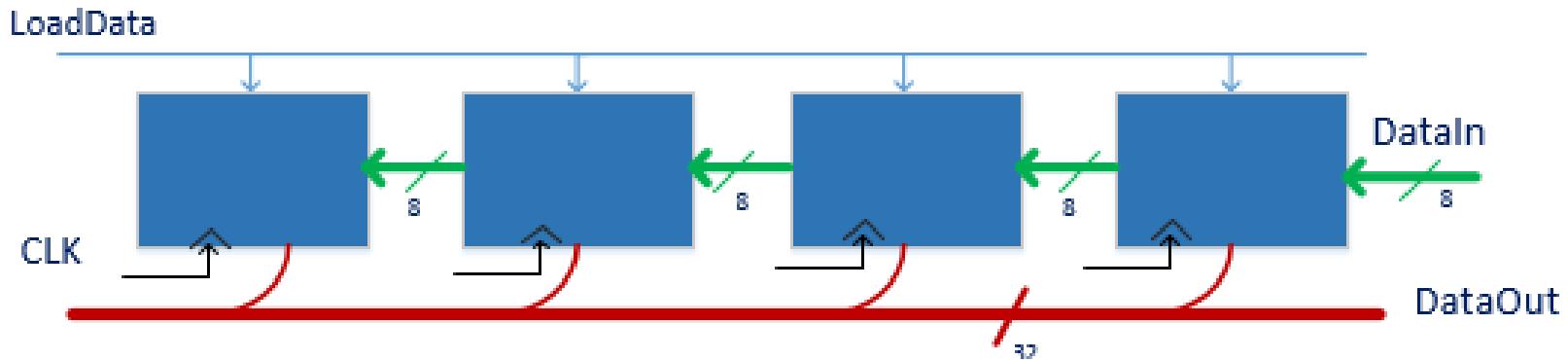

# Output Wrapper:

## State Machine

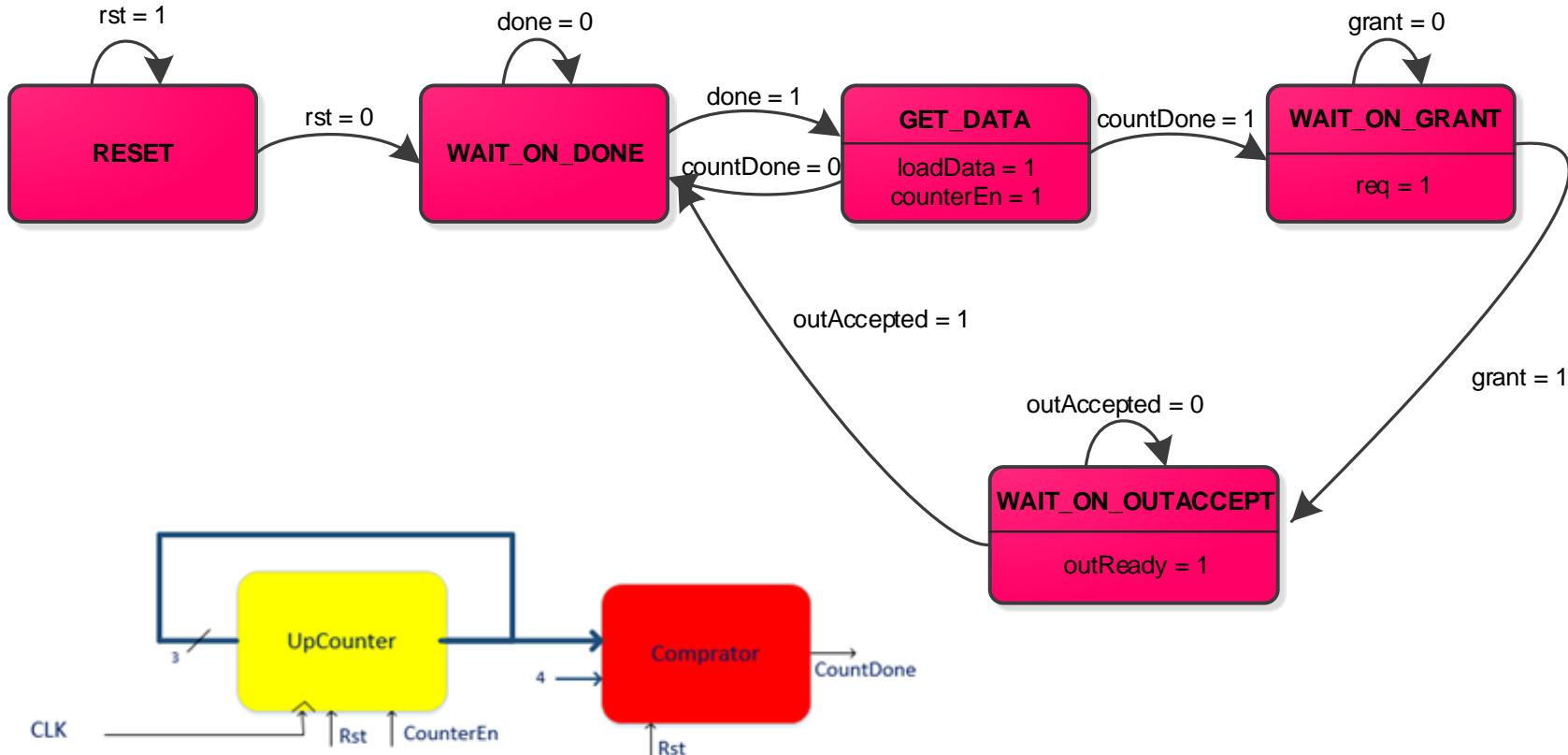

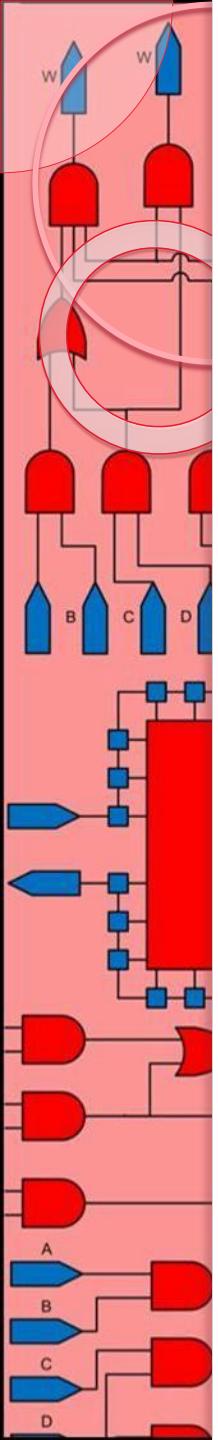


# Output Wrapper : Datapath Verilog Code

```
module outputDatapath      ( clk, rst, done, outAccepted,
                               loadData, dataIn, dataOut );

  parameter      BUS_SIZE = 32;
  parameter      DATA_SIZE = 8;
  parameter      NUM_REGS = 4;
  input         clk, rst, done, outAccepted, loadData;
  input [DATA_SIZE - 1:0] dataIn;
  output [BUS_SIZE - 1:0] dataOut;
  reg    [DATA_SIZE - 1:0] buffer [NUM_REGS-1:0];

  integer          i;
```

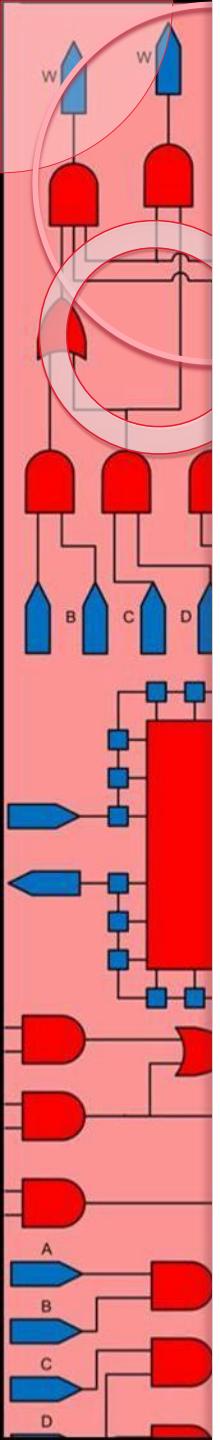

# Output Wrapper:


## Datapath Verilog Code

```
//=====
//Datapath
//=====

    //output register
    always @(posedge clk ) begin
        if( rst ) begin
            for ( i = 0; i < NUM_REGS ; i = i+1 )begin
                buffer[i] <= 0;
            end
        end
        else if( loadData ) begin
            for ( i = NUM_REGS-1; i > 0 ; i = i-1 )begin
                buffer[i] <= buffer[i-1];
            end
            buffer[0] <= dataIn;
        end
    end

    assign dataOut={buffer[3],buffer[2],buffer[1],buffer[0]};

endmodule;
```

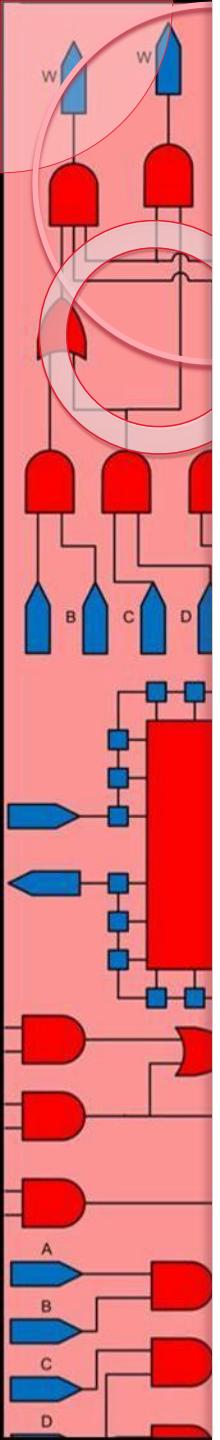

# Output Wrapper :

## Controller Verilog Code

```
'define RESET          0
#define WAIT_ON_DONE    1
#define GET_DATA         2
#define WAIT_ON_GRANT    3
#define WAIT_ON_OUTACCEPT 4

module outputController ( clk, rst, done, outAccepted, grant, , dataIn,
                         .....                                outReady, loadData, req );
  parameter DATA_SIZE = 8;
  input      .....                                clk, rst, done, outAccepted, grant;
  input      [DATA_SIZE-1:0] dataIn;
  output reg .....                                outReady, loadData, req;
  reg       [2:0]   ns, ps;
  reg       [2:0]   .....                                count;
  reg       .....                                countDone;
  reg       .....                                counterEn;

  //combinational part
  always @ ( ps or rst or done or outAccepted or countDone or grant ) begin
    outReady = 0;
    counterEn = 0;
    loadData = 0;
    req = 0;
```


# Output Wrapper :

## Controller Verilog Code

```
case ( ps )
    `RESET: begin
        if ( rst == 0 )
            ns = `WAIT_ON_DONE;
        else
            ns = `RESET;
    end
    `WAIT_ON_DONE: begin
        if ( done == 1 )
            ns = `GET_DATA;
        else
            ns = `WAIT_ON_DONE;
    end
    `GET_DATA: begin
        loadData = 1;
        counterEn = 1;
        if ( countDone )
            ns = `WAIT_ON_GRANT;
        else
            ns = `WAIT_ON_DONE;
    end
    `WAIT_ON_GRANT: begin
        req = 1;
        if ( grant )
            ns = `WAIT_ON_OUTACCEPT;
        else
            ns = `WAIT_ON_GRANT;
    end
```

```
`define R
`define W
`define G
`define W
`define W

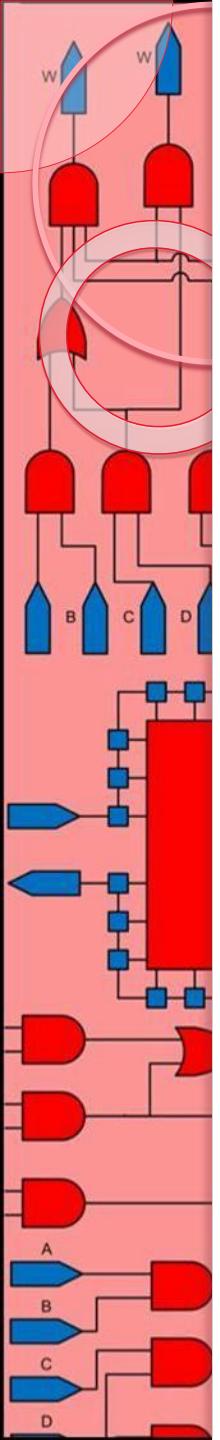
module ou
    ...
param
input
input
output
reg
reg
reg
reg
reg
//com
always
outRe
count
loadD
req =
```



# Output Wrapper :
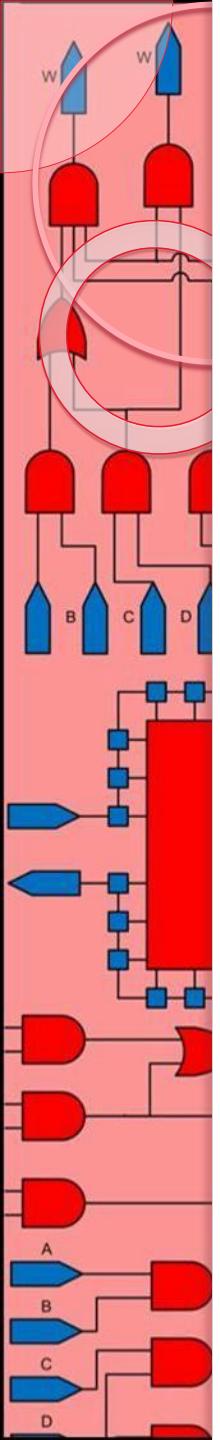
## Controller Verilog Code

```
'WAIT_ON_OUTACCEPT:begin
    outReady = 1;
    if ( outAccepted )
        ns = `WAIT_ON_DONE;
    else
        ns = `WAIT_ON_OUTACCEPT;
    end
endcase
end
//sequential part
always @ ( posedge clk ) begin
    if ( rst == 1 )
        ps <= `RESET;
    else
        ps <= ns;
end
//Up Counter
always @ ( posedge clk ) begin
    if( rst )
        count <= 0;
    else if( counterEn )
        count <= count + 1;
end
//Comparator
always @ ( count ) begin
    if( rst )
        countDone = 0;
    else if ( count==4 )
        countDone = 1;
    else
        countDone = 0;
end
```



# Output Wrapper :

## Complete Verilog Code

```
module outputWrapper ( clk, rst, dataIn, outAccepted, grant, busy,
                      done, outReady, dataOut, req );

  parameter BUS_SIZE = 32;
  parameter DATA_SIZE = 8;

  input          clk, rst, outAccepted, busy, done, grant;
  input  [DATA_SIZE-1:0] dataIn;


  output [BUS_SIZE-1:0] dataOut;
  output          outReady, req;

  wire           countDone, loadData, counterEn, loadInput;

  outputDatapath #(BUS_SIZE, DATA_SIZE) datapath
    ( clk, rst, done, outAccepted, loadData,
      dataIn, dataOut );
  ...

  outputController #(DATA_SIZE) controller
    ( clk, rst, done, outAccepted, grant, dataIn,
      outReady, loadData, req );
  ...


endmodule;
```

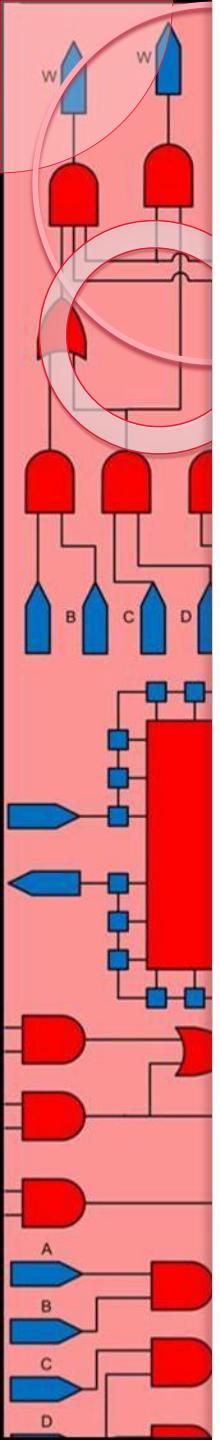


# Complete System

```
[module top ( clk, rst, inReady, grant, dataIn,
    . . . . . inAccepted, outAccepted, outReady, req, dataBus );
parameter   BUS_SIZE = 32;
parameter   DATA_SIZE = 8;
input        clk, rst, inReady, req;
input [BUS_SIZE-1:0] dataIn;
output       inAccepted, outAccepted, grant, outReady, grant;
output [BUS_SIZE-1:0] dataBus;
wire         start, busy, done;
wire [DATA_SIZE-1:0] dataOut;
wire [DATA_SIZE-1:0] data;
wire [DATA_SIZE-1:0] FloatingPart;
wire [1:0]      integerPart;
inputWrapper #(BUS_SIZE, DATA_SIZE)    inw
( clk, rst, dataIn, inReady, busy, done, inAccepted, start, dataOut );
exp          #(DATA_SIZE, 3, 3)         inst1
( clk, rst, start, dataOut, busy, done, integerPart, FloatingPart);
outputWrapper #(BUS_SIZE, DATA_SIZE)   outw
( clk, rst, data, outAccepted, grant, busy, done, outReady, dataBus, req );
//select most significant bits
assign data = {integerPart, FloatingPart[DATA_SIZE-1:DATA_SIZE-6]};
endmodule
```


# Complete System

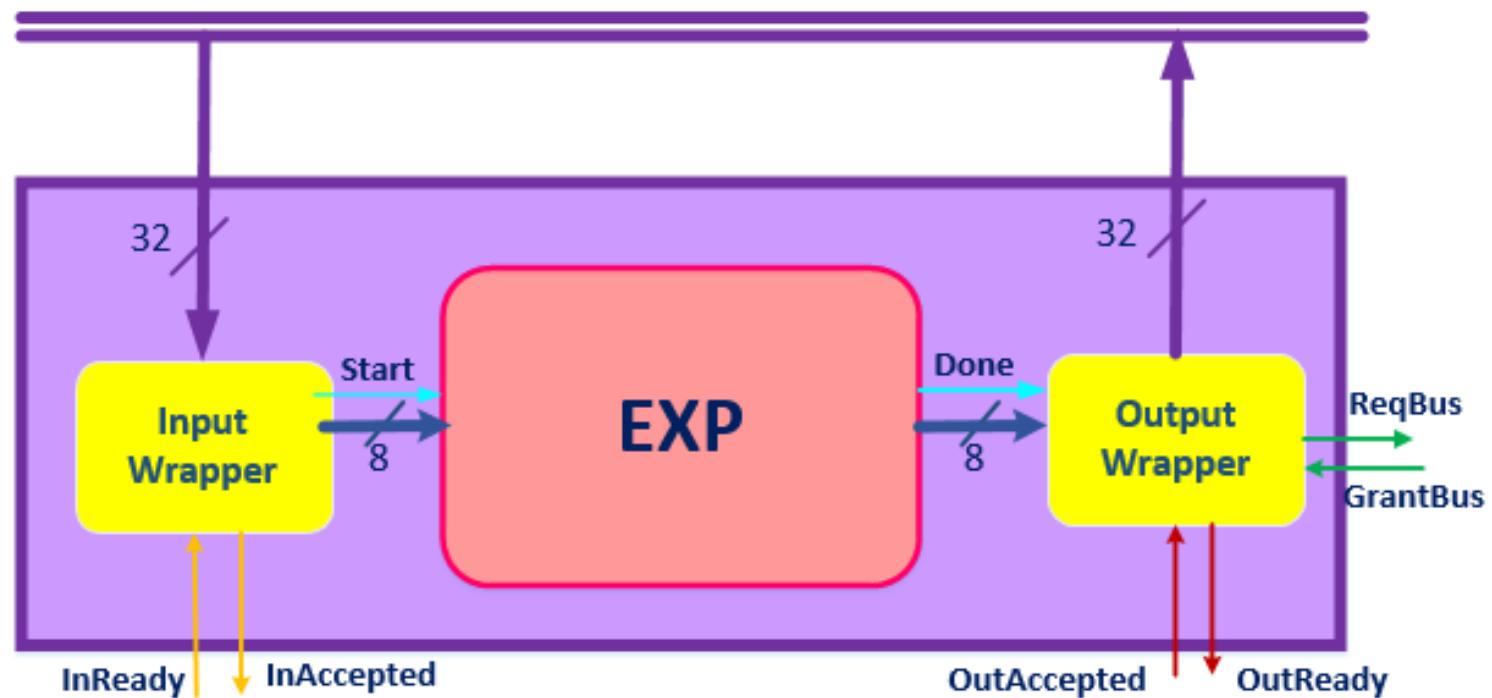

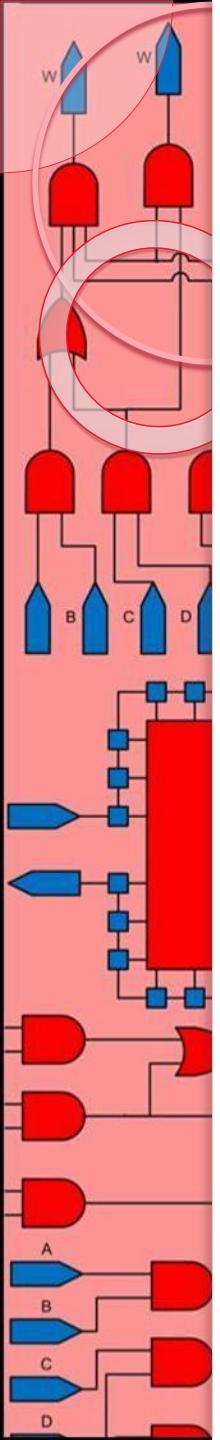

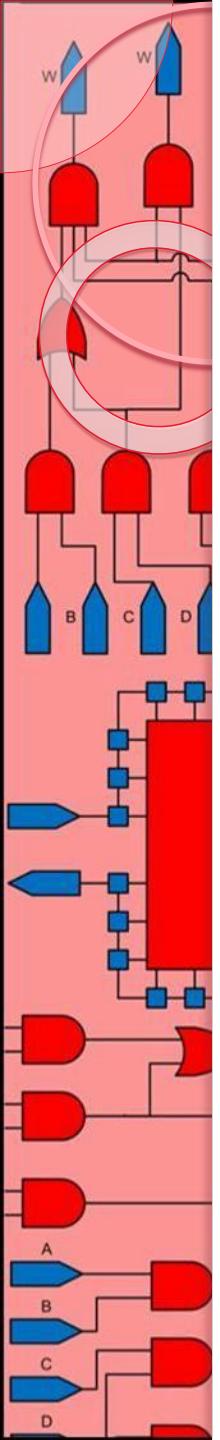
# Summary

- Overview
- PE and IO wrappers
- A PE example (includes Verilog)
  - Datapath controller partitioning
  - Datapath design
  - Controller design
- IO wrappers
  - Datapath controller partitioning
  - Datapath design
  - Controller design
- Summary


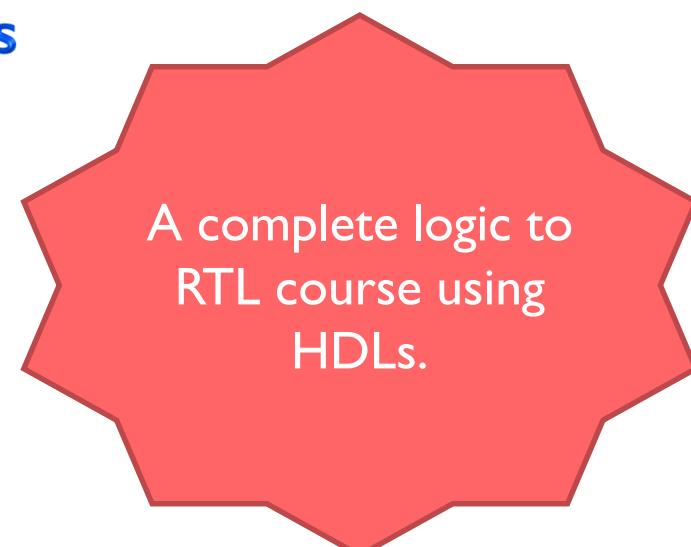
# Series Summary

- Basics of logic - Verilog
- Transistor and gate level timing - Verilog
- Boolean expressions – Verilog
- Behavioral logic description – Verilog
- Flip-flops – Verilog
- Combinational RTL elements
- Sequential RTL elements
- RTL design methodology
- Handshaking
- RTL PEs
- RTL Communications
- Complete systems



A complete logic to  
RTL course using  
HDLs.